

Name \_\_\_\_\_


Partial credit will be given if you show your work.

1. (25 pts.) Given the following truth table, find the minimum-cost sum-of-products (SOP) expression for  $f$ .

Row #	$x_1$	$x_2$	$x_3$	$f$
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

2. (25 pts.) Implement the multiplexer circuit using NAND gates. A multiplexer implements the following function:  $f = \bar{s}x_1 + sx_2$ .

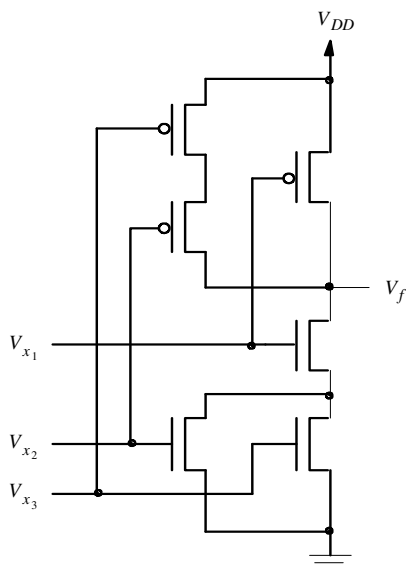3. (25 pts.) Find the function  $f$  the following circuit implements.



4. (25 pts.) In a CMOS inverter assume that  $k'_n = 20 \frac{\mu A}{V^2}$ ,  $k'_p = 0.4 \times k'_n$ ,  $\frac{W_n}{L_n} = \frac{W_p}{L_p} = \frac{5.0 \mu m}{0.5 \mu m}$ ,  $V_{DD} = 5V$ . If the inverter drives a capacitance of 150 fF, find the longest propagation delay we can expect from this gate.