


**EE 211 Circuit and Signals I, Fall 2012**  
**Exam 1 September 21, 2012**  
**Solution**

**Rules:** This is a closed-book exam. You may use only your brain, a calculator and pen/paper. Each numbered question counts equally toward your grade.

**Grading policy:** Only boxed answers count. If you have boxed the correct answer and show enough relevant math you get 10. If only one of them you get 5. Otherwise you get 0. Always include the unit on every answer and reduce to simple form!

**Node analysis**

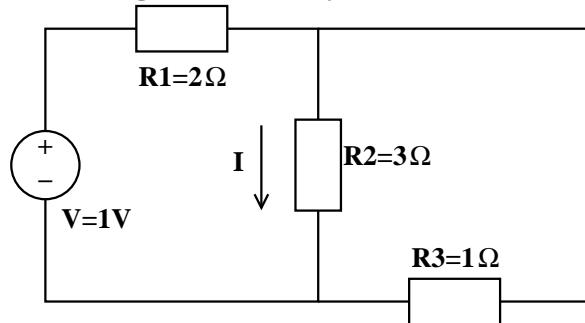1. Compute current  $I$  using nodal analysis.




$$\frac{IR_2 - V}{R_1} + \frac{IR_2}{R_3} + I = 0$$

$$I \left( \frac{R_2}{R_1} + \frac{R_2}{R_3} + 1 \right) = \frac{V}{R_1}$$

$$I = \frac{1}{11} \text{ A}$$

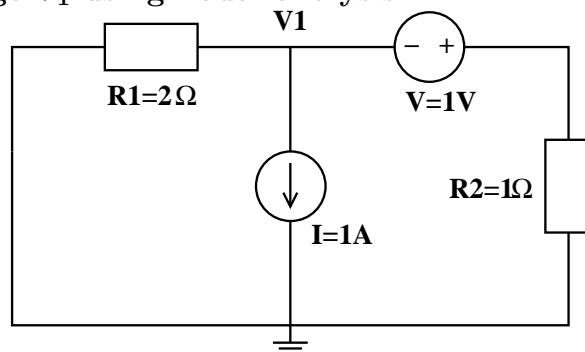2. Compute voltage  $V_1$  using nodal analysis.



$$\frac{V_1}{R_1} + I + \frac{V_2}{R_2} = 0$$

$$V_2 - V_1 = V$$


$$\frac{V_1}{R_1} + I + \frac{V}{R_2} + \frac{V_1}{R_2} = 0$$

$$V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = -I - \frac{V}{R_2}$$

$$V_1 = -\frac{4}{3} V$$

### Mesh analysis

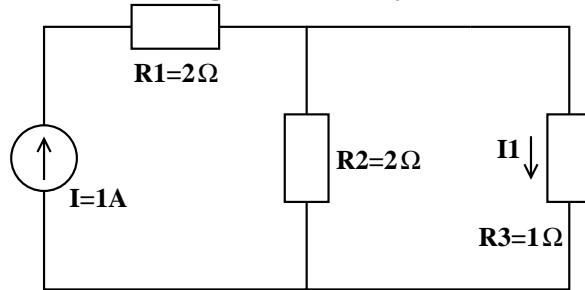
3. Compute the current  $I_1$  using mesh analysis.



$$(I_1 - I) R_2 + I_1 R_3 = 0$$

$$I_1 = \frac{IR_2}{R_2 + R_3} = \frac{2}{2+1} = \frac{2}{3} \text{ A}$$

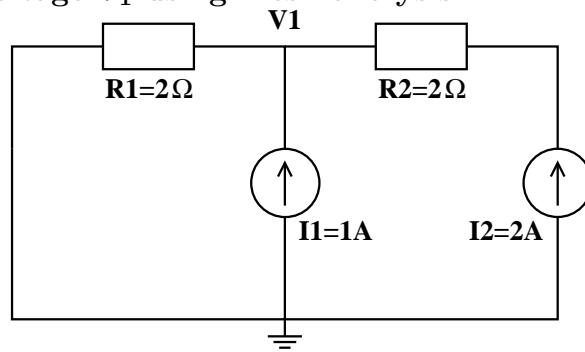4. Compute the voltage  $V_1$  using mesh analysis.



Clockwise mesh currents  $I_A$  (left) and  $I_B$  (right).

$$I_B = -I_2 = -2 \text{ A}$$


$$I_B - I_A = I_1$$

$$I_A = I_B - I_1 = 1 + 2 = 3 \text{ A}$$

$$V_1 = R_1 I_A = 2 \times 3 = 6 \text{ V}$$

### Operational amplifiers

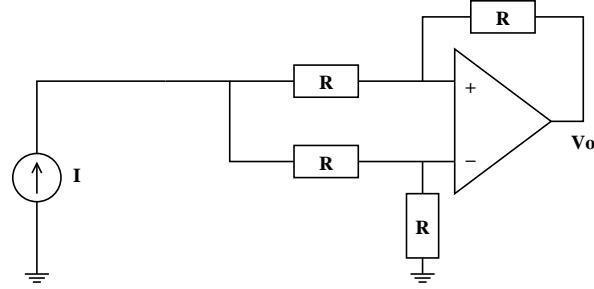5. Compute the gain  $V_O/I$  for this circuit




$$V_+ = \frac{V_I}{2} \quad I_- = I_+ = \frac{I}{2}$$

$$V_+ = V_- = \frac{IR}{2}$$

$$V_O = V_- - \frac{I}{2}R = \frac{IR}{2} - \frac{IR}{2} = 0$$

$$\frac{V_O}{I} = 0$$

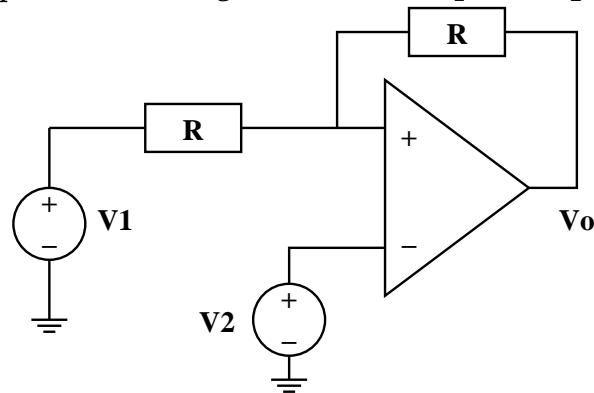6. Compute an expression for  $V_O$  in terms of  $V_1$  and  $V_2$



$$I = \frac{V_1 - V_2}{R}$$

$$V_O = V_2 - IR = V_2 - \frac{V_1 - V_2}{R}R = 2V_2 - V_1$$