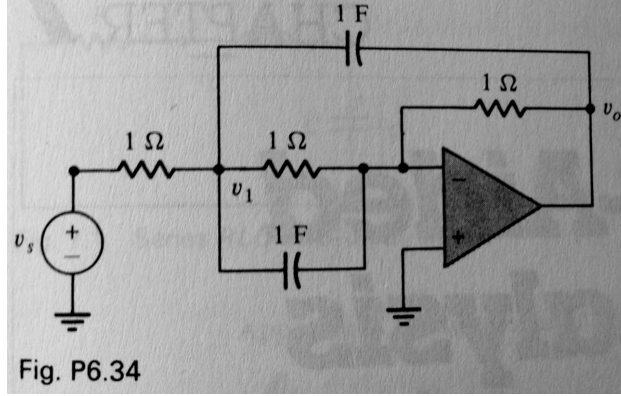


**EE 211 Circuit and Signals I, Fall 2012**  
**Example October 31, 2012**

**Problem 6.34.** For the op-amp circuit shown in Fig. P6.34, find the zero-state step response  $v_1(t)$  for the case that  $v_s(t) = u(t)$  V.



First, come up with the general differential equation for  $v_1$  for  $t > 0$ .

Nodal analysis at  $v_1$  produces

$$\frac{v_s - v_1}{R} + C \frac{d(v_o - v_1)}{dt} - \frac{v_1}{R} - C \frac{dv_1}{dt} = 0 \quad (1)$$

we need to eliminate  $v_o$  from that equation. We can, for example, say that

$$v_o = -i_F R$$

where  $i_F$  is the current flowing from inverting input to  $v_o$ , and then

$$i_F = \frac{v_1}{R} + C \frac{dv_1}{dt}$$

Inserting in equation 1 we get

$$\frac{v_s - v_1}{R} - C \frac{d}{dt} \left[ v_1 + RC \frac{dv_1}{dt} \right] - C \frac{dv_1}{dt} - \frac{v_1}{R} - C \frac{dv_1}{dt} = 0$$

$$\frac{v_s}{R} - \frac{v_1}{R} - C \frac{dv_1}{dt} - RC^2 \frac{d^2 v_1}{dt^2} - C \frac{dv_1}{dt} - \frac{v_1}{R} - C \frac{dv_1}{dt} = 0$$

Assembling same derivatives of  $v_1$  we get

$$RC^2 \frac{d^2 v_1}{dt^2} + 3C \frac{dv_1}{dt} + \frac{2}{R} v_1 = \frac{v_s}{R}$$

$$\frac{d^2 v_1}{dt^2} + \frac{3}{RC} \frac{dv_1}{dt} + \frac{2}{R^2 C^2} v_1 = \frac{v_s}{R^2 C^2} \quad (2)$$

Now we have it in the standard form and

$$\alpha = \frac{1}{2} \frac{3}{RC} = \frac{3}{2RC} \quad \omega_n = \sqrt{\frac{2}{R^2 C^2}} = \frac{\sqrt{2}}{RC}$$

What mode is this?

$$\alpha = \frac{3}{2RC} = \frac{3}{2} \quad \omega_n = \frac{\sqrt{2}}{RC} = \sqrt{2} \approx 1.41$$

Since  $\alpha > \omega_n$  the mode is overdamped with the solution

$$v_1 = A_1 e^{s_1 t} + A_2 e^{s_2 t} + K$$

where

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_n^2} = -\frac{3}{2} \pm \sqrt{\frac{9}{4} - 2} = -\frac{3}{2} \pm \frac{1}{2} = -1, -2$$

For  $t \rightarrow \infty$  the capacitors act as open circuits and  $v_1 = \frac{v_s}{2} = K$ . The solution is now

$$v_1 = A_1 e^{-1t} + A_2 e^{-2t} + \frac{v_s}{2} \quad (3)$$

Next we need to use the initial conditions. We are looking for the zero-state response, so we know that for  $t < 0$   $v_1(t) = 0$  and  $v_1'(t) = 0$ .

For  $t > 0$  we have that

$$v_1(t) = v_C(t) = \frac{1}{C} \int_0^t i_C dt$$

Since the current is finite and the integral is over zero time it must be that  $v_1(0+) = 0$ . and thus

$$A_1 + A_2 + \frac{v_s}{2} = 0 \quad (4)$$

Next we need to find the initial condition on  $v_1'(0+)$ . Notice  $v_0 = v_1 = 0$  because the voltage across the capacitor is initially zero. Since we have from earlier

$$v_o = -i_F R = -v_1 + RC \frac{dv_1}{dt}$$

we get

$$\frac{dv_1}{dt}(0) = 0 \quad (5)$$

which gives us

$$-A_1 - 2A_2 = 0 \quad (6)$$

From this we get that  $A_2 = -\frac{A_1}{2}$ . Inserting into equation 4 we get

$$A_1 - \frac{A_1}{2} + \frac{v_s}{2} = 0$$

$$A_1 = -v_s = -1 \quad (7)$$

and then

$$A_2 = -\frac{A_1}{2} = \frac{v_s}{2} = \frac{1}{2} \quad (8)$$

The expression for  $v_1$  now looks like

$$\begin{aligned} v_1(t) &= \begin{cases} 0 & t < 0 \\ -e^{-t} + \frac{1}{2}e^{-2t} + \frac{1}{2} & 0 \leq t \end{cases} \\ &= \left[ -e^{-t} + \frac{1}{2}e^{-2t} + \frac{1}{2} \right] u(t) \end{aligned} \quad (9)$$

and here is a plot of that curve and its components.

