

bias current of  $1 \mu\text{A}$  and an offset current of  $0.1 \mu\text{A}$ , what range of outputs would you expect? Indicate where you would add an additional resistor to compensate for the bias currents. What does the range of possible outputs then become? A designer wishes to use this amplifier with a  $15\text{-k}\Omega$  source. In order to compensate for the bias current in this case, what resistor would you use? And where?

**D2.106** The circuit of Fig. 2.36 is used to create an ac-coupled noninverting amplifier with a gain of  $200 \text{ V/V}$  using resistors no larger than  $100 \text{ k}\Omega$ . What values of  $R_1$ ,  $R_2$ , and  $R_3$  should be used? For a break frequency due to  $C_1$  at  $100 \text{ Hz}$ , and that due to  $C_2$  at  $10 \text{ Hz}$ , what values of  $C_1$  and  $C_2$  are needed?

**\*2.107** Consider the difference amplifier circuit in Fig. 2.16. Let  $R_1 = R_3 = 10 \text{ k}\Omega$  and  $R_2 = R_4 = 1 \text{ M}\Omega$ . If the op amp has  $V_{os} = 4 \text{ mV}$ ,  $I_B = 0.3 \mu\text{A}$ , and  $I_{os} = 50 \text{ nA}$ , find the worst-case (largest) dc offset voltage at the output.

**\*2.108** The circuit shown in Fig. P2.108 uses an op amp having a  $\pm 4\text{-mV}$  offset. What is its output offset voltage? What does the output offset become with the input ac coupled through a capacitor  $C$ ? If, instead, the  $1\text{-k}\Omega$  resistor is capacitively coupled to ground, what does the output offset become?

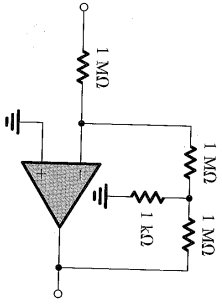


FIGURE P2.108

**2.109** Using offset-nulling facilities provided for the op amp, a closed-loop amplifier with gain of  $+1000$  is adjusted at  $25^\circ\text{C}$  to produce zero output with the input grounded. If the input offset-voltage drift of the op amp is specified to be  $10 \mu\text{V}/^\circ\text{C}$ , what output would you expect at  $0^\circ\text{C}$  and at  $75^\circ\text{C}$ ? While nothing can be said separately about the polarity of the output offset at either  $0$  or  $75^\circ\text{C}$ , what would you expect their relative polarities to be?

**2.110** An op amp is connected in a closed loop with gain of  $+100$  utilizing a feedback resistor of  $1 \text{ M}\Omega$ .

(a) If the input bias current is  $100 \text{ nA}$ , what output voltage results with the input grounded?

(b) If the input offset voltage is  $\pm 1 \text{ mV}$  and the input bias current as in (a), what is the largest possible output that can be observed with the input grounded?  
 (c) If bias-current compensation is used, what is the value of the required resistor? If the offset current is no more than one-tenth the bias current, what is the resulting output offset voltage (due to offset current alone)?  
 (d) With bias-current compensation as in (c) in place, what is the largest dc voltage at the output due to the combined effect of offset voltage and offset current?

**\*2.111** An op amp intended for operation with a closed-loop gain of  $-100 \text{ V/V}$  uses feedback resistors of  $10 \text{ k}\Omega$  and  $1 \text{ M}\Omega$  with a bias-current-compensation resistor  $R_3$ . What should the value of  $R_3$  be? With input grounded, the output offset voltage is found to be  $+0.21 \text{ V}$ . Estimate the input offset current assuming zero input offset voltage. If the input offset voltage can be as large as  $1 \text{ mV}$  of unknown polarity, what range of offset current is possible? What current injected into, or extracted from, the nongrounded end of  $R_3$  would reduce the op amp output voltage to zero? For available  $\pm 15\text{-V}$  supplies, what resistor and supply voltage would you use?

**SECTION 2.8: INTEGRATORS AND DIFFERENTIATORS**

**2.112** A Miller integrator incorporates an ideal op amp, a resistor  $R$  of  $100 \text{ k}\Omega$ , and a capacitor  $C$  of  $10 \text{ nF}$ . A sine-wave signal is applied to its input.

- (a) At what frequency (in Hz) are the input and output signals equal in amplitude?
- (b) At that frequency how does the phase of the output sine wave relate to that of the input?
- (c) If the frequency is lowered by a factor of  $10$  from that found in (a), by what factor does the output voltage change, and in what direction (smaller or larger)?
- (d) What is the phase relation between the input and output in situation (c)?

**D2.113** Design a Miller integrator with a time constant of one second and an input resistance of  $100 \text{ k}\Omega$ . For a dc voltage of  $-1$  volt applied at the input, at time  $0$ , at which moment  $v_o = -10 \text{ V}$ , how long does it take the output to reach  $0 \text{ V}$  or  $+10 \text{ V}$ ?

**2.114** An op-amp-based inverting integrator is measured at  $1 \text{ kHz}$  to have a voltage gain of  $-100 \text{ V/V}$ . At what frequency is its gain reduced to  $-1 \text{ V/V}$ ? What is the integrator time constant?

**D2.115** Design a Miller integrator that has a unity-gain frequency of  $1 \text{ Krad/s}$  and an input resistance of  $100 \text{ k}\Omega$ . Sketch the output you would expect for the situation in which, with output initially at  $0 \text{ V}$ , a  $2\text{-V}$   $2\text{-ms}$  pulse is applied to the input. Characterize the output that results when a sine wave  $2 \text{ sin } 1000t$  is applied to the input?

**D2.116** Design a Miller integrator whose input resistance is  $20 \text{ k}\Omega$  and unity-gain frequency is  $10 \text{ kHz}$ . What components are needed? For long-term stability, a feedback resistor is introduced across the capacitor, which limits the dc gain to  $40 \text{ dB}$ . What is its value? What is the associated lower  $3\text{-dB}$  frequency? Sketch and label the output which results with a  $0.1\text{-ms}$ ,  $1\text{-V}$  positive-input pulse (initially at  $0 \text{ V}$ ) with (a) no dc stabilization (but with the output initially at  $0 \text{ V}$ ) and (b) the feedback resistor connected.

**\*2.117** A Miller integrator whose input and output voltages are initially zero and whose time constant is  $1 \text{ ms}$  is driven by the signal shown in Fig. P2.117. Sketch and label the output waveform that results. Indicate what happens if the input levels are  $\pm 2 \text{ V}$ , with the time constant the same ( $1 \text{ ms}$ ) and with the time constant raised to  $2 \text{ ms}$ .

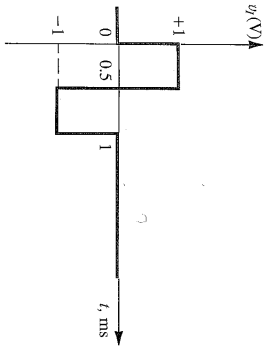


FIGURE P2.117

**2.118** Consider a Miller integrator having a time constant of  $1 \text{ ms}$ , and whose output is initially zero, when fed with a string of pulses of  $10\text{-}\mu\text{s}$  duration and  $1\text{-V}$  amplitude rising from  $0 \text{ V}$  (see Fig. P2.118). Sketch and label the output waveform resulting. How many pulses are required for an output voltage change of  $1 \text{ V}$ ?

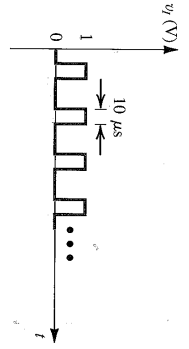


FIGURE P2.118

**D2.119** Figure P2.119 shows a circuit that performs a low-pass STC function. Such a circuit is known as a first-order low-pass active filter. Derive the transfer function and show that the dc gain is  $(-R_2/R_1)$  and the  $3\text{-dB}$  frequency

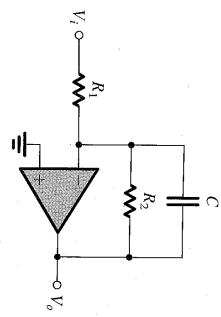


FIGURE P2.119

**2.120** A Miller integrator with  $R = 10 \text{ k}\Omega$  and  $C = 10 \text{ nF}$  is implemented using an op amp with  $V_{os} = 3 \text{ mV}$ ,  $I_B = 0.1 \mu\text{A}$ , and  $I_{os} = 10 \text{ nA}$ . To provide a finite dc gain, a  $1\text{-M}\Omega$  resistor is connected across the capacitor.

- (a) To compensate for the effect of  $I_{os}$ , a resistor is connected in series with the positive-input terminal of the op amp. What should its value be?
- (b) With the resistor of (a) in place, find the worst-case dc output voltage of the integrator when the input is grounded.

**2.121** A differentiator utilizes an ideal op amp, a  $10\text{-k}\Omega$  resistor, and a  $0.01\text{-}\mu\text{F}$  capacitor. What is the frequency  $f_0$  (in Hz) at which its input and output sine-wave signals have equal magnitude? What is the output signal for a  $1\text{-V}$  peak-to-peak sine-wave input with frequency equal to  $10/f_0$ ?

**2.122** An op-amp differentiator with  $1\text{-ms}$  time constant is driven by the rate-controlled step shown in Fig. P2.122. Assuming  $v_o$  to be zero initially, sketch and label its waveform.

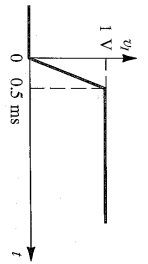


FIGURE P2.122

**\*2.123** An op-amp differentiator, employing the circuit shown in Fig. 2.44(a), has  $R = 10 \text{ k}\Omega$  and  $C = 0.1 \mu\text{F}$ . When a triangle wave of  $\pm 1\text{-V}$  peak amplitude at  $1 \text{ kHz}$  is applied to the input, what form of output results? What is its frequency? What is its peak amplitude? What is its average value? What value of  $R$  is needed to cause the output to have a  $10\text{-V}$  peak amplitude? When a  $1\text{-V}$  peak sine wave at  $1 \text{ kHz}$  is applied to