


EE 321 Analog Electronics, Fall 2011
Exam 4 December 12, 2011
Solution

Rules: This is a closed-book exam. You may use only your brain, a calculator and pen/paper. Each numbered question counts equally toward your grade.

Note: The questions are designed to test your conceptual understanding, not your ability to do many pages of math. If you find yourself doing long calculations there is a high probability that you are doing something wrong.

Operational amplifier

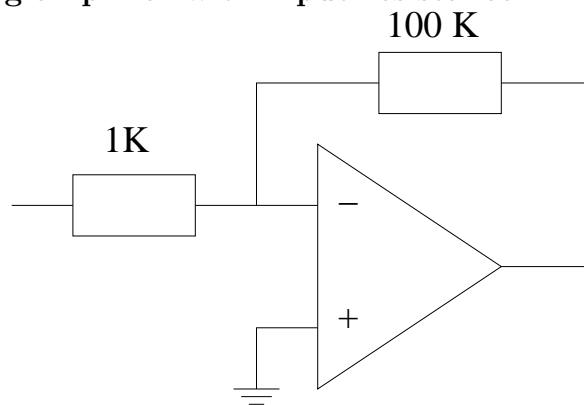1. Draw an inverting amplifier with input resistance $1\text{ k}\Omega$ and gain of -100 .




2. Compute the output voltage due to an input offset voltage of 1 mV .


The offset voltage is amplified by the non-inverting gain, so

$$V_{\text{out}} = \left(1 + \frac{R_2}{R_1}\right) V_{OS} = 101 \times 1\text{ mV} = 0.101\text{ V}$$

Diode

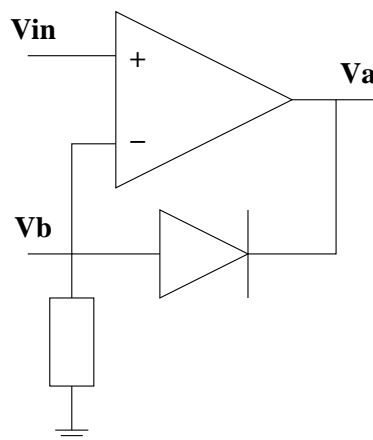


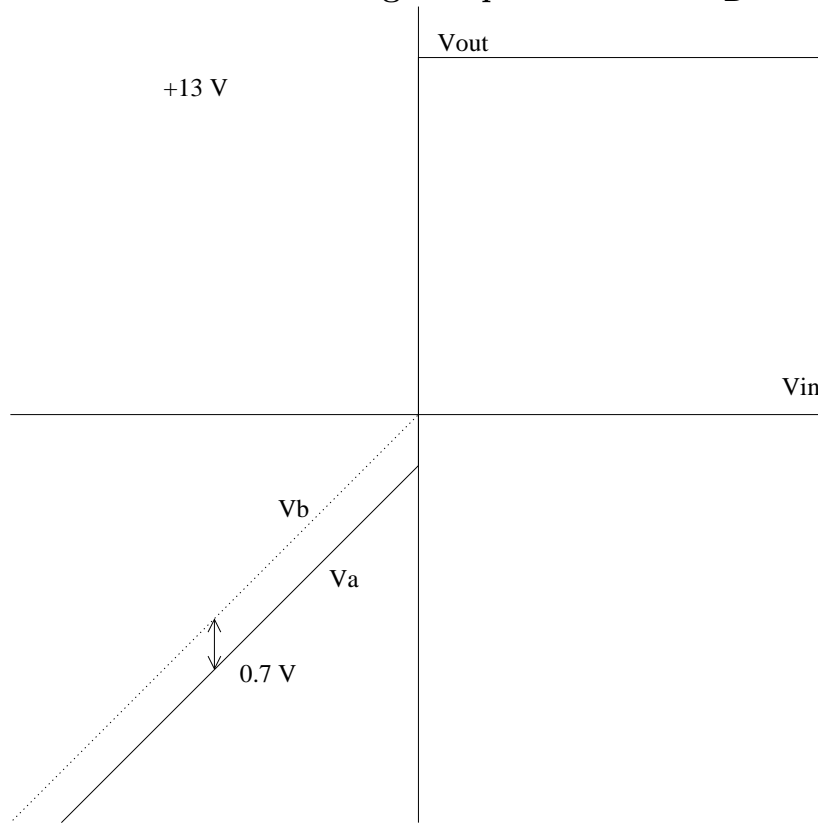3. Carefully plot the labeled voltages V_A and V_B as a function of V_{in} between -5 and +5 V. The saturation voltage levels of the op-amp are ± 13 V. For the diode assume the fixed voltage drop model with $V_D = 0.7$ V.



BJT

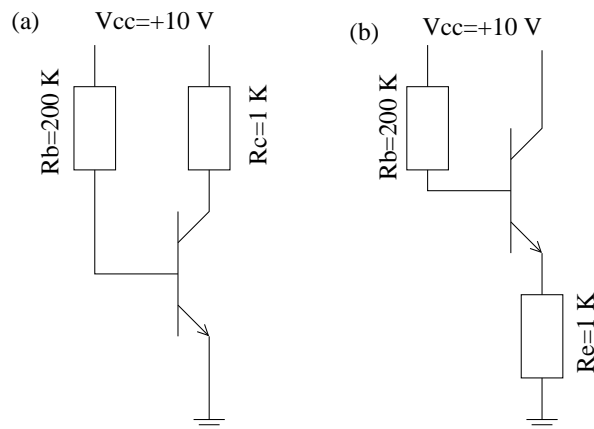4. Find all voltages and currents in these two circuits (assume $\beta = 100$)



- (a) Assume active mode operation

$$V_{CC} = i_B R_B + V_{BE}$$

$$i_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{10 - 0.7}{200} = 46.5 \mu\text{A}$$

$$i_C = \beta i_B = 4.65 \text{ mA}$$

$$v_C = V_{CC} - i_C R_C = 10 - 4.65 \times 1 = 5.35 \text{ V}$$

$$v_B = V_{BE} = 0.7 \text{ V}$$

active mode confirmed

$$v_E = 0$$

$$i_E = (\beta + 1) i_B = 4.70 \text{ mA}$$

(b) This BJT is obviously in active mode

$$V_{CC} = i_B R_B + V_{BE} + i_E R_E = i_B [R_B + (\beta + 1) R_E] + V_{BE}$$

$$i_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} = \frac{10 - 0.7}{200 + 101 \times 1} = 30.9 \mu\text{A}$$

$$v_B = V_{CC} - i_B R_B = 10 - 30.9 \times 200 = 3.82 \text{ V}$$


$$i_C = \beta i_B = 100 \times 30.9 \times 10^{-6} = 3.09 \text{ mA}$$

$$v_C = V_{CC} = 10 \text{ V}$$

$$i_E = (\beta + 1) i_B = 101 \times 30.9 \times 10^{-6} = 3.12 \text{ mA}$$

$$v_E = i_E R_E = 3.12 \times 1 = 3.12 \text{ V}$$

MOSFET

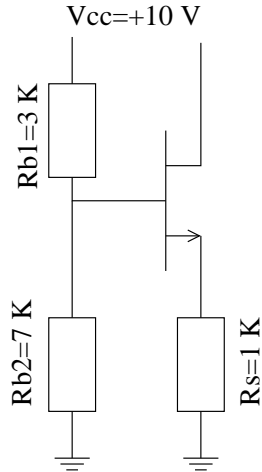

5. Compute the voltages and currents for this circuit. Use $V_t = 2 \text{ V}$ and $k'_n \frac{W}{L} = 1 \frac{\text{mA}}{\text{V}^2}$

First we see that $V_G = 7 \text{ V}$. We also know that $I_G = 0$. The MOSFET is in saturation mode so that

$$i_D = \frac{k'_n W}{2 L} (v_{GS} - V_t)^2$$

$$v_{GS} = V_G - i_D R_S$$

$$i_D = \frac{k'_n W}{2 L} (V_G - i_D R_S - V_t)^2$$

$$i_D = \frac{k'_n W}{2 L} [i_D^2 R_S^2 + (V_G - V_t)^2 - 2i_D R_S (V_G - V_t)]$$

$$\frac{k'_n W}{2 L} R_S^2 i_D^2 - 2 \frac{k'_n W}{2 L} i_D R_S (V_G - V_t) - i_D + (V_G - V_t)^2 = 0$$

$$i_D^2 - 13i_D + 36 = 0$$

$$i_D = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A} = \frac{13 \pm 5}{2} = 4 \text{ mA or } 9 \text{ mA}$$

$i_D = 4 \text{ mA}$ is the only answer that is consistent with saturation mode.