

EE 321 Analog Electronics, Fall 2011 Homework #6 solution

5.15. (a) Use the Ebers-Moll expressions in Eqs. 5.26 and 5.27 to show that the i_C - v_{CB} relationship sketch in Fig. 59. can be described by

$$i_C = \alpha_F I_E - I_S \left(\frac{1}{\alpha_R} - \alpha_F \right) e^{\frac{v_{BC}}{V_T}}$$

(b) Calculate and sketch i_C - v_{CB} curves for a transistor for which $I_S = 10^{-15}$ A, $\alpha_F \approx 1$, and $\alpha_R = 0.1$. Sketch graphs for $I_E = 0.1$ mA, 0.5 mA, and 1 mA. For each, give the values of v_{BC} , v_{BE} , and v_{CE} for which (a) $i_C = 0.5\alpha_F I_E$ and (b) $i_C = 0$.

(a) The Ebers-Moll equations are

$$i_E = \frac{I_S}{\alpha_F} \left(e^{\frac{v_{BE}}{V_T}} - 1 \right) - I_S \left(e^{\frac{v_{BC}}{V_T}} - 1 \right)$$

$$i_C = I_S \left(e^{\frac{v_{BE}}{V_T}} - 1 \right) - \frac{I_S}{\alpha_R} \left(e^{\frac{v_{BC}}{V_T}} - 1 \right)$$


Eliminate $e^{\frac{v_{BE}}{V_T}}$ from the second equation by substituting the first equation into it. i_C is then a function of i_E (which the book assumes fixed biased so it calls it I_E) and v_{BC} . Re-arrange the first equation:

$$I_S \left(e^{\frac{v_{BC}}{V_T}} - 1 \right) = \alpha_F I_E + \alpha_F I_S \left(e^{\frac{v_{BC}}{V_T}} - 1 \right)$$

Insert in the second equation

$$\begin{aligned} i_C &= \alpha_F I_E + \alpha_F I_S \left(e^{\frac{v_{BC}}{V_T}} - 1 \right) - \frac{I_S}{\alpha_R} \left(e^{\frac{v_{BC}}{V_T}} - 1 \right) \\ &= \alpha_F I_E - I_S \left(\frac{1}{\alpha_R} - \alpha_F \right) e^{\frac{v_{BC}}{V_T}} \end{aligned}$$

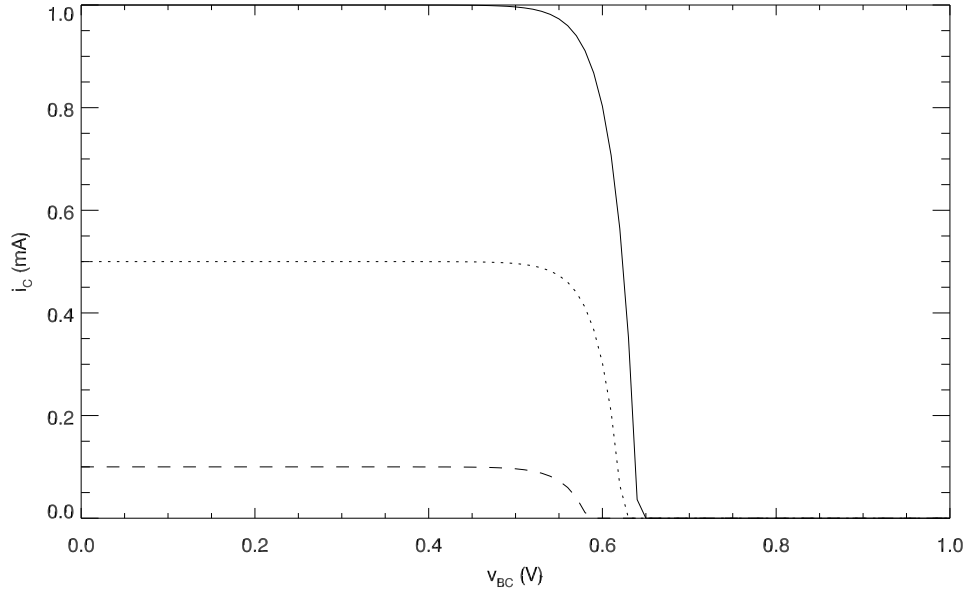(b) This plot shows i_C as a function of v_{CB} .



The solid curve is for $i_C = 1$ mA, the dotted is for $i_C = 0.5$ mA, and the dashed is for $i_C = 0.1$ mA.

(a) The value of v_{CB} for which $i_C = 0.5\alpha_F I_E$ can be found from

$$0.5\alpha_F I_E = \alpha_F I_E - I_S \left(\frac{1}{\alpha_R} - \alpha_F \right) e^{\frac{v_{BC}}{V_T}}$$

$$v_{BC} = V_T \ln \left(\frac{0.5\alpha_F I_E}{I_S \left(\frac{1}{\alpha_R} - \alpha_F \right)} \right)$$

The values are tabulated here:

I_E	v_{BC}
0.1 mA	0.57 V
0.5 mA	0.61 V
1 mA	0.62 V

(b) The value for v_{CB} for which $i_C = 0$ can be found from

$$0 = \alpha_F I_E - I_S \left(\frac{1}{\alpha_R} - \alpha_F \right) e^{\frac{v_{BC}}{V_T}}$$

$$v_{BC} = V_T \ln \left(\frac{\alpha_F I_E}{I_S \left(\frac{1}{\alpha_R} - \alpha_F \right)} \right)$$

The values are tabulated here

I_E	v_{BC}
0.1 mA	0.58 V
0.5 mA	0.62 V
1 mA	0.64 V

5.20. For the circuits in Fig P5.20, assume that the transistors have very large β . Some measurements have been made on these circuits, with the results indicated in the figure. Find the values of the other labeled voltages and currents.

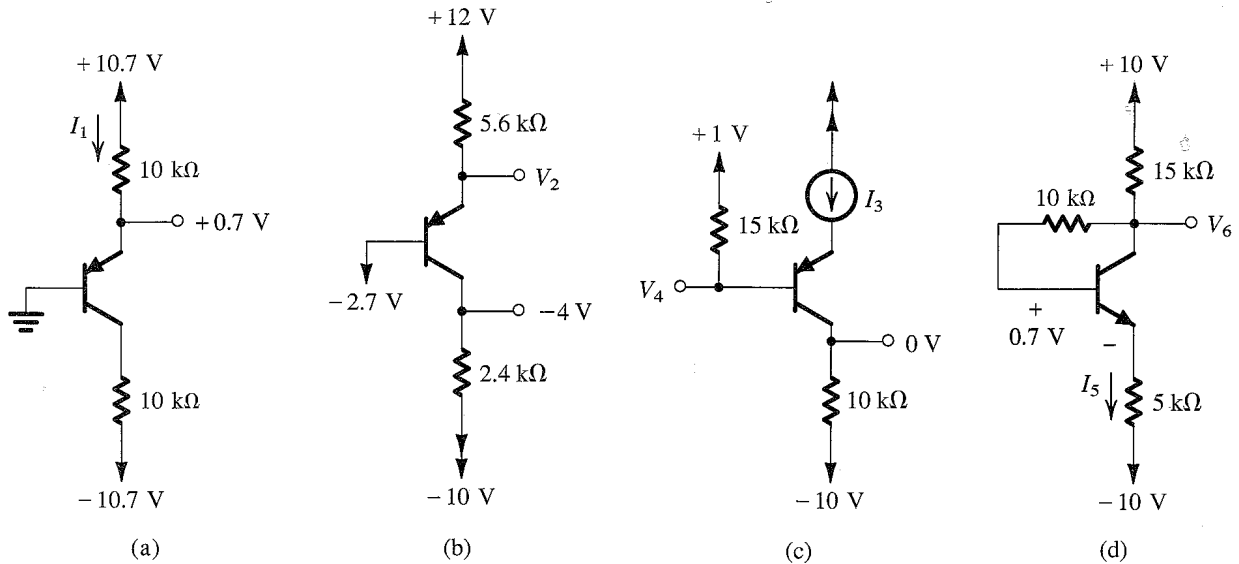


FIGURE P5.20

The hint that β is very large means that we can assume that $i_C = i_E$.

(a) $I_1 = \frac{V_{CC} - V_E}{R_E} = \frac{10.7 - 0.7}{10} = 10 \text{ mA}$

(b) We can see that the transistor must be on, so $V_2 = V_B + V_{BE} = -2.7 + 0.7 = -2 \text{ V}$

(c) The transistor is on because there is collector current flowing.

$$I_3 = I_E = I_C = \frac{V_C - V_{CC}}{R_C} = \frac{0 + 10}{10} = 1 \text{ mA}$$

Since β is very large there is no current flowing in the base, so $V_4 = V_{BE} = 1 \text{ V}$.

(d) Since β is very large there is no current flowing in the base and thus $V_B = V_C$, and we can write

$$V_{CC} - V_{EE} = I_5 (R_C + R_E) + V_{BE}$$

and thus

$$I_5 = \frac{V_{CC} - V_{EE} - V_{BE}}{R_C + R_E} = \frac{10 + 10 - 0.7}{15 + 5} = 0.97 \text{ mA}$$

$$V_6 = V_{CC} - I_C R_C = 10 - 0.97 \times 15 = -4.6 \text{ V}$$

5.21. Measurements on the circuits of Fig. P5.21 produce labeled voltages as indicated. find the value of β for each transistor.

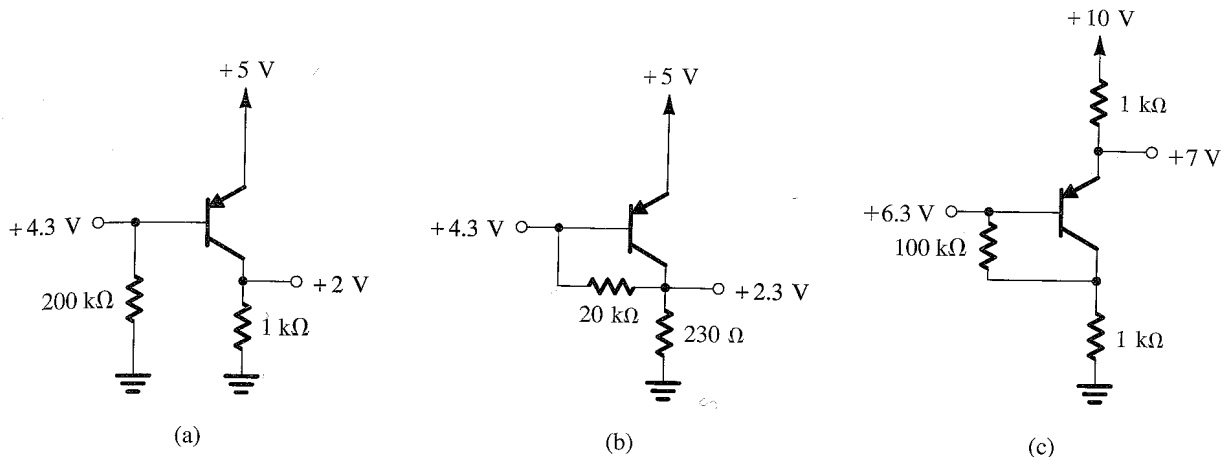


FIGURE P5.21

- (a) $I_B = \frac{V_B}{R_B} = \frac{4.3}{200} = 21.5 \mu\text{A}$, $I_C = \frac{V_C}{R_C} = \frac{2}{1} = 2 \text{ mA}$. We can verify that the transistor is in the active mode since $V_C < V_B$. Then we get $\beta = \frac{I_C}{I_B} = \frac{2000}{21.5} = 93$.
- (b) In this case we have $I_E = \frac{V_C}{R_C} = \frac{2.3}{0.23} = 10 \text{ mA}$. It is I_E because I_B and I_C are merged. We also have $I_B = \frac{V_B - V_C}{R_B} = \frac{4.3 - 2.3}{20} = 0.1 \text{ mA}$. We verify active mode since $V_C < V_B$, and we get $\beta = \frac{I_E}{I_B} - 1 = \frac{10}{0.1} - 1 = 99$.
- (c) $I_E = \frac{V_{EE} - V_E}{R_E} = \frac{10 - 7}{1} = 3 \text{ mA}$. Then it must also be that $V_C = 0 + 3 \text{ V} = 3 \text{ V}$ since $R_C = R_E$ and we have I_E flowing through R_C . Then we have $I_B = \frac{V_B - V_C}{R_B} = \frac{6.3 - 3}{100} = 33 \mu\text{A}$. We verify active mode operation and get $\beta = \frac{I_E}{I_B} - 1 = \frac{3}{0.033} - 1 = 90$.

5.24. for each of the circuits shown in Fig. P5.24, find the emitter, base, and collector voltages and currents. Use $\beta = 30$, but assume $|V_{BE}| = 0.7 \text{ V}$ independent of current level.

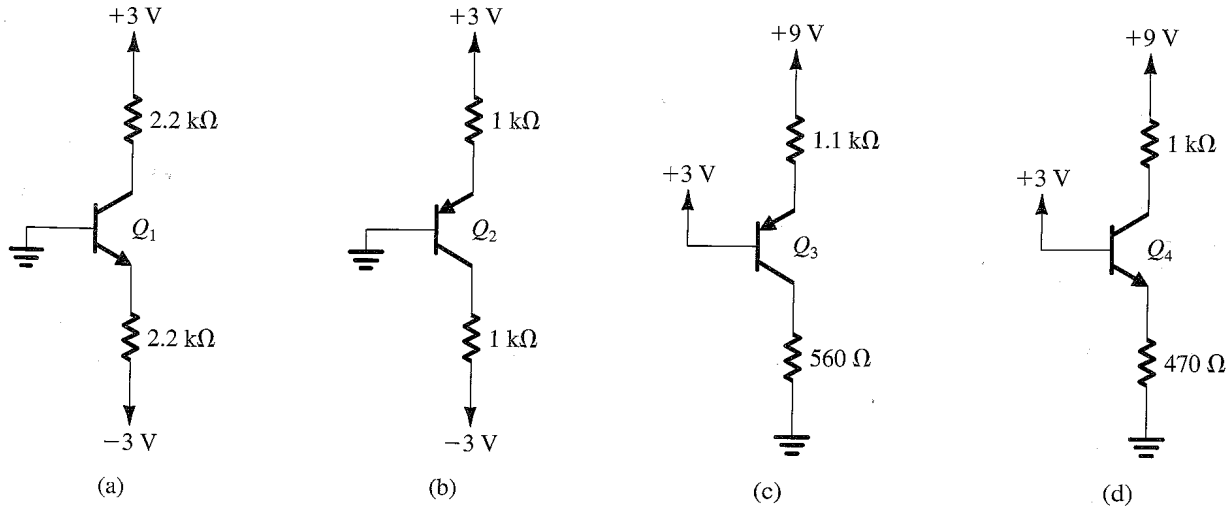


FIGURE P5.24

- (a) First, $V_B = 0\text{ V}$. The transistor must be on, so $V_E = V_B - V_{BE} = 0 - 0.7\text{ V} = -0.7\text{ V}$. Then $I_E = \frac{V_E - V_{EE}}{R_E} = \frac{-0.7 + 3}{2.2} = 1.0\text{ mA}$. Next assume active mode and we get $I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{30}{30 + 1} \times 1.0 = 1.01\text{ mA}$. Then $V_C = V_{CC} - I_C R_C = 3 - 1.01 \times 2.2 = 0.78\text{ V}$. Active mode is verified. Then finally, $I_B = \frac{I_C}{\beta} = \frac{1.01}{30} = 33\text{ }\mu\text{A}$.
- (b) $V_B = 0\text{ V}$. The transistor is on, so $V_E = 0.7\text{ V}$. Then $I_E = \frac{V_{EE} - V_E}{R_E} = \frac{3 - 0.7}{1} = 2.3\text{ mA}$. If we assume active mode then $I_C = \alpha I_E = \frac{30}{30 + 1} \times 2.3 = 2.2\text{ mA}$. Then $V_C = V_{CC} + I_C R_C = 3 + 2.2 = 5.2\text{ V}$, and active mode is verified. Finally, $I_B = \frac{I_C}{\beta} = \frac{2.2}{30} = 73\text{ }\mu\text{A}$.
- (c) $V_B = 3\text{ V}$, and the transistor is on, so $V_E = V_B + V_{EB} = 3 + 0.7 = 3.7\text{ V}$. Then $I_E = \frac{V_{EE} - V_E}{R_E} = \frac{9 - 3.7}{1.1} = 4.8\text{ mA}$. Assuming active mode we get $I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{30}{30 + 1} \times 4.8 = 4.6\text{ mA}$. Then $V_C = R_C I_C = 0.56 \times 4.6 = 2.6\text{ V}$. Since $V_C < V_B$ active mode is verified. Finally, $I_B = \frac{I_C}{\beta} = \frac{4.6}{30} = 153\text{ }\mu\text{A}$.
- (d) $V_B = 3\text{ V}$, and the transistor is on so $V_E = V_B - V_{BE} = 3 - 0.7 = 2.3\text{ V}$. Then $I_E = \frac{V_E}{R_E} = \frac{2.3}{0.47} = 4.9\text{ mA}$. Then, assuming active mode, $I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{30}{30 + 1} \times 4.9 = 4.7\text{ mA}$. Then $V_C = V_{CC} - I_C R_C = 9 - 4.7 \times 1 = 4.3\text{ V}$. Since $V_C > V_B$ active mode is verified. Then finally $I_B = \frac{I_C}{\beta} = \frac{4.7}{30} = 157\text{ }\mu\text{A}$.