

Since we are particularly interested in linear amplification, we will have to devise a way to achieve it in the face of the highly nonlinear behavior of the transistor, namely, that the collector current  $i_C$  is exponentially related to  $v_{BE}$ . We will use the approach described in general terms in Section 1.4. Specifically, we will bias the transistor to operate at a dc base-emitter voltage  $V_{BE}$  and a corresponding dc collector current  $I_C$ . Then we will superimpose the signal to be amplified,  $v_{be}$ , on the dc voltage  $V_{BE}$ . By keeping the amplitude of the signal  $v_{be}$  small, we will be able to constrain the transistor to operate on a short, almost linear segment of the  $i_C$ - $v_{BE}$  characteristic; thus, the change in collector current,  $i_c$ , will be linearly related to  $v_{be}$ . We will study the small-signal operation of the BJT later in this section and in greater detail in Section 5.5. First, however, we will look at the "big picture": We will study the total or large-signal operation of a BJT amplifier. From the transfer characteristic of the circuit, we will be able to see clearly the region over which the circuit can be operated as a linear amplifier. We also will be able to see how the BJT can be employed as a switch.

### 5.3.1 Large-Signal Operation—The Transfer Characteristic

Figure 5.26(a) shows the basic structure (a skeleton) of the most commonly used BJT amplifier, the **grounded-emitter** or **common-emitter (CE)** circuit. The total input voltage  $v_i$  (bias + signal) is applied between base and emitter; that is,  $v_{BE} = v_i$ . The total output voltage  $v_o$  (bias + signal) is taken between collector and ground; that is,  $v_o = v_{CE}$ . Resistor  $R_C$  has two functions: to establish a desired dc bias voltage at the collector, and to convert the collector signal current  $i_c$  to an output voltage,  $v_{ce}$  or  $v_o$ . The supply voltage  $V_{CC}$  is needed to bias the BJT as well as to supply the power needed for the operation of the amplifier.

Figure 5.26(b) shows the voltage transfer characteristic of the CE circuit of Fig. 5.26(a). To understand how this characteristic arises, we first express  $v_o$  as

$$v_o = v_{CE} = V_{CC} - R_C i_C \quad (5.50)$$

Next, we observe that since  $v_{BE} = v_i$ , the transistor will be effectively cutoff for  $v_i < 0.5$  V or so. Thus, for the range  $0 < v_i < 0.5$  V,  $i_C$  will be negligibly small, and  $v_o$  will be equal to the supply voltage  $V_{CC}$  (segment XY of the transfer curve).


As  $v_i$  is increased above 0.5 V, the transistor begins to conduct, and  $i_C$  increases. From Eq. (5.50), we see that  $v_o$  decreases. However, since initially  $v_o$  will be large, the BJT will be operating in the active mode, which gives rise to the sharply descending segment YZ of the voltage transfer curve. The equation for this segment can be obtained by substituting in Eq. (5.50) the active-mode expression for  $i_C$ , namely,

$$\begin{aligned} i_C &\cong I_S e^{v_{BE}/V_T} \\ &= I_S e^{v_i/V_T} \end{aligned}$$

where we have, for simplicity, neglected the Early effect. Thus we obtain

$$v_o = V_{CC} - R_C I_S e^{v_i/V_T} \quad (5.51)$$

We observe that the exponential term in this equation gives rise to the steep slope of the YZ segment of the transfer curve. Active-mode operation ends when the collector voltage ( $v_o$  or  $v_{CE}$ ) falls by 0.4 V or so below that of the base ( $v_i$  or  $v_{BE}$ ). At this point, the BJT turns on, and the transistor enters the saturation region. This is indicated by point Z on the transfer curve.

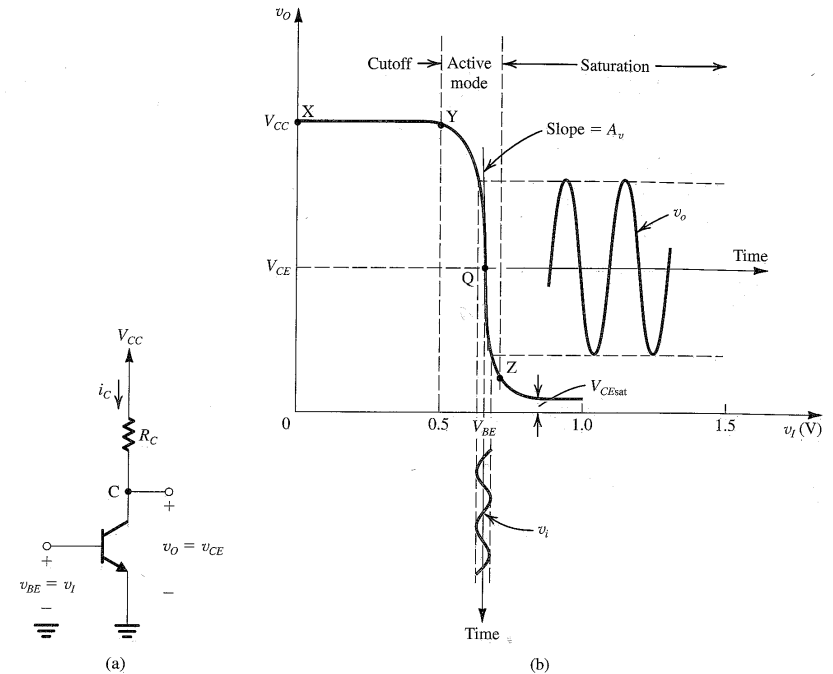

**FIGURE 5.26** (a) Basic common-emitter amplifier circuit. (b) Transfer characteristic of the circuit in (a). The amplifier is biased at a point Q, and a small voltage signal  $v_i$  is superimposed on the dc bias voltage  $V_{BE}$ . The resulting output signal  $v_o$  appears superimposed on the dc collector voltage  $V_{CE}$ . The amplitude of  $v_o$  is larger than that of  $v_i$  by the voltage gain  $A_v$ .

Observe that a further increase in  $v_{BE}$  causes  $v_{CE}$  to decrease only slightly: In the saturation region,  $v_{CE} = V_{CEsat}$ , which falls in the narrow range of 0.1 V to 0.2 V. It is the almost-constant  $V_{CEsat}$  that gives this region of BJT operation the name *saturation*. The collector current will also remain nearly constant at the value  $I_{Csat}$ .

$$I_{Csat} = \frac{V_{CC} - V_{CEsat}}{R_C} \quad (5.52)$$

We recall from our study of the saturation region of operation in the previous section that the saturated BJT exhibits a very small resistance  $R_{CEsat}$  between its collector and emitter. Thus, when saturated, the transistor in Fig. 5.26 provides a low-resistance path between the collector node C and ground and hence can be thought of as a closed switch. On the other hand, when the BJT is cut off, it conducts negligibly small (ideally zero)