

EE 321 Analog Electronics, Fall 2012  
Exam 1 October 1, 2012  
Solution

This is a closed-book exam. Calculators allowed. The exam is designed for conceptual understanding not long derivations. You MUST box your answer. Correct answer boxed and derivation gives you 10 points. Either is 5 points. Neither is 0 points.

You have a source,  $v_S$  with output resistance  $R_S = 1 \text{ k}\Omega$ , amplifier A with gain  $A_{voA} = 10$ ,  $R_{inA} = 1 \text{ k}\Omega$ , and  $R_{outA} = 10 \text{ k}\Omega$ , amplifier B with gain  $A_{voB} = 10$ ,  $R_{inB} = 10 \text{ k}\Omega$ , and  $R_{outB} = 1 \text{ k}\Omega$ , and a load  $R_L = 1 \text{ k}\Omega$ . Which arrangement, source-A-B-load, or source-B-A-load will result in the largest overall  $G_v$ , and what is that value?

1. Compute  $G_v$  for the source-A-B-load sequence.

$$\begin{aligned} G_v &= \frac{R_{inA}}{R_{inA} + R_S} \times A_{voA} \times \frac{R_{inB}}{R_{outA} + R_{inB}} \times A_{voB} \times \frac{R_L}{R_L + R_{outB}} \\ &= \frac{1}{1+1} \times 10 \times \frac{10}{10+10} \times 10 \times \frac{1}{1+1} \\ &= 12.5 \end{aligned}$$

2. Compute  $G_v$  for the source-B-A-load sequence and indicate which of the two sequences produces the greater  $G_v$ .

$$\begin{aligned} G_v &= \frac{10}{10+1} \times 10 \times \frac{1}{1+1} \times 10 \times \frac{1}{1+10} \\ &= 4.13 \end{aligned}$$

Thus, SABL configuration creates the larger gain.

We model an op-amp open-loop gain in the usual way as a LP circuit with  $A_0 = 10^6$  and  $f_0 = 10 \text{ Hz}$ .

3. What is the bandwidth of an amplifier, built with this op-amp, which has a gain of  $10^3$ ?

$$\text{GBWP} = 10 \times 10^6 = 10^7. \text{ BW} = \frac{\text{GBWP}}{G} = \frac{10^7}{10^3} = 10^4 \text{ Hz.}$$

4. If you cascade two amplifiers to get a total gain of  $10^3$ , what is the bandwidth?

$$\text{BW} = \frac{\text{GBWP}}{\sqrt{G}} = \frac{10^7}{\sqrt{10^3}} = 3.2 \times 10^5 \text{ Hz.}$$

An op-amp has  $V_{OS} = 1 \text{ mV}$  and  $I_B = 1 \mu\text{A}$ . You use it to build an inverting amplifier with input resistance  $1 \text{ k}\Omega$ .

5. If the gain is  $-100$  how big (absolute value) can the output get for zero input?

The effect of  $V_{OS}$  is

$$V_o = (|G| + 1) V_{OS} = 101 \times 10^{-3} = 101 \text{ mV}$$

The effect of  $I_B$  is

$$V_o = -I_B R_2 = I_B G R_1 = -100 \times 10^{-6} \times 10^3 = -100 \text{ mV}$$

Total effect is (absolute)  $V_o = 201 \text{ mV}$ .

6. What value of the gain will produce a maximum (again absolute) output of  $1 \text{ V}$ ?


Write (in absolute terms)

$$V_o = I_B |G| R_1 + (|G| + 1) V_{OS}$$

$$|G| = \frac{V_o - V_{OS}}{I_B R_1 + V_{OS}} = \frac{1 - 10^{-3}}{10^{-6} \times 10^3 + 10^{-3}} = 500$$

so  $G = -500$  is the largest we can allow.

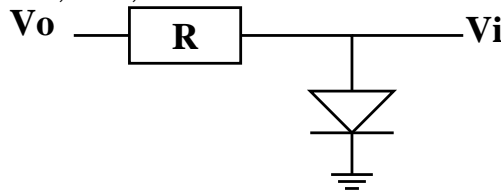Consider this diode circuit with  $R = 10 \Omega$ . Compute the value of  $V_o$  for three different values of  $V_i$ ,  $-2 \text{ V}$ ,  $1 \text{ V}$ , and  $3 \text{ V}$  in the two cases below.



7. When modeling the diode as a fixed voltage drop,  $V_D = 0.7 \text{ V}$ .

In this case output equals  $V_D$  when  $V_i \geq V_D$ . So the answers are  $-2 \text{ V}$ ,  $0.7 \text{ V}$ , and  $0.7 \text{ V}$ .

8. When modeling the diode as a piecewise linear model with  $V_{D0} = 0.65 \text{ V}$ , and  $r_D = 5 \Omega$ .

in this case the output equals

$$V_o = \begin{cases} 0 & V_i < V_{D0} \\ V_{D0} + \frac{V_i - V_{D0}}{3} & V_i > V_{D0} \end{cases}$$

So we get for the three cases  $-2 \text{ V}$ ,  $0.77 \text{ V}$ , and  $1.43 \text{ V}$ .