


EE 321 Analog Electronics, Fall 2011 Exam 1 October 3, 2011

Rules: This is a closed-book exam. You may use only your brain, a calculator and pen/paper. Each numbered question counts equally toward your grade.

Note: The questions are designed to test your conceptual understanding. Thus, except for question 2, which requires some derivation, the solutions to all the problems are literally 1- or 2-line calculations. If you get stuck on long calculations you are doing something wrong.

Diode circuits

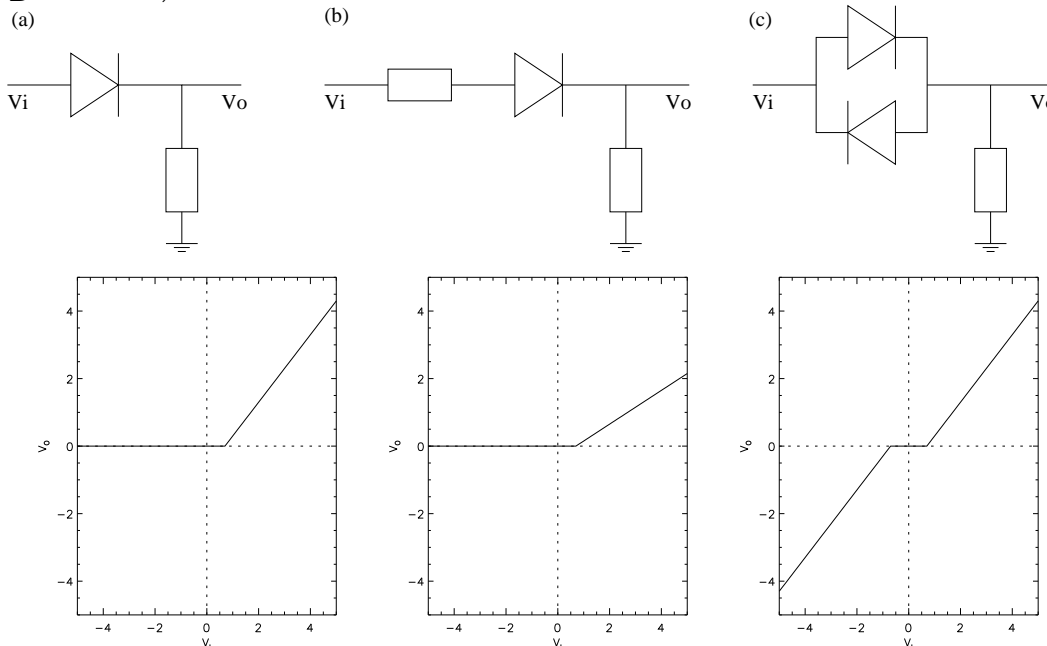1. Carefully plot the output as a function of the input for $-5\text{ V} < V_{\text{in}} < 5\text{ V}$ for the following circuits. By “carefully” is meant that voltage pairs can be read off your plot. Assume the fixed voltage drop diode model with $V_D = 0.7\text{ V}$, and that the resistors are identical.



Finite open-loop gain

2. Show that the expression for the closed-loop gain of a non-inverting amplifier with finite open-loop gain is

$$v_o = \frac{Av_i}{1 + \frac{A}{\frac{R_2}{R_1} + 1}}$$

Show that it reduces to the well-known expression for a ideal op-amp

Begin with

$$v_o = A(v_i - v_-) \qquad R_2 I = v_o - v_- \qquad R_1 I = v_-$$

Next we eliminate v_- and I between these equations. First eliminate I between the last two equations to get

$$\frac{v_o - v_-}{R_2} = \frac{v_-}{R_1}$$

Isolate v_-

$$\frac{v_o}{R_2} = v_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$v_o = v_- \left(\frac{R_2}{R_1} + 1 \right)$$

$$v_- = \frac{v_o}{\frac{R_2}{R_1} + 1}$$

Next insert this into the first equation

$$v_o = A \left(v_i - \frac{v_o}{\frac{R_2}{R_1} + 1} \right)$$

$$v_o \left(1 + \frac{A}{\frac{R_2}{R_1} + 1} \right) = Av_i$$

$$\frac{v_o}{v_i} = \frac{A}{1 + \frac{A}{\frac{R_2}{R_1} + 1}} = \left(\frac{R_2}{R_1} + 1 \right) \frac{1}{\frac{1}{A} \left(\frac{R_2}{R_1} + 1 \right) + 1}$$

If we let $A \rightarrow \infty$ then the fraction factor goes to unity.

3. If A is a low-pass filter with $\omega_0 = 10 \text{ s}^{-1}$, and $A_0 = 10^5$, what is the gain-bandwidth product, in Hz? And then what is the bandwidth of an amplifier design with a gain of 10^3 , again in Hz?

$$\text{GBWP} = \omega_0 A_0 = 10 \times 10^5 = 10^6 \text{ s}^{-1} = \frac{10^6}{2\pi} \text{ Hz} = 159 \text{ kHz}$$

$$\text{BW} = \frac{\text{GBWP}}{G} = \frac{159 \times 10^3}{10^3} = 159 \text{ Hz}$$

Offset and bias current

An op-amp has $V_{OS} = 1 \text{ mV}$, $I_B = 1 \mu\text{A}$, and $I_{OS} = 100 \text{ nA}$.

4. For an inverting amplifier, what is the largest value of the feedback resistor allowed to keep the output below 10 mV (consider only the bias current).

$$R_{2,\max} I_B = 10 \text{ mV}$$

$$R_{2,\max} = \frac{10 \text{ mV}}{I_B} = \frac{10 \times 10^{-3}}{1 \times 10^{-6}} = 10 \text{ k}\Omega$$

5. Using the maximum value for the feedback, what value of the input resistor will produce a gain (A_{vo}) of -10 . What is the size of the output due to V_{OS} ?

$$A_{vo} = -\frac{R_2}{R_1}$$

$$R_1 = -\frac{R_2}{A_{vo}} = -\frac{10^3}{-10} = 1 \text{ k}\Omega$$

The output due to V_{OS} is simply V_{OS} amplified by the non-inverting gain, so

$$v_O(V_{OS}) = 1 \times 11 = 11 \text{ mV}$$

6. What would be G_{vo} if attaching a source with output resistance $R_S = 100 \text{ k}\Omega$, and what is a simple way to restore the original gain of -10 ?

The gain would be

$$G_{vo} = A_{vo} \frac{R_1}{R_1 + R_S} = -10 \times \frac{10^3}{100 \times 10^3} = -0.1$$

A simple way to restore the gain is to place a buffer/follower between the source and R_1 .

Zener diode regulator

Assume a piecewise linear model for a Zener diode, with $V_{Z0} = 5.6 \text{ V}$ and $r_Z = 5 \Omega$.

7. Using a 10 V supply, design a regulator (choose resistor value in series with Zener), which outputs exactly V_{Z0} to a load resistor $R_L = 100 \Omega$.

This requires voltage division like this:

$$V \frac{R_L}{R + R_L} = V_{Z0}$$

$$R = \frac{V}{V_{Z0}} R_L - R_L = 100 \times \left(\frac{10}{5.6} - 1 \right) = 78.6 \Omega$$

8. By how much does the output voltage change if we change to $R_L = 200 \Omega$? In setting up the problem you should simplify the problem by assuming that V_Z is essentially unchanged, otherwise you will run out of time mired in longer calculations. You will need to obtain the change in current through the Zener diode

The quick approximation is that the output voltage changes very little, so that the new R_L carries half the current. The rest is carried through the Zener, and that current has a small voltage increase associated with it,

$$\Delta V = I r_Z = \frac{1}{2} \frac{V_{Z0}}{R_L} r_z = \frac{1}{2} \frac{5.6}{100} \times 5 = 0.14 \text{ V}$$

9. When no load is attached, what is the change in output voltage for each volt change in the supply voltage?

The voltage above V_{Z0} is voltage divided between r_z and R , and thus

$$v_O = V_{Z0} + (v_I - v_{Z0}) \frac{r_z}{r_z + R}$$

and then

$$\frac{dv_O}{dv_I} = \frac{r_z}{r_z + R} = \frac{5}{5 + 78.6} = 0.060 \frac{\text{V}}{\text{V}}$$