

# EE 321 Analog Electronics, Fall 2010


## Exam 1 September 27, 2010

**Rules:** This is a closed-book exam. You may only use what you can remember and/or derive. The exam will last 50 minutes. Each problem counts equally toward your grade. None of the problems require long calculations.

### Amplifier cascade

Consider four components: A voltage source with output resistance  $1\text{ k}\Omega$ , a transconductance amplifier with input resistance  $1\text{ k}\Omega$ , gain  $G_1 = 10\text{ A/V}$ , and output resistance  $100\ \Omega$ , a voltage amplifier with input resistance  $1\text{ k}\Omega$ , gain  $A_2 = 100$ , and output resistance  $2\text{ k}\Omega$ , and a load with resistance  $100\ \Omega$ .

1. Draw each of the four components.

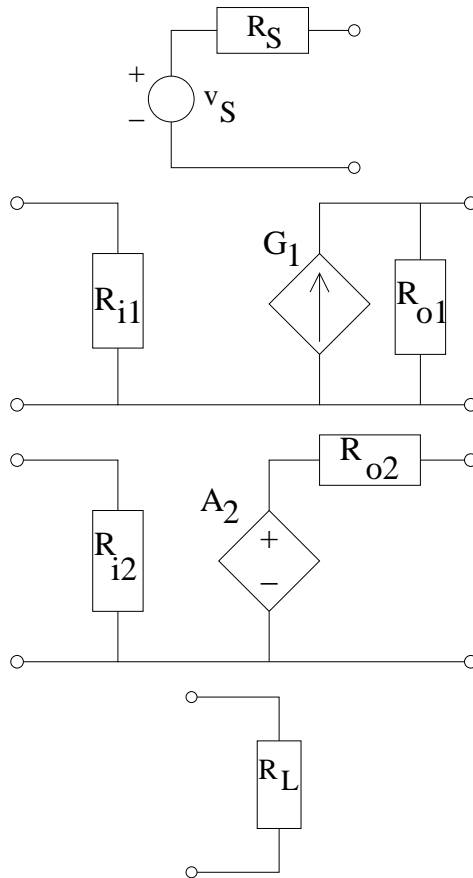

2. What is the total gain,  $v_O/v_S$  if the components are connected in the sequence in which they are described above?

We have

$$\frac{v_O}{v_S} = \frac{v_{i1}}{v_S} \frac{v_{o1}}{v_{i1}} \frac{v_{i2}}{v_{o1}} \frac{v_{o2}}{v_{i2}} \frac{v_O}{v_{o2}}$$

$$= \frac{R_{i1}}{R_{i1} + R_S} G_1 (R_{o1} || R_{i2}) A_2 \frac{R_L}{R_L + R_{o2}}$$


where each term corresponds to a fraction above, except that  $\frac{v_{i2}}{v_{o1}} = 1$  was omitted. Inserting values we get

$$\frac{v_O}{v_S} = \frac{1}{1 + 1} \times 10 \times \frac{100 \times 1000}{100 + 1000} \times 100 \times \frac{100}{100 + 2000} = 2164$$

### Summer

You can make a circuit which implements the function  $v_O = v_1 - v_2 + v_3 - v_4$  with two inverting summers (made from op-amps) in sequence. The first op-amp takes the voltages which add positively, and the second takes the output of the first and the voltages which add negatively.

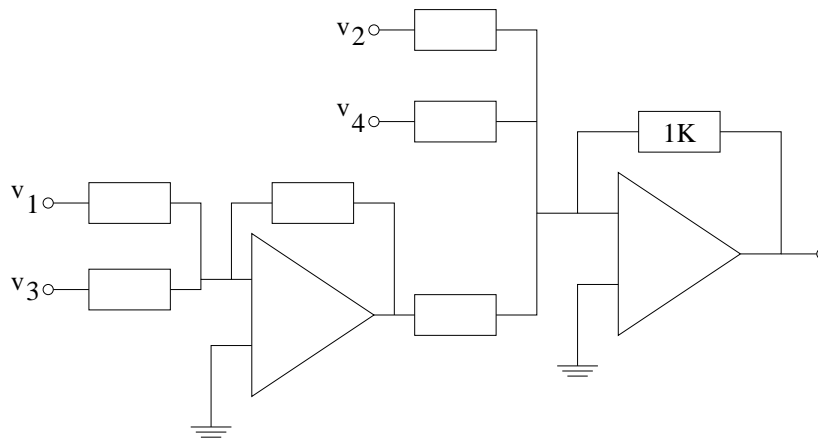3. Sketch the circuit and label the inputs and the output.




4. Determine the values of all resistors if the feedback resistor of the second op-amp is  $R_{f2} = 1\text{ k}\Omega$ .

We can assign all other resistors to  $1\text{ k}\Omega$  as well to obtain the correct gains.

### Finite open-loop gain

Consider a non-ideal op-amp which has open-loop gain  $A_{vo} = 100$ .

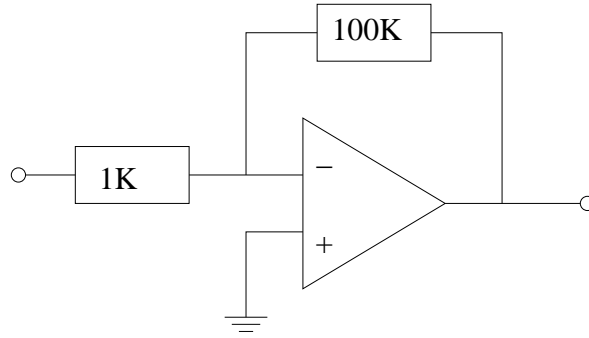5. Design an inverting circuit with input resistance  $1\text{ k}\Omega$  and feedback resistance equal to what you would choose for a gain of  $-100$  when using an ideal op-amp.



6. Compute the actual gain. Hint:  $v_- = \frac{v_o R_1 + v_s R_2}{R_1 + R_2}$

We have  $v_O = -Av_-$ , which we can use to eliminate  $v_-$  in the given equation,

$$-\frac{v_O}{A} = \frac{v_o R_1 + v_s R_2}{R_1 + R_2}$$

Next we isolate  $v_O$ ,

$$v_O \left( \frac{1}{A} + \frac{R_1}{R_1 + R_2} \right) = -\frac{v_s R_2}{R_1 + R_2}$$

$$\frac{v_O}{v_S} = -\frac{\frac{R_2}{R_1 + R_2}}{\frac{1}{A} + \frac{R_1}{R_1 + R_2}}$$


Inserting the known values,  $A = 100$ ,  $R_1 = 1 \text{ k}\Omega$ , and  $R_2 = 100 \text{ k}\Omega$ , we get

$$\frac{v_O}{v_S} = -\frac{\frac{100}{1+100}}{\frac{1}{100} + \frac{1}{1+100}} = 49.8$$

### Offset voltage and bias current

Consider a non-ideal op-amp with  $V_{OS} = 3 \text{ mV}$ ,  $I_B = 100 \text{ nA}$ .

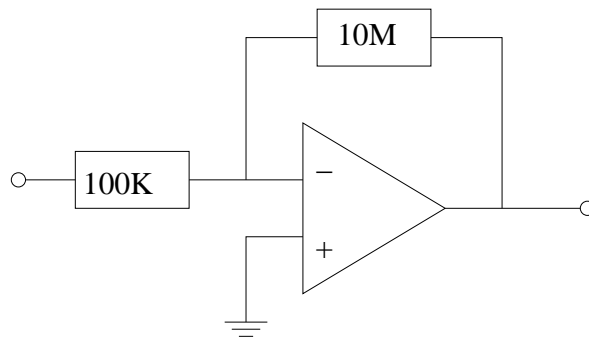7. Using this op-amp design an amplifier with input resistance of  $100 \text{ k}\Omega$  and gain of  $-100$ .



8. Derive the expression for the output offset and compute a value assuming that  $V_{OS}$  and  $I_B$  are both positive.

Actually it is slightly unclear what is meant with “both positive,” so several different answers are acceptable. We can use superposition.  $V_{OS}$  is amplified by the non-inverting gain, 101, and  $I_B$  results in an output voltage  $I_B R_2$ , so the total output is

$$v_O = V_{OS} \left( 1 + \frac{R_2}{R_1} \right) + I_B R_2$$

Inserting known values we get

$$\begin{aligned} v_O &= 3 \times 10^{-3} \times 101 + 100 \times 10^{-9} \times 10 \times 10^6 \\ &= 1.3 \text{ V} \end{aligned}$$