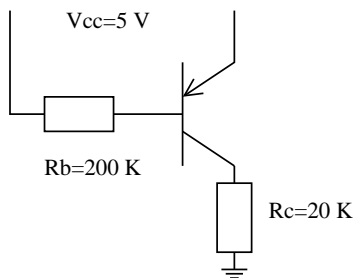


**EE 321 Analog Electronics, Fall 2012**  
**Exam 2 October 31, 2012**  
**solution**

This is a closed-book exam. Calculators allowed. The exam is designed for conceptual understanding not long derivations. You **MUST** box your answer. When there are multiples values in an answer summarize them in a single box. Correct answer boxed and derivation gives you 10 points. Either is 5 points. Neither is 0 points.


1. Find all the voltages and currents in this circuit. (Careful!)



This transistor is in cutoff mode. Thus

$$i_C = i_E = i_B = 0 \text{ and } v_B = v_E = 5 \text{ V and } v_C = 0 \text{ V.}$$

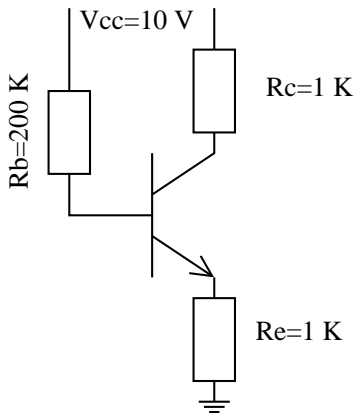2. Assuming  $\beta = 50$  find all the voltages and currents in this circuit



Begin with assuming active mode

$$i_B R_B + V_{BE} + (\beta + 1) i_B R_E = V_{CC}$$

$$i_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} = \frac{10 - 0.7}{200 + 51 \times 1} = 37.1 \mu\text{A}$$

$$v_B = V_{CC} - i_B R_B = 10 - 0.2 \times 37.1 = 2.58 \text{ V}$$

$$i_C = \beta i_B = 50 \times 37.1 \times 10^{-3} = 1.86 \text{ mA}$$

$$v_C = V_{CC} - i_C R_C = 10 - 1.86 \times 1 = 8.15 \text{ V}$$

Since  $v_C > v_B - 0.4 \text{ V}$  active mode is confirmed.

$$i_E = (\beta + 1) i_B = 51 \times 37.1 \times 10^{-3} = 1.89 \text{ mA}$$

$$v_E = i_E R_E = 1.89 \times 1 = 1.89 \text{ V}$$

$i_B = 37.1 \mu\text{A}, i_C = 1.86 \text{ mA}, i_E = 1.89 \text{ mA}, v_B = 2.58 \text{ V}, v_C = 8.15 \text{ V}, v_E = 1.89 \text{ V}$
--

3. For the same circuit estimate  $A_{vo}$  using the quick approximation when it is used as a common-emitter amplifier with emitter resistance (you may assume inputs and outputs are capacitively coupled as in the text book).

$$A_{vo} = -\frac{R_C}{R_E} = -1$$

$A_{vo} = -1$
---------------

4. Design a NPN common-emitter amplifier operating between  $V_{CC} = 10\text{ V}$  supply and ground following these steps in order (again you may assume capacitive coupling of input and outputs for simplicity).

- (a) What should  $V_C$  be to get  $A_{vo} = -200$ ?

$$A_{vo} = -\frac{I_C R_C}{V_T} = -\frac{V_{CC} - V_C}{V_T}$$

$$V_C = V_{CC} + V_T A_{vo} = 10 - 25 \times 10^{-3} \times 200 = 5\text{ V}$$

$$\boxed{V_C = 5\text{ V}}$$

- (b) What is  $I_C$  if the output resistance should be  $5\text{ k}\Omega$ ?

$$R_C = R_{\text{out}}, \text{ and } A_{vo} = -\frac{R_C I_C}{V_T}, \text{ so}$$

$$I_C = -\frac{A_{vo} V_T}{R_C} = \frac{200 \times 25 \times 10^{-3}}{5 \times 10^3} = 1\text{ mA}$$

$$\boxed{I_C = 1\text{ mA}}$$

- (c) If the base is biased with a resistor,  $R_B$ , to  $V_{CC}$ , what should be the value of  $R_B$ ? Assume  $\beta = 100$ .

$$I_B = \frac{I_C}{\beta} = \frac{1}{100} = 10\text{ }\mu\text{A}$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{10 - 0.7}{10 \times 10^{-3}} = 930 \text{ k}\Omega$$



$$\boxed{R_B = 930 \text{ k}\Omega}$$

(d) What is the input resistance of this amplifier?

$$\begin{aligned} R_{\text{in}} &= R_B \parallel r_{\pi} = R_B \parallel \frac{\beta}{g_m} = R_B \parallel \frac{\beta V_T}{I_C} \\ &= 930 \times 10^3 \parallel \frac{100 \times 25 \times 10^{-3}}{1 \times 10^{-3}} \\ &= 930 \parallel 2.5 = 2.49 \text{ k}\Omega \end{aligned}$$

$$\boxed{R_{\text{in}} = 2.49 \text{ k}\Omega}$$

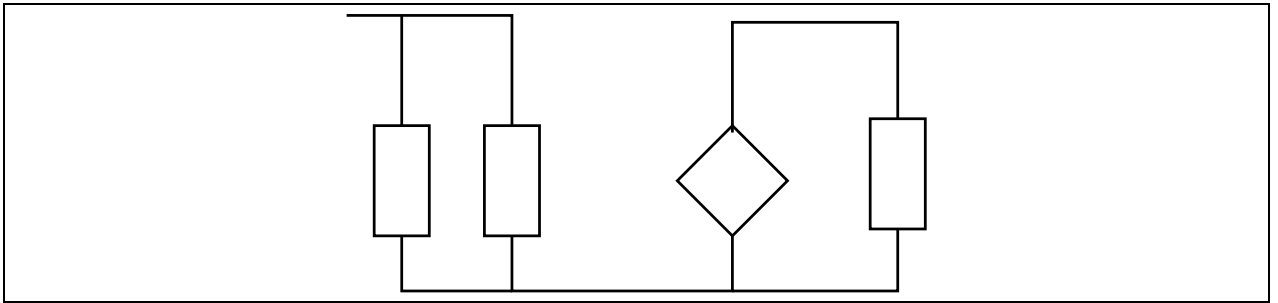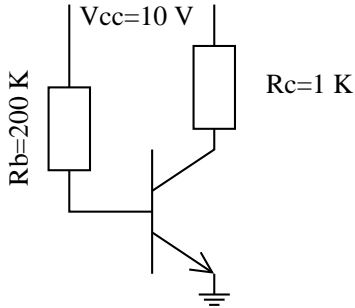5. Draw the small-signal  $\pi$ -model circuit for this amplifier, give  $r_\pi$  and  $g_m$ ,  $R_{in}$ , and  $R_{out}$ ,  $A_{vo}$ , and  $G_v$  if a source has output resistance  $R_S = 10\text{ k}\Omega$  and a  $1\text{ k}\Omega$  load is attached (yet again assume capacitive coupling of inputs and outputs).



Assume  $\beta = 100$ , and we get

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{10 - 0.7}{200} = 46.5\ \mu\text{A}$$

$$I_C = \beta I_B = 4.65\ \text{mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{4.65}{25} = 0.19\ \Omega^{-1}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{0.19} = 530\ \Omega$$

$$R_{in} = r_\pi || R_B = r_\pi$$

$$R_{out} = R_C = 1\ \text{k}\Omega$$

$$A_{vo} = -\frac{I_C R_C}{V_T} = -\frac{4.65 \times 1}{25 \times 10^{-3}} = -186$$

$$\begin{aligned} G_v &= \frac{R_{\text{in}}}{R_S + R_{\text{in}}} A_{vo} \frac{R_L}{R_{\text{out}} + R_L} \\ &= - \frac{530}{10 \times 10^3 + 530} \times 186 \times \frac{1}{1 + 1} \\ &= -4.68 \end{aligned}$$

$r_{\pi} = 538 \Omega, g_m = 0.19 \Omega^{-1}, R_{\text{in}} = 530 \Omega, R_{\text{out}} = 1 \text{ k}\Omega, A_{vo} = -186, G_v = -4.68$
--