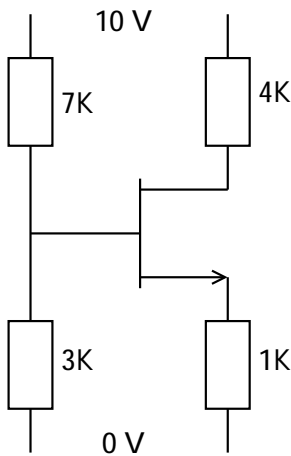


EE 321 Analog Electronics, Fall 2012
Exam 3 November 30, 2012
solution

This is a closed-book exam. Calculators allowed. The exam is designed for conceptual understanding not long derivations. You MUST box your answer. When there are multiples values in an answer summarize them in a single box. Correct answer boxed and derivation gives you 10 points. Either is 5 points. Neither is 0 points.

1. Find i_D , v_D , v_S , and v_G for this circuit, with $V_t = 1\text{ V}$, and $k'_n \frac{W}{L} = 1\text{ mA/V}^2$



$v_G = 3\text{ V}$. GUESS SATURATION.

$$i_D = \frac{1}{2} (v_G - V_t)^2 = \frac{1}{2} (v_G - V_t - i_D R_S)^2$$

$$2i_D = (v_G - V_t)^2 + i_D^2 R_S^2 - 2i_D R_S (v_G - V_t)$$

$$2i_D = 4 + i_D^2 - 4i_D$$

$$i_D = \frac{6 \pm \sqrt{20}}{2} = 0.76 \text{ OR } 5.2\text{ mA}$$

MUST BE FIRST. THEN


$$v_S = 0.76\text{ V} \quad v_G = 3\text{ V} \quad v_D = 6.94\text{ V} \quad i_D = 0.76\text{ mA}$$

2. Replace the $4\text{ k}\Omega$ with a $10\text{ k}\Omega$ and find the same quantities.

GUESS SATURATION MODE. THEN i_D IS THE SAME, AND $v_D = V_{DD} - i_D R_D = 10 - 0.76 \cdot 10 = 2.4\text{ V}$. v_G IS ALSO THE SAME, SO WE FIND THAT $v_{DS} > v_{GS} - V_t$ WHICH VERIFIES SATURATION MODE.

$$v_S = 0.76\text{ V} \quad v_G = 3\text{ V} \quad v_D = 2.4\text{ V} \quad i_D = 0.76\text{ mA}$$

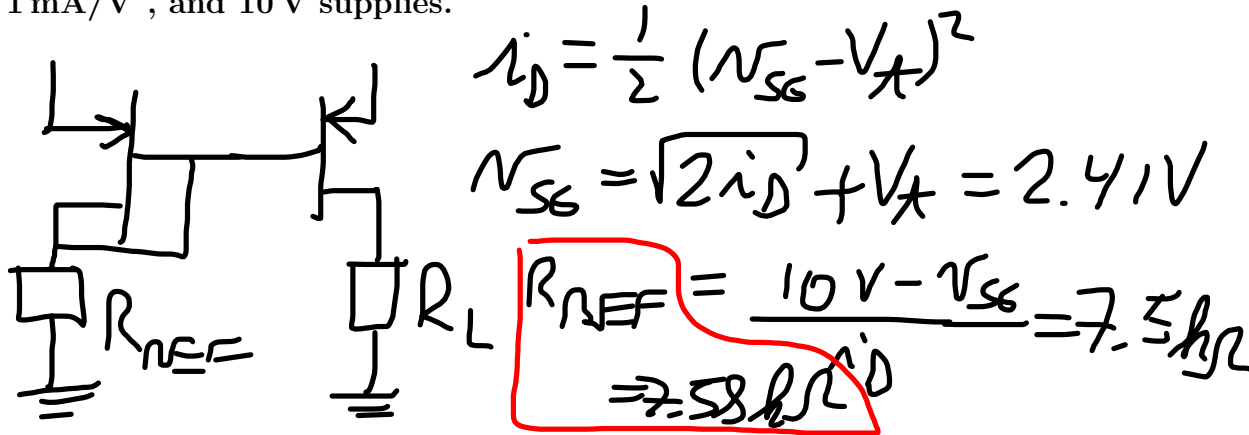3. Make a MOSFET current mirror which provides 1 mA to a load connected between ground and the current mirror output. Assume $V_t = 1\text{ V}$, and $k'_p \frac{W}{L} = 1\text{ mA/V}^2$, and 10 V supplies.




4. For the current mirror in the previous circuit what is the largest value of the load resistor that will maintain saturation mode operation of the MOSFETs?

MAX VOLTAGE IS $10\text{ V} - (V_{SG} - V_t) = 10\text{ V} - 1.41\text{ V} = 8.59\text{ V}$

MAX RESISTANCE

$$R_{L\text{MAX}} = 8.59\text{ k}\Omega$$

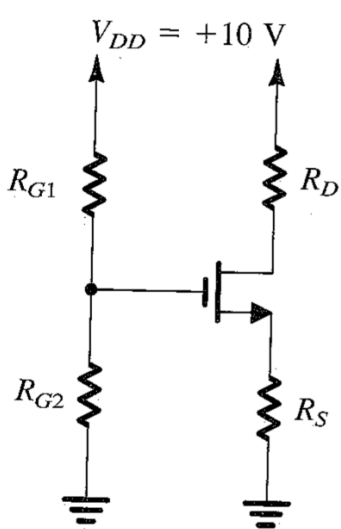5. Pick resistors in this circuit such that a CS amplifier is implemented (not a CS with R_S) which has (a) output biased at 5 V, (b) $A_{vo} = -10$, (c) smallest gate resistor of 1 M Ω . Assume $k'_n \frac{W}{L} = 1 \frac{\text{mA}}{\text{V}^2}$ and $V_t = 1\text{ V}$.



$$R_S = 0 \quad A_{vo} = -\frac{2I_D R_D}{V_{GS} - V_t}$$

$$I_D R_D = 5\text{ V} \Rightarrow V_{GS} = -\frac{2I_D R_D}{A_{vo}} + V_t = \frac{10}{-10} + 1$$

$$= 2\text{ V}$$

$$\Rightarrow R_{G2} = 1\text{ M}\Omega, R_{G1} = 5\text{ M}\Omega$$

$$I_D = \frac{1}{2} (V_{GS} - V_t)^2$$

$$= 0.5\text{ mA}$$

$$\Rightarrow R_D = 10\text{ k}\Omega$$


$$R_S = 0$$

$$R_D = 10\text{ k}\Omega$$

$$R_{G1} = 5\text{ M}\Omega$$

$$R_{G2} = 1\text{ M}\Omega$$

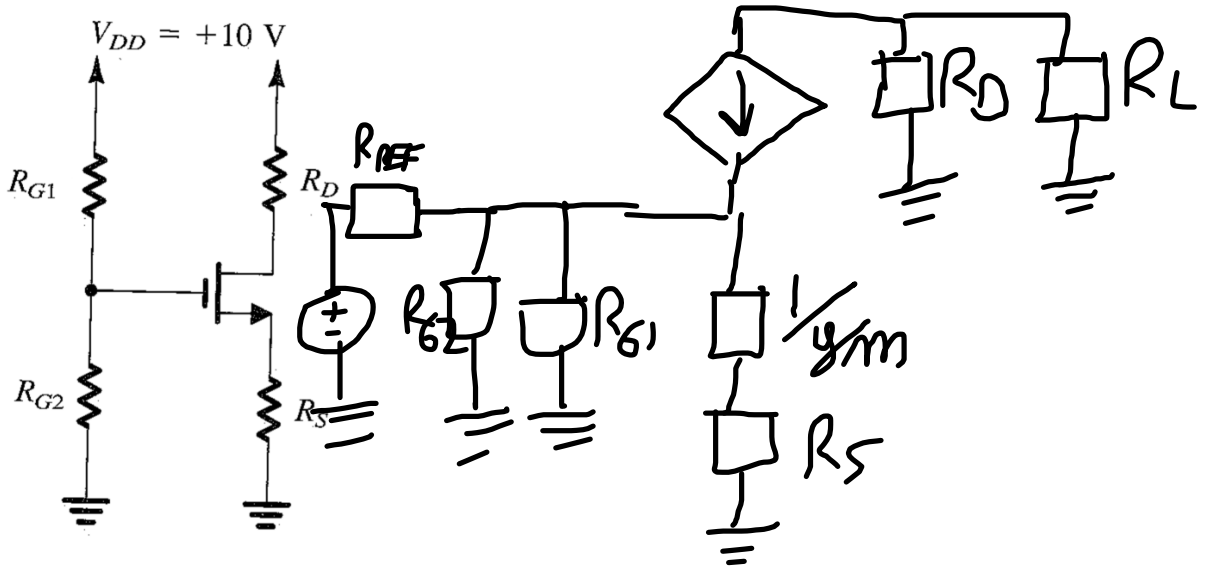6. Draw the small-signal model for this amplifier, adding also a source (with R_{src}) and a load (R_L).



7. If $R_{G1} = 200 \text{ k}\Omega$, $R_{G2} = 800 \text{ k}\Omega$, $R_S = 1 \text{ k}\Omega$, $R_D = 5 \text{ k}\Omega$, $V_t = 1 \text{ V}$, $k'_n \frac{W}{L} = 1 \text{ mA/V}^2$, $R_{src} = 100 \text{ k}\Omega$, and $R_L = 3 \text{ k}\Omega$, what are A_{vo} , A_v , G_v , R_{in} , and R_{out} ?

$$I_D = \frac{1}{2} (V_G - V_t - I_D R_S)^2$$

$$2I_D = (V_G - V_t)^2 + I_D^2 R_S^2 - 2I_D R_S (V_G - V_t)$$

$$2I_D = 1 + I_D^2 - 2I_D$$

$$I_D^2 - 4I_D + 1 = 0 \quad I_D = \frac{4 \pm \sqrt{16 - 4}}{2}$$

$$g_m = \frac{2I_D}{V_{GS} - V_t}$$

$$= \frac{2 \cdot 0.27}{1}$$

$$= 0.54 \cdot 10^{-3} \text{ A/V}$$

$$= 0.27 \text{ mA} \text{ or } 3.73 \text{ mA}$$

$$A_{no} = -2.7$$

$$A_{vr} = -1.0$$

$$G_{no} = -1.66$$

$$G_{vr} = -0.62$$

$$A_{no} = -g_m R_D = -2.7$$

$$A_{vr} = -g_m (R_D \parallel R_L) = -1.0$$

$$G_{vr} = \frac{R_{G1} \parallel R_{G2} A_{vr}}{R_{src} + R_{G1} \parallel R_{G2}} = \frac{160 (-1.0)}{100 + 160} = -0.62$$

$$G_{no} = \frac{R_{G1} \parallel R_{G2}}{R_{src} + R_{G1} \parallel R_{G2}} = -1.66$$

$$R_{in} = R_{G1} \parallel R_{G2} = 160 \text{ k}\Omega$$

$$R_{out} = R_D = 5 \text{ k}\Omega$$

IF WE DO THE SIMPLE APPROXIMATION: $A_{no} = -\frac{R_D}{R_S} = -5$, $A_{vr} = -\frac{5 \parallel 3}{1} = -1.88$

$$A_{no} = -5 \quad G_{no} = -3.1$$

$$A_{vr} = -1.88 \quad G_{vr} = -1.16$$

$$G_{vr} = A_{no} \frac{R_{in}}{R_{in} + R_{src}} = -3.1 \quad G_{vr} = -1.16$$