


EE 321 Analog Electronics, Fall 2011
Exam 3 November 30, 2011
Solution

Rules: This is a closed-book exam. You may use only your brain, a calculator and pen/paper. Each numbered question counts equally toward your grade.

Note: The questions are designed to test your conceptual understanding, not your ability to do many pages of math. If you find yourself doing long calculations there is a high probability that you are doing something wrong.

DC analysis

 1. Find all the voltages and currents in this circuit. Assume $\beta = 100$, $V_t = 1$ V, and $k'_n \frac{W}{L} = 1$ mA/V².



For the first circuit we see that it is in cutoff mode, so no current is flowing, thus $I_B = I_C = I_E = 0$, and then the voltages are $V_B = V_C = V = 10$ V, and $V_E = 0$ V.

For the second circuit it is on, and must be in active mode. We can write

$$V = I_B R_B + V_{BE} + (\beta + 1) I_B R_E$$

or

$$I_B = \frac{V - V_{BE}}{R_B + (\beta + 1) R_E} = \frac{10 - 0.7}{100 + 101} = 46.3 \mu\text{A}$$

Then

$$I_C = \beta I_B = 100 \times 46.3 = 4.63 \text{ mA}$$

and

$$I_E = (\beta + 1) I_B = 101 \times 46.3 = 4.67 \text{ mA}$$

The voltages are

$$V_B = V - I_B R_B = 10 - 49.8 \times 10^{-6} \times 100 \times 10^5 = 5.37 \text{ V}$$

$$V_C = V = 10 \text{ V}$$

$$V_E = I_E R_E = 4.67 \times 1 = 4.67 \text{ V}$$

The third circuit is a NMOS. We have immediately $V_{GS} = 3 \text{ V}$ as a voltage division of 10 V , and $V_S = 0 \text{ V}$. Also $I_G = 0$ of course. Let's assume saturation mode. In that case we have


$$I_D = \frac{k'_n W}{2 L} (V_{GS} - V_t)^2 = \frac{1}{2} (3 - 1)^2 = 2 \text{ mA}$$

and

$$V_D = V - I_D R_D = 10 - 2 = 8 \text{ V}$$

which is consistent with the saturation mode assumption.

Amplifier analysis

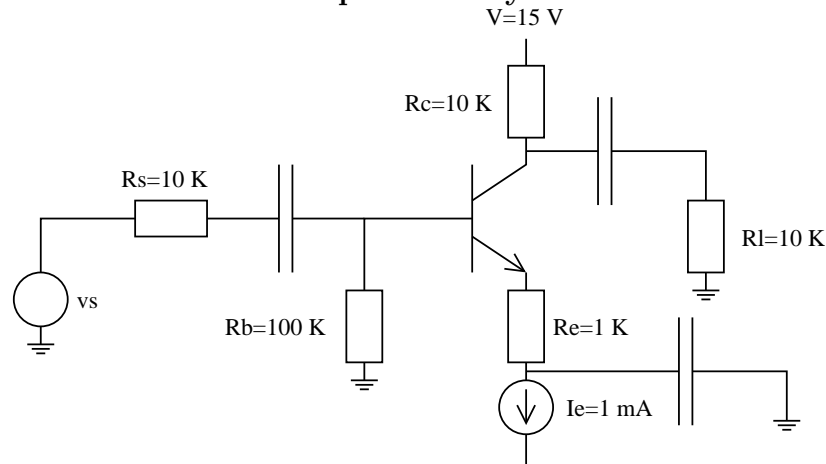

assume $\beta = 100$

2. Explain why this circuit has $A_{vo} \approx -10$ and $V_C \approx 5 \text{ V}$ (you may assume these values in the following questions).

The gain is approximately the collector resistance divided by the emitter resistance. Ignoring r_e we get a gain of 10. The bias current is 1 mA , and $V_C = V_{CC} - I_C R_C = 10 - 1 \times 10 = 5 \text{ V}$.

3. What is the smallest signal output permitted while the BJT remains in the active mode? (careful, the base is not at ground)

The edge of active mode corresponds to $V_{CB} = -0.4\text{ V}$. The base voltage is $V_B = -I_B R_B = \frac{I_E}{\beta+1} R_B = -\frac{1}{101} \times 100 = -0.99\text{ V}$. Thus the smallest allowed $v_C = -0.99 - 0.4 = -1.34$, and the smallest signal, $v_c = -1.34 - 5 = -6.34\text{ V}$.

4. Draw the small-signal model for the circuit.

5. What is R_{in} , and what is G_v ?

R_{in} is the parallel combination of R_B and $(\beta + 1)r_e + R_E$. First get

$$r_e = \frac{V_T}{I} = \frac{25}{1} = 25\ \Omega$$

next,

$$R_{in} = R_B \parallel (\beta + 1)(r_e + R_E) = 100 \parallel 101 \times 1025 = 50.9\text{ k}\Omega$$

Next, G_v is A_{vo} with a voltage division on the output and a voltage division on the input

$$G_v = \frac{R_{in}}{R_S + R_{in}} A_{vo} \frac{R_C}{R_L + R_C} = -\frac{50.9}{10 + 50.9} \times 10 \times \frac{10}{10 + 10} = -4.18$$