## EE 321 Analog Electronics, Fall 2013 Homework #8 solution

5.110. The following table summarizes some of the basic attributes of a number of BJTs of different types, operating as amplifiers under various conditions. Provide the missing entries.

α	1.000					0.90	
β		100		00		v	
$I_{C}$ (mA)	1.00		1.00				
$I_E$ (mA)		1.00				5	
$I_{\mathcal{B}}(\mathrm{mA})$			0.020				1.10
g <sub>m</sub> (mA/V)							700
$r_{e}\left(\Omega ight)$	•			25	100		
$r_{\pi}(\Omega)$					$10.1 \ \mathrm{k\Omega}$		

(*Note:* Isn't it remarkable how much two parameters can reveal?)

I will just provide the explicit equations for the first column, (a):

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$I_E = \frac{I_C}{\alpha}$$

$$I_B = \frac{I_C}{\beta}$$

$$g_m = \frac{I_C}{V_T}$$

$$r_e = \frac{\alpha}{g_m}$$
Transistor a b c d e f g  

$$\alpha \quad 1.000 \quad 0.99 \quad 0.98 \quad 1 \quad 0.99 \quad 0.9 \quad 0.9844$$

$$\beta \quad \infty \quad 100 \quad 50 \quad \infty \quad 100 \quad 9 \quad 62.8$$

$$I_C (\text{mA}) \quad 1.00 \quad 1.00 \quad 1.02 \quad 1 \quad 0.253 \quad 5 \quad 70.2$$

$$I_B (\text{mA}) \quad 0 \quad 0.0099 \quad 0.02 \quad 0 \quad 0.0025 \quad 0.5 \quad 1.10$$

$$g_m (\text{mA/V}) \quad 40 \quad 39.6 \quad 40 \quad 40 \quad 9.9 \quad 180 \quad 700$$

$$r_e (\Omega) \quad 25 \quad 25 \quad 24.5 \quad 25 \quad 100 \quad 5 \quad 1.41$$

$$r_\pi (\Omega) \quad \infty \quad 2530 \quad 1250 \quad \infty \quad 10.1 \text{K} \quad 50 \quad 89.7$$

5.114. A biased BJT operates as a grounded-emitter amplifier between a signal source, with a source resistance of  $10 k\Omega$ , connected to the base and a  $10 k\Omega$ 

load connected as a collector resistance  $R_c$ . In the corresponding model,  $g_m$  is 40 mA/V and  $r_{\pi}$  is 2.5 k $\Omega$ . Draw the complete amplifier model using the hybrid- $\pi$  BJT equivalent circuit. Calculate the overall voltage gain  $v_c/v_s$ . What is the value of BJT  $\beta$  implied by the values of the model parameters? To what value must  $\beta$  be increased to double the overall voltage gain?



The value of  $\beta$  can be found from

$$r_{\pi} = \frac{\beta}{g_m}$$

or

$$\beta = r_{\pi}g_m = 2.5 \times 10^3 \times 0.04 = 100$$

To double the gain we would want to double the factor

$$\frac{r_{\pi}}{R_s + r_{\pi}}$$

It is currently equal to

$$\frac{2.5}{10+2.5} = 0.2$$

To double it we would need to change  $r_{\pi}$ :

$$\frac{r_{\pi}}{R_s + r_{\pi}} = 0.4$$
$$r_{\pi} = \frac{0.4}{0.6} R_s = 0.67 R_s = 6.7 \,\text{k}\Omega$$

The factor increase in  $\beta$  is the same as the factor increase in  $r_{\pi}$ :

$$\beta_{\text{new}} = \beta_{\text{old}} \frac{r_{\pi \text{ new}}}{r_{\pi} \text{ old}} = 100 \times \frac{6.7}{2.5} = 268$$

5.115. For the circuit shown in Fig. P5.115, draw a complete small-signal equivalent circuit utilizing an appropriate T model for the BJT (use  $\alpha = 0.99$ ). Your

circuit should show the values of all components, including the model parameters. What is the input resistance  $R_{\rm in}$ ? Calculate the overall gain  $v_o/v_{\rm sig}$ .



where

The overall voltage can be found from

$$v_o = -(R_C ||R_L) i_c$$
$$i_c = \alpha i_e$$
$$i_e = -\frac{v_{\text{sig}}}{R_{\text{sig}} + r_e}$$

 $\mathbf{SO}$ 

$$\frac{v_o}{v_{\text{sig}}} = (R_C || R_L) \, \alpha \frac{1}{R_{\text{sig}} + r_e}$$
$$= (10||10) \, 0.99 \frac{1}{50 + 50}$$
$$= 49.5$$

5.128. A common-emitter amplifier of the type shown in Fig 5.60(a) is biased to operate at  $I_C = 0.2 \text{ mA}$  and has a collector resistance  $R_C = 24 \text{ k}\Omega$ . The transistor has  $\beta = 100$  and a large  $V_A$ . The signal source is directly coupled to the base and  $C_{c1}$  and  $R_B$  are eliminated. Find  $R_{\text{in}}$ , the voltage gain  $A_{vo}$ , and  $R_o$ . Use these results to determine the overall voltage gain when a  $10 \text{ k}\Omega$  resistor is connected to the collector and the source resistance  $R_{\text{sig}} = 10 \text{ k}\Omega$ .





**FIGURE 5.60** (a) A common-emitter amplifier using the structure of Fig. 5.59. (b) Equivalent circuit obtained by replacing the transistor with its hybrid- $\pi$  model.

This is a common-emitter amplifier with  $R_B = \infty$ , so the input resistance is

$$R_{\rm in} = r_{\pi} = \frac{\beta V_T}{I_C} = \frac{100 \times 25}{0.2} = 12.5 \,\mathrm{k}\Omega$$
$$A_{vo} = -g_m R_C = -\frac{I_C}{V_T} R_C = -\frac{0.2}{25} 10 \times 10^3 = -80$$

$$R_O = R_C = 10 \,\mathrm{k}\Omega$$

The overall voltage gain,  $v_o/v_{\rm sig}$  is then

$$G_v = \frac{v_o}{v_{\text{sig}}} = \frac{r_\pi}{R_{\text{sig}} + r_\pi} A_{vo} \frac{R_L}{R_L + R_O}$$
$$= \frac{12.5}{10 + 12.5} (-80) \frac{10}{10 + 10}$$
$$= -22.2$$

5.130. For the common-emitter amplifier shown in Figure P5.130, let  $V_{CC} = 9 \text{ V}$ ,  $R_1 = 27 \text{ k}\Omega$ ,  $R_2 = 15 \text{ k}\Omega$ ,  $R_E = 1.2 \text{ k}\Omega$ , and  $R_C = 2.2 \text{ k}\Omega$ . The transistor has  $\beta = 100$ , and  $V_A = 100 \text{ V}$ . Calculate the dc bias current  $I_E$ . If the amplifier operates between a source for which  $R_{\text{sig}} = 10 \text{ k}\Omega$  and a load of  $2 \text{ k}\Omega$ , replace the transistor with its bybrid- $\pi$  model, and find the values of  $R_{\text{in}}$ , the voltage gain  $v_o/v_{\text{sig}}$ , and the current gain  $i_o/i_i$ .



FIGURE P5.130

We have

$$V_B = (i_1 - i_B) R_2$$
  $V_B = V_{BE} + (\beta + 1) R_E i_B$   $V_B = V_{CC} - i_1 R_1$ 

and we can eliminate  $i_D$  and  $i_B$  from the first equation.

$$V_B = \left(\frac{V_{CC} - V_B}{R_1} - \frac{V_B - V_{BE}}{(\beta + 1) R_E}\right) R_2$$
$$V_B \left[1 + \frac{R_2}{R_1} + \frac{R_2}{(\beta + 1) R_E}\right] = V_{CC} \frac{R_2}{R_1} + V_{BE} \frac{R_2}{(\beta + 1) R_E}$$
$$V_B = \frac{V_{CC} \frac{R_2}{R_1} + V_{BE} \frac{R_2}{(\beta + 1) R_E}}{1 + \frac{R_2}{R_1} + \frac{R_2}{(\beta + 1) R_E}} = \frac{9 \times \frac{15}{27} + 0.7 \times \frac{15}{101 \times 1.2}}{1 + \frac{15}{27} + \frac{15}{101 \times 1.2}} = 3.03 \text{ V}$$

Note that for  $(\beta + 1) R_E \gg R_2$  and  $V_{CC} \gg V_{BE}$  the expression for  $V_B$  reduces to the voltage divider expression,

$$V_B = V_{CC} \frac{\frac{R_2}{R_1}}{1 + \frac{R_2}{R_1}} = V_{CC} \frac{R_2}{R_1 + R_2} = 9 \times \frac{15}{15 + 27} = 3.21 \,\mathrm{V}$$

I will proceed with the result from the fully correct expression. Next, the emitter current is

$$I_E = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E} = \frac{3.03 - 0.7}{1.2} = 1.94 \,\mathrm{mA}$$

The small-signal model looks like this



The input resistance is

$$R_{\rm in} = R_1 ||R_2||r_\pi$$

where

$$r_{\pi} = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C} = \frac{\beta V_T}{\alpha I_E} = \frac{(\beta + 1) V_T}{I_E} = \frac{101 \times 25}{1.94} = 1302 \,\Omega$$

such that

$$R_{\rm in} = R_1 ||R_2||r_{\pi} = 27||15||1.302 = 1.15\,\rm k\Omega$$

The voltage gain is

$$G_{v} = -\frac{R_{\text{in}}}{R_{\text{in}} + R_{s}} A_{v} = -\frac{R_{\text{in}}}{R_{\text{in}} + R_{s}} g_{m} \left( R_{C} ||r_{o}||R_{L} \right) = -\frac{R_{\text{in}}}{R_{\text{in}} + R_{s}} \frac{\beta I_{E}}{(\beta + 1) V_{T}} \left( R_{C} ||r_{o}||R_{L} \right)$$

where

$$r_o = \frac{V_A}{I_C} = \frac{V_A}{\alpha I_E} = \frac{(\beta + 1) V_A}{\beta I_E} = \frac{101 \times 100}{100 \times 1.94 \times 10^{-3}} = 52.1 \,\mathrm{k\Omega}$$

and then

$$G_v = -\frac{R_{\rm in}}{R_{\rm in} + R_s} \frac{\beta I_E}{(\beta + 1) V_T} \left( R_C ||r_o||R_L \right)$$
  
=  $-\frac{1.14}{1.14 + 10} \frac{100 \times 1.94}{101 \times 25} \left( 2.2 ||52.1||2 \right)$   
=  $-8.07$ 

5.131. Using the topology of Fig. P5.130, design an amplifier to operate between a 10 k $\Omega$  source and a 2 k $\Omega$  load with a gain  $v_o/v_{\rm sig}$  of -8. The power supply available is 9 V. Use an emitter current of approximately 2 mA and a current of about one-tenth of that in the voltage divider that feeds the base, with the dc voltage at the base about one third of the supply. The transistor available has  $\beta = 100$  and  $V_A = 100$  V. Use standard 5% resistors (See Appendix G)

This is the same circuit as before, except choose the nearest 5% resistors. In that case choose  $R_1 = 27 \,\mathrm{k\Omega}, R_2 = 15 \,\mathrm{k\Omega}, R_E = 1.2 \,\mathrm{k\Omega}, R_C = 2.2 \,\mathrm{k\Omega}$ . Well, it turns out the problem is identical to P5.130. That was easy.