

EE 322 Advanced Analog Electronics, Spring 2008

Homework #3 Extra Problem

1. Derive an expression for I_{\min} for the step-down switching voltage regulator following the approach outlined in handout #1 (Note that handout #1 concerns the inverting switching regulator).