

EE 322 Advanced Analog Electronics, Spring 2008

Homework #9 Assignment

1. Horowitz & Hill exercise 7.4
2. Design a phase-locked loop (following the general approach outlined by Horowitz & Hill) which produces an output signal at 1500 Hz from a 1000 Hz input signal. Design the LP filter in accordance with the rules of thumb outlined by Horowitz & Hill, and such that the output will not be affected (to within a decay time at least) by a 0.1 s dropout in the input.
3. Derive an expression for the signal-to-noise ratio of a non-inverting op-amp when the amplifier has a white noise input power spectrum of e_{na}^2 , and the resistors produce white noise as well. Express it in terms of the amplifier gain K , the size of one of the resistors, the temperature of the resistors, and the amplitude of the (assumed sinusoidal) input.