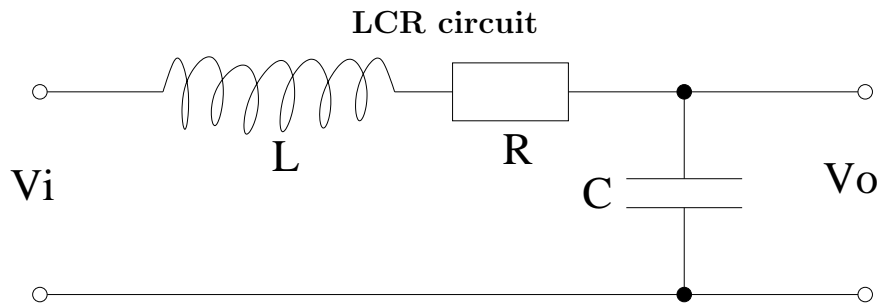


**EE 322 Analog Electronics, Spring 2010**  
**Exam 2 March 31, 2010**  
**Solution**

**Rules:** This is an open book test. You may use the textbooks as well as your notes. The exam will last 50 minutes. Each numbered problem counts equally toward your grade.



1. Derive the transfer function for this circuit.
2. What is the order and kind of filter is this? (e.g. high-, low-, etc...)
3. What is the natural frequency and  $Q$  value?
4. Extra credit: How is the filter modified if a inductor is added in parallel with the capacitor?

1. The transfer function is found from

$$T(s) = \frac{Z_2}{Z_1 + Z_2}$$

where

$$Z_2 = \frac{1}{sC} \quad Z_1 = sL + R$$

Then

$$T(s) = \frac{\frac{1}{sC}}{sL + R + \frac{1}{sC}} = \frac{1}{s^2LC + sCR + 1} = \frac{\frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

2. This is a second-order low-pass filter.
3. The natural frequency is

$$\omega_0 = \frac{1}{LC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

The  $Q$  value is found from

$$\frac{\omega_0}{Q} = \frac{R}{L} \quad Q = \frac{\omega_0 L}{R} = \frac{L}{\sqrt{LCR}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

4. If we add an inductor in series with the capacitor then

$$Z_2 = \frac{1}{\frac{1}{sL} + sC} = \frac{sL}{1 + s^2 LC}$$

and the transfer function becomes

$$\begin{aligned} T(s) &= \frac{\frac{sL}{1+s^2LC}}{\frac{sL}{1+s^2LC} + sL + R} = \frac{sL}{sL + (1 + s^2 LC)(sL + R)} \\ &= \frac{sL}{sL + sL + R + s^3 L^2 C + s^2 LCR} = \frac{sL}{s^3 L^2 C + s^2 LCR + 2sL + R} \\ &= \frac{s\frac{C}{L}}{s^3 + s^2 \frac{R}{L} + s\frac{1}{LC} + \frac{R}{L^2 C}} \end{aligned}$$

This is a third-order filter, and it is low-pass, although it only goes to zero at 40 dB per decade due to the single zero located at zero frequency.

### Filter implementation

Consider a filter with poles  $p_1 = 10^4 e^{j120^\circ}$  rad/s, and  $p_2 = 10^4 e^{j180^\circ}$  rad/s, and  $p_3 = 10^4 e^{j240^\circ}$  rad/s, and three zeros at infinity.

5. Is this one of our known standard filter types, and if so which one? What is the order of this filter? Is it a low-pass or high-pass filter? What is its 3 dB frequency?
  6. Draw a circuit which implements this filter, using a bi-quadratic circuit followed by a passive RC circuit.
  7. What should be the  $Q$  value of the second order portion of the circuit?
  8. Use 1 nF capacitors throughout and a 100 k $\Omega$  value for the input and feedback resistors, and specify the rest of the resistors.
  9. What is the maximum gain of the circuit, and at what frequency does it occur?
5. The poles are located at a fixed radius and spaced evenly in angle with a half of the angle spacing near the imaginary axis. This is the recipe for the Butterworth filter. There are three poles, so it is a 3rd order filter. All three zeros are located at infinity so it is a low-pass filter.

Regarding the 3-dB frequency, if we look carefully at the expressions and plots defining the Butterworth filter (particularly Figures 12.8 and 12.9) we can see that the 3-dB frequency is the pass-band edge when  $\epsilon = 1$ . And in that case,  $\omega_p = \omega_0 = 10^4$  rad/s.

6. It is a biquad circuit as shown in figure 12.24a, with a low-pass RC filter attached to the  $V_{lp}$  output, with the output voltage taken across the capacitor to ground.
7. Consult the book and find that the real component of  $p_1$  is  $-\frac{\omega_0}{2Q}$ , and thus

$$\cos(120^\circ) = -\frac{1}{2Q}$$

$$Q = -\frac{1}{2 \cos(120^\circ)} = 1$$

8. We are told that  $R_f = 100$  k $\Omega$  and  $R_2 = 100$  k $\Omega$ . Then  $R_1 = R_f = 100$  k $\Omega$ . We also have that  $R_3/R_2 = 2Q - 1$ , such that  $R_3 = (2Q - 1) R_2 = R_2 = 100$  k $\Omega$ . Finally,  $\omega_0 = \frac{1}{RC}$ , so that  $R = \frac{1}{\omega_0 C} = \frac{1}{10^4 \times 10 \times 10^{-9}} = 10$  k $\Omega$ .
9. Since this is a low-pass filter the maximum gain occurs at zero frequency. The maximum gain is

$$K = 2 - \frac{1}{Q} = 2 - 1 = 1$$