

# EE 322 Advanced Analog Electronics, Spring 2010 Homework #4 solution

SS 13.34. Figure P13.34 shows a monostable multivibrator circuit. In the stable state,  $v_o = L_+$ ,  $v_A = 0$ , and  $v_B = -V_{\text{ref}}$ . the circuit can be triggered by applying a positive input pulse of height greater than  $V_{\text{ref}}$ . For normal operation,  $C_1 R_1 \ll CR$ . Show the resulting waveforms of  $v_o$  and  $v_A$ . Also, show that the pulse generated at the output will have a width  $T$  given by

$$T = CR \ln \left( \frac{L_+ - L_-}{V_{\text{ref}}} \right)$$


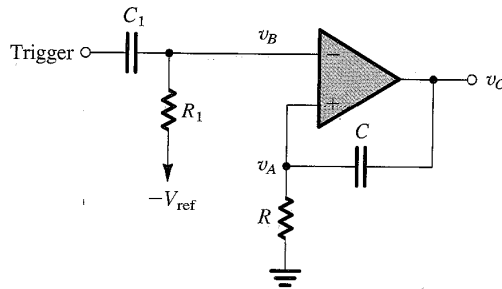


FIGURE P13.34

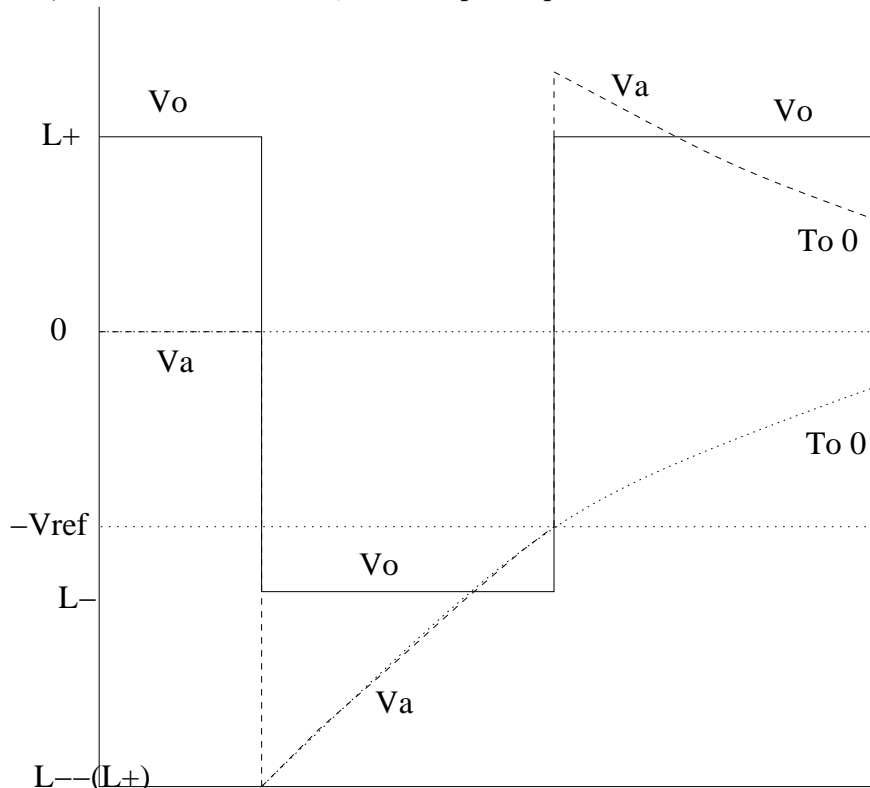$v_A$  begins at ground because there is no current through  $R$ . As the positive pulse is applied to trigger,  $v_B$  is pulled low which causes  $v_o$  to go low. The voltage across the capacitor is still  $L_+$ , so the voltage  $v_A = L_- - L_+$ . The capacitor begins to charge from that voltage to ground. However, once it reaches  $-V_{\text{ref}}$  the output flips. The waveforms are here



and here is the expression for determining  $T$


$$(L_- - L_+) e^{-\frac{T}{RC}} = -V_{\text{ref}}$$

which can be re-written as

$$\ln\left(\frac{-V_{\text{ref}}}{L_- - L_+}\right) = -\frac{T}{RC}$$

$$T = RC \ln\left(\frac{L_+ - L_-}{V_{\text{ref}}}\right)$$

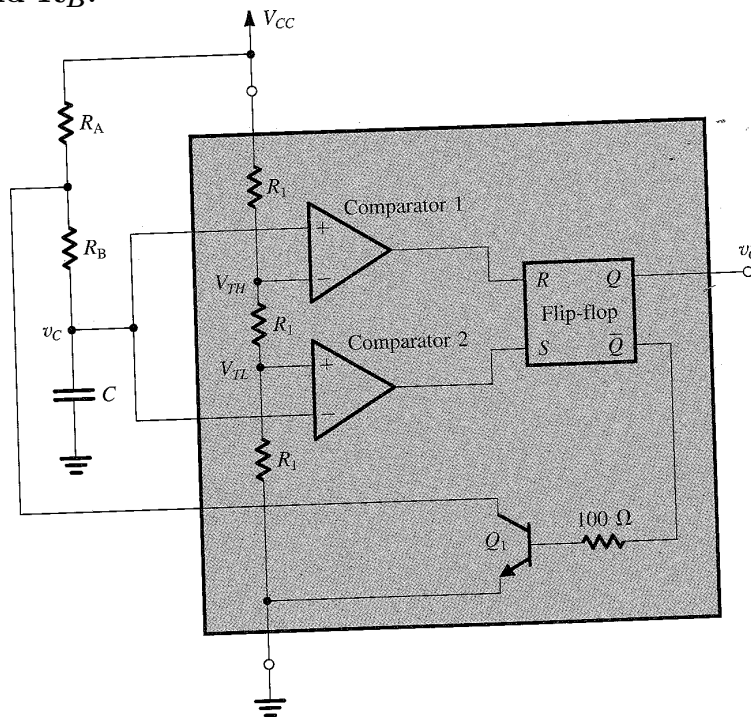**SS 13.39.** Using a 680 pF capacitor, design the astable circuit of Fig. 13.29(a) to obtain a square wave with a 50 kHz frequency and a 75% duty cycle. Specify the values of  $R_A$  and  $R_B$ .



This is a straightforward application of formulas given in the text book,

$$T = \frac{1}{f} = 0.69C(R_A + 2R_B) \quad \text{duty} = \frac{R_A + R_B}{R_A + 2R_B}$$

Begin by finding  $R_A + 2R_B$ ,

$$R_A + 2R_B = \frac{1}{0.69 f C} = \frac{1}{0.69 \times 50 \times 10^3 \times 680 \times 10^{-12}} = 42.63 \text{ k}\Omega$$

Next, find  $R_A + R_B$  from the duty cycle formula,

$$R_A + R_B = \text{duty} \times (R_A + 2R_B) = 0.75 \times 42.63 = 31.97 \text{ k}\Omega$$

Next,

$$R_B = (R_A + 2R_B) - (R_A + R_B) = 42.63 - 31.97 = 10.66 \text{ k}\Omega$$

and

$$R_A = (R_A + R_B) - R_B = 31.97 - 10.66 = 21.31 \text{ k}\Omega$$