

EE 322 Advanced Analog Electronics, Spring 2010 Homework #9 solution

SS 12.48. It is required to design a third-order low-pass filter whose $|T|$ is equiripple in both the passband and the stopband (in the manner shown in Fig. 12.3, except that the response shown is for $N = 5$). The filter passband extends from $\omega = 0$ to $\omega = 1$ rad/s and the stopband edge is at $\omega = 1.2$ rad/s. The following transfer function was obtained using filter design tables:

$$T(s) = \frac{0.4508(s^2 + 1.6996)}{(s + 0.7294)(s^2 + s0.2786 + 1.0504)}$$


The actual filter is to have $\omega_p = 10^4$ rad/s.

- (a) Obtain the transfer function of the actual filter by replacing s by $s/10^4$.
- (b) Realize this filter as the cascade connection of a first-order LP op-amp RC circuit of the type shown in Fig. 12.13(a) and a second-order LPN circuit of the type shown in Fig. 12.22(e). Each section is to have a dc gain of unity. Select appropriate component values. (Note: A filter with an equiripple response in both the passband and the stopband is known as an elliptic filter).


(a) Replacing s by $s/10^4$ we get

$$\begin{aligned} T(s) &= \frac{0.4508 \left(\frac{s^2}{10^8} + 1.6996 \right)}{\left(\frac{s}{10^4} + 0.7294 \right) \left(\frac{s^2}{10^8} + \frac{s0.2786}{10^4} + 1.0504 \right)} \\ &= \frac{4.508 \times 10^3 (s^2 + 1.6996 \times 10^8)}{(s + 7.294 \times 10^3) (s^2 + s2.786 \times 10^3 + 1.0504 \times 10^8)} \end{aligned}$$

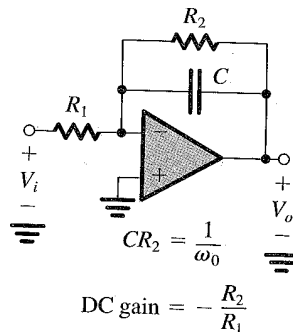(b) Here are the two filters we are to cascade. The first-order LP filter



and the second-order LPN filter

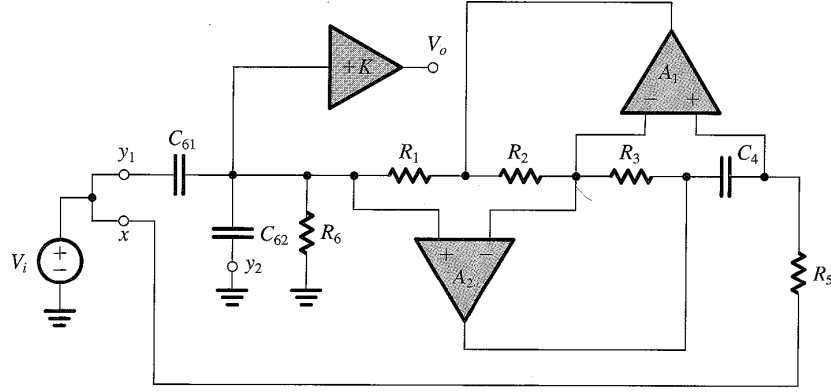

(e) LPN, $\omega_n \geq \omega_0$

The DC gain of the third-order filter is 0.9778, but I will design each filter for unity DC gain as directed.

For the first-order filter we need

$$CR_2 = \frac{1}{\omega_0} \quad \omega_0 = 7.294 \times 10^3 \text{ s}^{-1}$$

Choose $C = 10 \text{ nF}$ we get

$$R_2 = \frac{1}{\omega_0 C} = \frac{1}{7.294 \times 10^3 \times 10 \times 10^{-9}} = 13.7 \text{ k}\Omega$$

For unity DC gain amplitude we need $R_1 = R_2 = 13.7 \text{ k}\Omega$

Here are the properties of the 2nd-order LPN filter:

Low-pass notch (LPN)
Fig. 12.22(e)

$$T(s) = K \frac{C_{61}}{C_{61} + C_{62}}$$

$$\times \frac{s^2 + (R_2/C_4 C_{61} R_1 R_3 R_5)}{s^2 + s \frac{1}{(C_{61} + C_{62}) R_6} + \frac{R_2}{C_4 (C_{61} + C_{62}) R_1 R_3 R_5}} \quad K = \text{DC gain}$$

$$\omega_n = 1/\sqrt{C_4 C_{61} R_1 R_3 R_5 / R_2} \quad C_{61} + C_{62} = C_6 = C$$

$$\omega_0 = 1/\sqrt{C_4 (C_{61} + C_{62}) R_1 R_3 R_5 / R_2} \quad C_{61} = C(\omega_0 / \omega_n)^2$$

$$Q = R_6 \sqrt{\frac{C_{61} + C_{62}}{C_4} \frac{R_2}{R_1 R_3 R_5}} \quad C_{62} = C - C_{61}$$

Comparing this to the transfer function let's begin by selecting $R_6 = 10 \text{ k}\Omega$, and using the first-order term in the denominator. Then

$$C_{61} + C_{62} = \frac{1}{2.786 \times 10^3 \times R_6} = \frac{1}{2.786 \times 10^3 \times 10 \times 10^3} = 35.9 \text{ nF}$$

which is a reasonable value, so we proceed. Next, if we look at the constant term in the denominator and choose $R_1 = R_2 = R_3 = R_5 = 10 \text{ k}\Omega$, we get

$$\begin{aligned}
C_4 &= \frac{R_2}{1.0504 \times 10^8 \times (C_{61} + C_{62}) R_1 R_3 R_5} \\
&= \frac{10^4}{1.0504 \times 10^8 \times 35.9 \times 10^{-9} \times (10^4)^3} \\
&= 2.65 \text{ nF}
\end{aligned}$$

This is also an acceptable value, so we proceed. Next, we use the constant term in the parenthesis in numerator to determine C_{61} . We get

$$\begin{aligned}
C_{61} &= \frac{R_2}{1.6996 \times 10^8 C_4 R_1 R_3 R_5} \\
&= \frac{10^4}{1.6996 \times 10^8 \times 2.65 \times 10^{-9} \times (10^4)^3} \\
&= 22.2 \text{ nF}
\end{aligned}$$

This is also a reasonable value, and fortunately less than $C_{61} + C_{62}$, so we can now determine $C_{62} = C_{61} + C_{62} - C_{61} = 35.9 - 22.2 = 13.7 \text{ nF}$