

## Homework 2, due February 9, 2011

1. Derive the relationship between input and output voltages ( $V_{\text{in}}$ ,  $V_{\text{out}}$ ) and switch open and closed times ( $T_O$ ,  $T_C$ ) for the inverting and step-up switching regulators.
2. For a inverting switching regulator carefully plot the voltage at the output, and at the junction which connects the switch, the diode, and the inductor for continuous mode operation where  $V_{\text{in}} = 5 \text{ V}$  and  $V_{\text{out}} = -10 \text{ V}$ .
3. Repeat the previous question for discontinuous mode operation.
4. For a step-up switching regulator carefully plot the voltage at the output, and at the junction which connects the switch, the diode, and the inductor for continuous mode operation where  $V_{\text{in}} = 5 \text{ V}$  and  $V_{\text{out}} = 20 \text{ V}$ .
5. Repeat the previous question for discontinuous mode operation.