


# EE 322 Advanced Electronics, Spring 2012

## Homework #1 solution
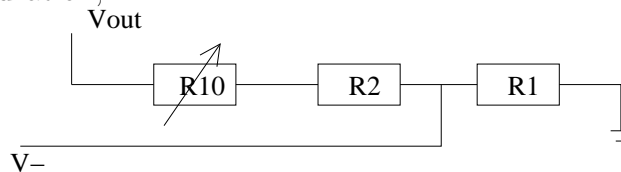
### HH 6.1

We are going to place a voltage divider on both the reference, and on the output. The output problem hints that we should compare a fraction of the output to half of the input, so let us place a voltage divider across the input. I will use two 4.7K resistors for that. We thus have an input of  $V_+ = 7.15/2 = 3.575\text{ V}$  on the input.

On the output we want to be able to adjust the voltage from +5 V to +10 V. We must have a voltage divider which can take a fraction of this and compare it to the input of the comparator. I will use a 10K potentiometer as the variable element. Let's say that when the potentiometer has zero resistance we want +5 V on the output whereas when the potentiometer has full resistance we want +10 V on the output. We will use two more resistors in this configuration,



and the relevant equations are

$$V_{\text{out,max}} \frac{R_1}{R_{10} + R_2 + R_1} = V_- \quad \text{and} \quad V_{\text{out,min}} \frac{R_1}{R_2 + R_1} = V_-$$

Dividing the two equations and re-arranging we get

$$\frac{V_{\text{out,max}}}{V_{\text{out,min}}} = \frac{R_{10} + R_2 + R_1}{R_2 + R_1}$$

Which gives us

$$2(R_2 + R_1) = R_{10} + R_2 + R_1$$

or

$$R_2 + R_1 = R_{10} = 10K$$

Next we go back to the equation for the minimum voltage and find that

$$\frac{V_{\text{out,min}}}{V_-} = \frac{R_2 + R_1}{R_1} = \frac{R_2}{R_1} + 1$$

Inserting  $V_{\text{out,min}}/V_- = 5/3.575 = 1.4$ , we get

$$\frac{R_2}{R_1} = 0.4$$

Inserting  $R_2 = R_{10} - R_1$  we get

$$\frac{R_{10} - R_1}{R_1} = 0.4$$

$$R_{10} - R_1 = 0.4R_1 \quad R_1 = \frac{R_{10}}{1.4} = 7.14K$$

Then


$$R_2 = R_{10} - R_1 = 10 - 7.14 = 2.86K$$

To limit the current to  $I_{\max} = 50 \text{ mA}$ , we insert a current-sensing resistor,  $R_{CS}$  such that

$$V_{BE,min} = I_{\max}R_{CS} \implies R_{CS} = \frac{V_{BE,min}}{I_{\max}} = \frac{0.5}{50 \times 10^{-3}} = 10 \Omega$$
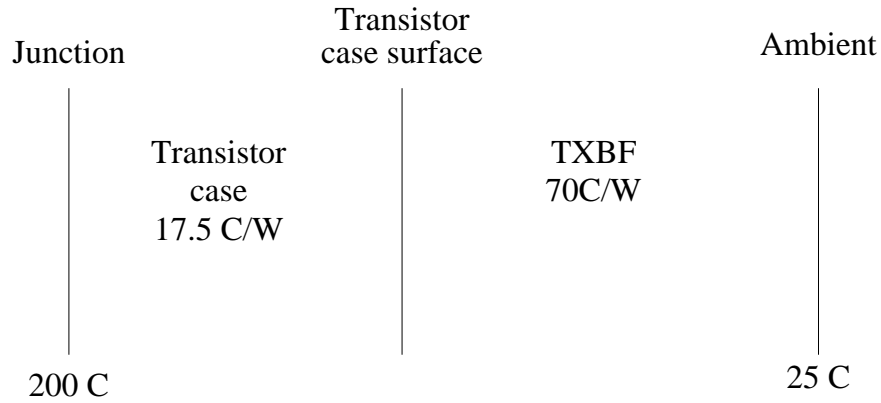
### HH 6.2

The scenario is illustrated in this figure



The temperature difference can be written as

$$T_{\text{junction}} - T_{\text{ambient}} = (\theta_{2N5320} + \theta_{\text{TXBF}}) P$$

And we wish to find  $P_{\max}$  corresponding to  $T_{\text{junction,max}} = 200^\circ\text{C}$ .

$$P_{\max} = \frac{T_{\text{junction,max}} - T_{\text{ambient}}}{\theta_{2N5320} + \theta_{\text{TXBF}}}$$

Inserting values we get

$$P_{\max} = \frac{200 - 25}{17.5 + 70} = 2 \text{ W}$$

### HH 6.3

I will first find the relationship between  $R_2$  and  $R_1$  with the formula

$$\frac{I_{\max}}{I_{\text{SC}}} = 1 + \frac{R_2}{R_1 + R_2} \frac{V_{\text{reg}}}{V_{\text{BE}}}$$

assuming that having  $R_1$  and  $R_2$  above  $1K\Omega$  will be sufficient to not draw significant current away from the current sensing resistor. We find

$$\frac{R_2}{R_1 + R_2} = \left( \frac{I_{\max}}{I_{\text{SC}}} - 1 \right) \frac{V_{\text{BE}}}{V_{\text{reg}}}$$

Inserting values from the problem we get

$$\frac{R_2}{R_1 + R_2} = \left( \frac{1}{0.4} - 1 \right) \frac{0.5}{5} = 0.15$$

If we choose  $R_2 = 1K$ , we get

$$R_2 = 0.15(R_1 + R_2) \Rightarrow R_2 = 0.15R_1 + 0.15R_2 \Rightarrow 0.85R_2 = 0.15R_1$$

$$R_1 = \frac{1 - 0.15}{0.15} R_2 = 5.7K$$

Next we want to find the value of the current sensing resistor,  $R_S$ . We will use the formula

$$I_{SC} = \frac{1}{R_S} \left( 1 + \frac{R_2}{R_1} \right) V_{BE}$$

or

$$R_S = \frac{1}{I_{SC}} \left( 1 + \frac{R_2}{R_1} \right) V_{BE}$$

Inserting values we get

$$R_S = \frac{1}{0.4} \left( 1 + \frac{1}{5.7K} \right) 0.5 = 1.25 \Omega$$

Note that the value of  $R_S$  is much smaller than the values we picked for  $R_1$  and  $R_2$ .