
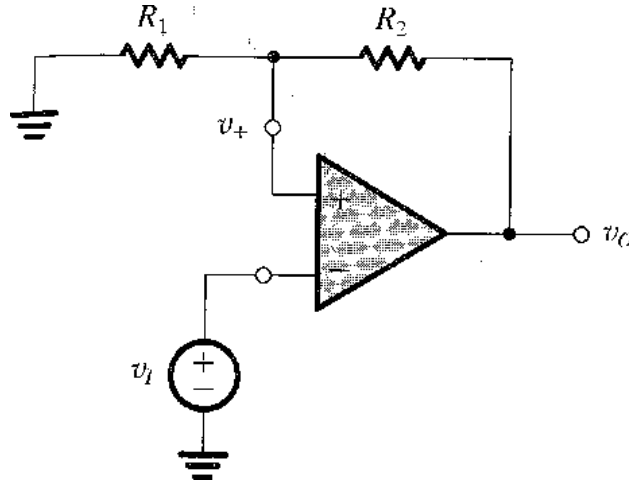


EE 322 Advanced Analog Electronics, Spring 2012 Homework #8 solution

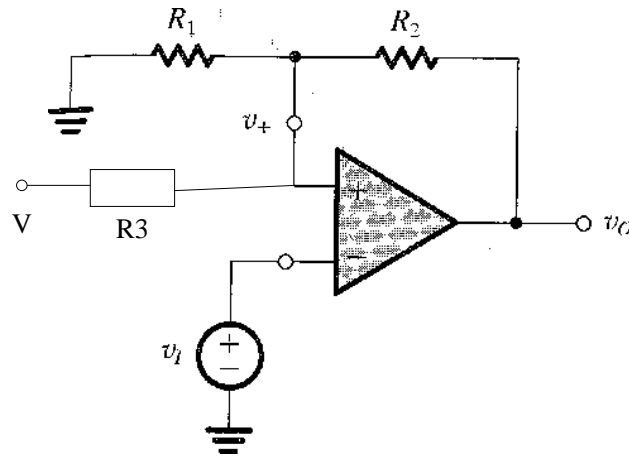SS 13.24 Consider the bistable circuit of Figure 13.19(a) with the op-amp's positive-input terminal connected to a positive voltage source V through a resistor R_3



The circuit we will consider looks like this



(a) Derive expressions for the threshold voltage V_{TL} and V_{TH} as a function of the op-amp's saturation levels L_+ and L_- , R_1 , R_2 , R_3 , and V .

To solve this we consider that the output can be either L_+ or L_- . Then it is a simple matter of computing V_+ for those two conditions. For the condition when $V_o = L_+$, we are computing V_{TH} , whereas when $V_o = L_-$, we are computing V_{TL} . First the generic expression for V_+ . We use current balance,

$$\frac{V - V_+}{R_3} + \frac{0 - V_+}{R_1} + \frac{V_o - V_+}{R_2} = 0$$

$$\frac{V}{R_3} + \frac{V_o}{R_2} = V_+ \left(\frac{1}{R_3} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_+ = \frac{\frac{V}{R_3} + \frac{V_o}{R_2}}{\frac{1}{R_3} + \frac{1}{R_1} + \frac{1}{R_2}}$$

$$= \frac{VR_1R_2 + V_oR_1R_3}{R_1R_2 + R_1R_3 + R_2R_3}$$

Now as mentioned before, for V_{TL} we insert $V_o = L_-$,

$$V_{TL} = \frac{VR_1R_2 + L_-R_1R_3}{R_1R_2 + R_1R_3 + R_2R_3}$$

and to find V_{TH} we insert $V_o = L_+$,

$$V_{TH} = \frac{VR_1R_2 + L_+R_1R_3}{R_1R_2 + R_1R_3 + R_2R_3}$$

(b) Let $L_+ = L_- = 13 \text{ V}$, $V = 15 \text{ V}$, and $R_1 = 10 \text{ k}\Omega$. Find the values of R_2 and R_3 that result in $V_{TL} = 4.9 \text{ V}$ and $V_{TH} = 5.1 \text{ V}$.

Manipulate the two equations with two unknowns R_2 and R_3 .

$$V_{TL}(R_1R_2 + R_1R_3 + R_2R_3) = VR_1R_2 + L_-R_1R_3$$

$$V_{TH}(R_1R_2 + R_1R_3 + R_2R_3) = VR_1R_2 + L_+R_1R_3$$

First, isolate R_3 in both equations,

$$R_3 = \frac{(V - V_{TL})R_1R_2}{V_{TL}R_1 + V_{TL}R_2 - L_-R_1}$$

$$R_3 = \frac{(V - V_{TH})R_1R_2}{V_{TH}R_1 + V_{TH}R_2 - L_+R_1}$$

Next take the ratio

$$1 = \frac{(V - V_{TL})[V_{TH}(R_1 + R_2) - L_+R_1]}{(V - V_{TH})[V_{TL}(R_1 + R_2) - L_-R_1]}$$

$$(V - V_{TH})[V_{TL}(R_1 + R_2) - L_-R_1] = (V - V_{TL})[V_{TH}(R_1 + R_2) - L_+R_1]$$

Now isolate R_2 ,

$$(V - V_{TL})V_{TH}R_2 - (V - V_{TH})V_{TL}R_2 =$$

$$(V - V_{TH})V_{TL}R_1 - (V - V_{TL})V_{TH}R_1 + (L_+(V - V_{TL}) - L_-(V - V_{TH}))R_1$$

$$(V_{TH} - V_{TL})V_{TH}R_2 = (V_{TL} - V_{TH})V_{TL}R_1 + (L_+(V - V_{TL}) - L_-(V - V_{TH}))R_1$$

$$R_2 = \left[\frac{L_+ (V - V_{TL}) - L_- (V - V_{TH})}{(V_{TH} - V_{TL}) V} - 1 \right] R_1$$

Inserting values we get

$$R_2 = \left[\frac{13 (15 - 4.9) + 13 (15 - 5.1)}{(5.1 - 4.9) 15} - 1 \right] 10 \text{ k}\Omega$$

$$= 856 \text{ k}\Omega$$

Now returning to one of the expressions for R_3 we get

$$R_3 = \frac{(V - V_{TL}) R_1 R_2}{V_{TL} (R_1 + R_2) - L_- R_1}$$

$$= \frac{(15 - 4.9) 10 \times 10^3 \times 856 \times 10^3}{4.9 (10 \times 10^3 + 856 \times 10^3) - 4.9 \times 10 \times 10^3}$$

$$= 20.6 \text{ k}\Omega$$

SS 13.26 For the circuit in Figure P13.26 sketch the transfer characteristics $v_o - v_i$. The diodes are assumed to have a constant 0.7 V drop when conducting, and the op-amp saturates at ± 12 V. What is the maximum diode current?

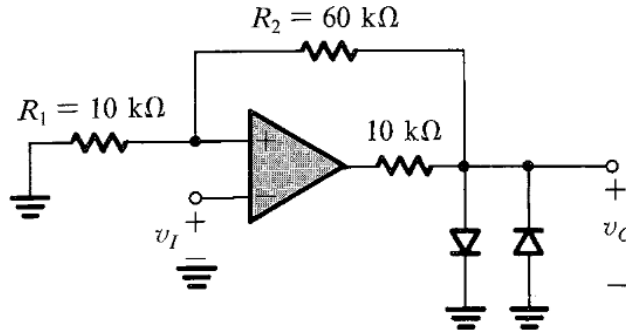


FIGURE P13.26


When the output of the op-amp is high, the output is 0.7 V. When the output of the op-amp is low, the output is -0.7 V. When the output is high (input is low), V_+ equals the high threshold voltage, V_{TH} ,

$$V_{TH} = V_o \frac{R_1}{R_1 + R_2} = 0.7 \frac{10}{10 + 60} = 0.1 \text{ V}$$

When the output is low (input is high), V_+ equals the low threshold voltage, V_{TL} ,

$$V_{TL} = V_o \frac{R_1}{R_1 + R_2} = -0.7 \frac{10}{10 + 60} = -0.1 \text{ V}$$

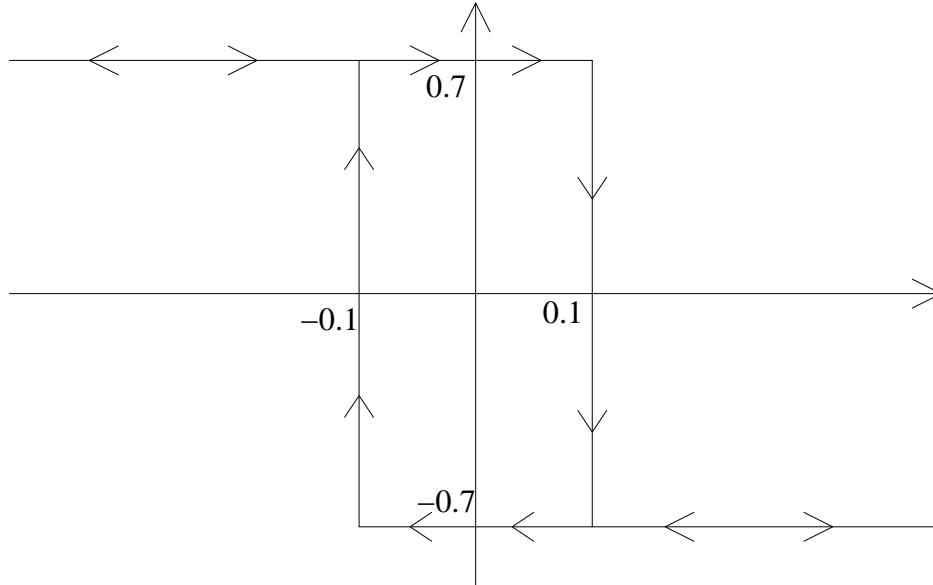
The transfer function thus looks like this




The maximum diode current is the output current from the op-amp minus the current diverted in the feedback loop.

$$\begin{aligned}
 I_{D,\max} &= (V_{12} - V_D) 10\text{ k}\Omega - \frac{V_D}{R_2 + R_1} \\
 &= \frac{12 - 0.7}{10 \times 10^3} - \frac{0.7}{70 \times 10^3} \\
 &= 1.12\text{ mA}
 \end{aligned}$$

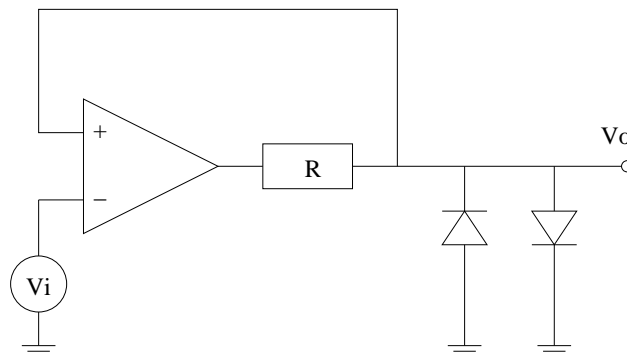
SS 13.27 Consider the circuit in Figure P13.26 with R_1 eliminated and R_2 short-circuited. Sketch and label the transfer characteristics $v_o - v_i$. Assume the diodes have a constant 0.7 V drop when conducting, and the op-amp saturates at $\pm 12\text{ V}$. The circuit looks like this



In this case, when the output is high (input is low), $V_+ = 0.7\text{ V}$, so $V_{TH} = 0.7\text{ V}$. When the output is low (input is high), $V_+ = -0.7\text{ V}$, so $V_{TL} = -0.7\text{ V}$. the transfer function looks like this

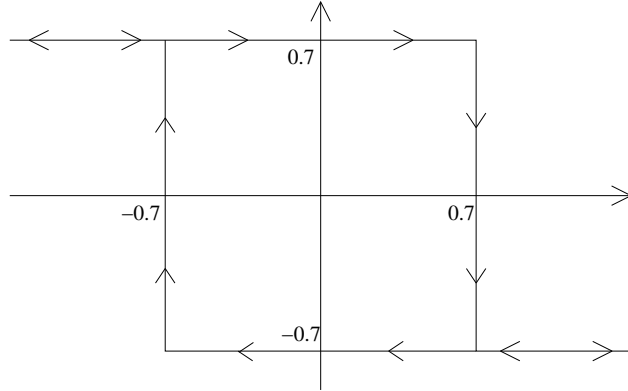

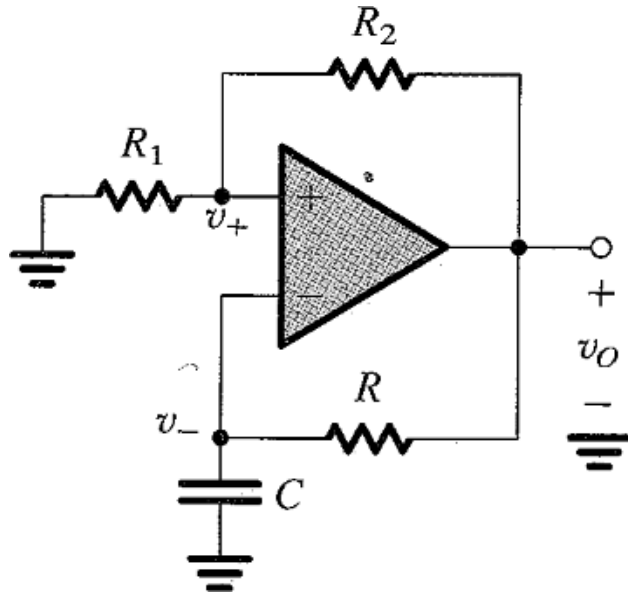SS 13.30 Find the frequency of oscillation of the circuit in Figure 13.24b for the case $R_1 = 10 \text{ k}\Omega$, $R_2 = 16 \text{ k}\Omega$, $C = 10 \text{ nF}$, and $R = 62 \text{ k}\Omega$.



In order to solve this problem we either need to know what the values of L_+ and L_- are, or we need to know that $L_+ = -L_-$. I will assume the latter. In that case we can use SS equation 13.33,

$$T = 2\tau \ln \frac{1 + \beta}{1 - \beta},$$

where $\tau = RC = 0.62 \text{ ms}$, and $\beta = \frac{R_1}{R_1 + R_2} = 0.3846$. We get

$$T = 2 \times 0.62 \times \ln \frac{1.3846}{0.6154} = 1.01 \text{ ms}$$