

### Homework 4, February 18, 2013

1. Design an inverting amplifier with a gain  $-10$  and an input resistance of  $100\text{ k}\Omega$ .
2. Assume  $T = 293\text{ K}$ , and amplifier  $e_{na} = 10\text{ nV}/\sqrt{\text{Hz}}$ , computing the output noise power spectrum.
3. If the input is a sinusoidal signal with amplitude  $1\text{ }\mu\text{V}$ , what is the SNR at the output in a  $1\text{ kHz}$  bandpass? And in a  $40\text{ Hz}$  bandpass.
4. If the source has output resistance  $1\text{ M}\Omega$  (consider its noise), which amplifier gain will maximize the output SNR?