

## EE 322 Advanced Electronics, Spring 2013

### Exam 1

Monday March 4, 2013

**Rules:** This is a closed-book exam. You may use only your brain, a calculator and pen/paper. Each numbered question counts equally toward your grade.

**Note:** The questions are designed to test your conceptual understanding, not your ability to do many pages of math. If you find yourself doing long calculations there is a high probability that you are doing something wrong.

#### Linear regulator

The LM317 linear regulator has 3 pins: a input pin, a output pin, and a adjust pin. The output voltage is selected through a voltage divider scheme involving the output, the adjust pin, and ground. The voltage between output and regulation is 1.25 V.

1. Select resistors to create an output voltage of 5 V, with the smallest resistor being 10 k $\Omega$ . Show the circuit with component values.

Smallest resistor is between ADJ and output, call it  $R_2 = 10 \text{ k}\Omega$ . We then have

$$1.25 = \frac{R_2}{R_1 + R_2} \times 5$$

$$1.25 (R_1 + R_2) = 5R_2$$

$$R_1 = \frac{3.75 R_2}{1.25} = 30 \text{ k}\Omega$$

2. Add a bypass BJT and resistor such that the bypass turns on when the power dissipation in the LM317 reaches 0.5 W for a 15 V input. Show the circuit with component values.

The voltage drop across the LM317 will be  $15 - 5 - 0.5 = 9.5 \text{ V}$  (the 0.5 from drop across current sense resistor). The maximum current comes from


$$I = \frac{P}{V} = \frac{0.5}{9.5} = 53 \text{ mA}$$

That current must produce 0.5 V across the current sense resistor, thus

$$R_s = \frac{0.5}{0.053} = 9.4 \Omega$$

## Switching regulator

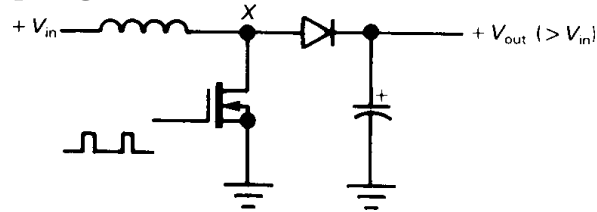3. Draw the step-up regulator we discussed in class.



4. What is the output voltage if the input voltage is 5 V and the inductor current ramps up for twice as long as it ramps down?

The slope is

$$\frac{dI}{dt} = \frac{\Delta V}{L}$$

and the down slope is twice the up slope, so the voltage while the current is decreasing is twice the voltage while it is increasing. The decreasing current voltage is  $V_{\text{out}} - V_{\text{in}}$  and thus we must conclude that  $V_{\text{out}} = 15 \text{ V}$ .

5. Plot, for discontinuous mode, the voltage at the junction of the switch, diode, and inductor. Make sure to show the correct ratio between duration of up- and down-ramp. You may assume ideal components.

### Electronic noise

Examine a inverting amplifier. You need to amplify a source signal by a  $G_{vo} = -100$ . The source has output resistance  $1\text{ M}\Omega$ . A amplifier with finite input resistance thus needs a gain ( $A_{vo}$ ) larger than that to provide the specified  $G_{vo}$ . The op-amp noise is  $e_{na} = 100\text{ nV}/\sqrt{\text{Hz}}$ . You may assume  $T = 300\text{ K}$ ,  $k = 1.4 \times 10^{-23}$ , and  $B = 1\text{ kHz}$ .

6. If the amplifier input resistance is  $1\text{ M}\Omega$ , select the appropriate feedback resistor and compute the output RMS noise.

Since the amplifier input resistance equals the source resistance the signal is cut in half at the amplifier input and we thus need a gain of  $-200$  on the amplifier. That means that  $R_2 = 200\text{ M}\Omega$ . The noise on the output is then

$$\begin{aligned} v_n &= \sqrt{4kT(R_s + R_1)A^2 + e_{na}^2(|A| + 1)^2 + 4kTR_2}\sqrt{B} \\ &= \sqrt{4 \times 1.4 \times 10^{-23} \times 300 \times 2 \times 10^6 \times 200^2} \\ &\quad + (100 \times 10^{-9})^2 \times 201^2 \quad \times \sqrt{10^3} \\ &\quad + 4 \times 1.4 \times 10^{-23} \times 300 \times 200 \times 10^6 \\ &= 1.0\text{ mV} \end{aligned}$$

7. Does the noise improve (get smaller) if you use a  $100\text{ M}\Omega$  input resistance instead (and correspondingly smaller  $A_{vo}$ )?

In this case the input resistance is MUCH larger than the source resistance so I will just approximate a gain of  $-100$  and thus the feedback resistance is  $10\text{ G}\Omega$ . Use the same equation as in the previous question but with  $R_1 = 100\text{ M}\Omega$ ,  $A = -100$ ,  $R_2 = 10\text{ G}\Omega$ .

$$\begin{aligned} v_n &= \sqrt{4kT(R_s + R_1)A^2 + e_{na}^2(|A| + 1)^2 + 4kTR_2}\sqrt{B} \\ &= \sqrt{4 \times 1.4 \times 10^{-23} \times 300 \times 101 \times 10^6 \times 100^2} \\ &\quad + (100 \times 10^{-9})^2 \times 101^2 \quad \times \sqrt{10^3} \\ &\quad + 4 \times 1.4 \times 10^{-23} \times 300 \times 10 \times 10^9 \\ &= 4.2\text{ mV} \end{aligned}$$

Thus the answer is no, using larger input resistance does not improve the noise in this case.