

EE 322 Advanced Electronics, Spring 2013


Exam 3
Friday April 26, 2013

Rules: This is a closed-book exam. You may use only your brain, a calculator and pen/paper. Each numbered question counts equally toward your grade.

Note: The questions are designed to test your conceptual understanding, not your ability to do many pages of math. If you find yourself doing long calculations there is a high probability that you are doing something wrong.

Relaxation Oscillators

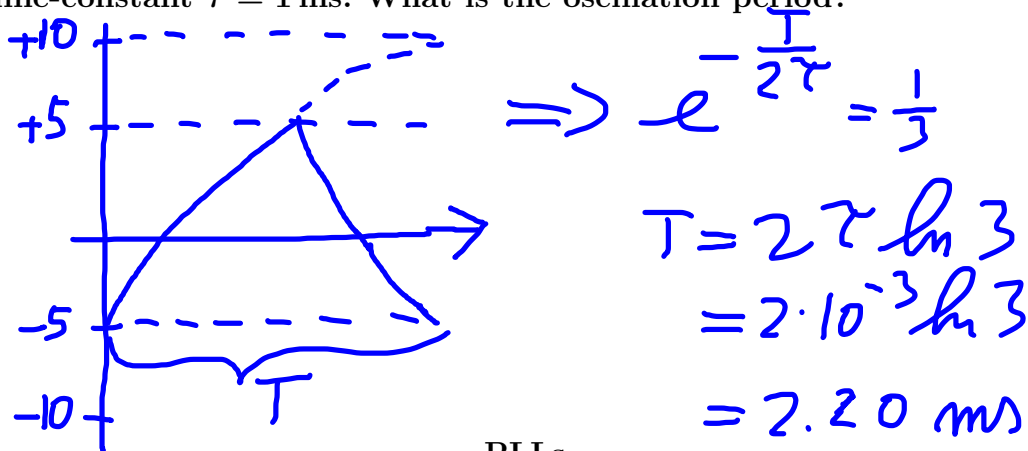1. A relaxation oscillator has $L_+ = -L_- = 10\text{ V}$ and $V_{TH} = -V_{TL} = 5\text{ V}$, and time-constant $\tau = 1\text{ ms}$. What is the oscillation period?




PLLs

Consider a PLL with a XOR phase detector producing output levels of 0 and 5 V. The VCO is modeled as $f = 2\text{ kHz} + 1 \frac{\text{kHz}}{\text{V}} \times V_{in}$, and the VCO output is fed directly back to the phase detector without division.

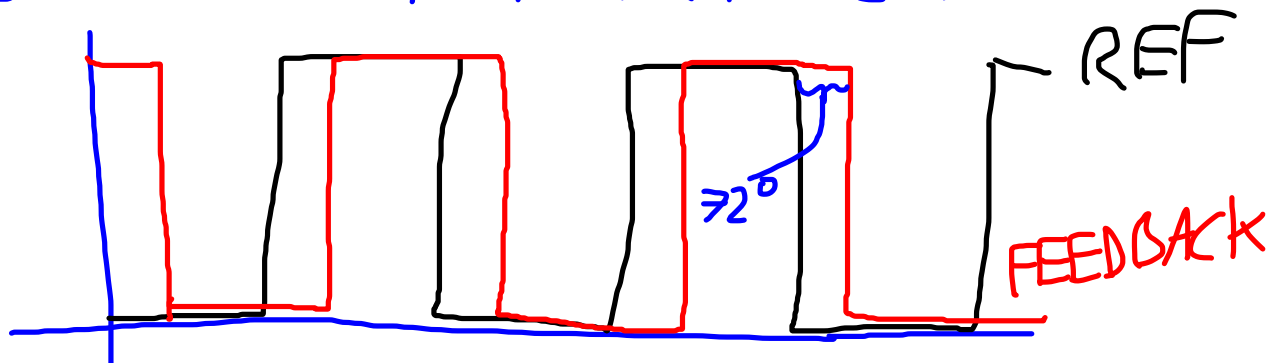2. For $f = 4\text{ kHz}$ compute the phase difference between the reference signal and the feedback signal (both have 50% duty cycle) and sketch several periods with the phase labeled accurately.


PLL INPUT IS $\frac{4-2}{1} = 2\text{ V}$
 THEN WE HAVE $\frac{\Delta\phi}{180} = \frac{2}{5} \Rightarrow \Delta\phi = 72^\circ$
 POSITIVE SLOPE MEANS REFERENCE LEADS.



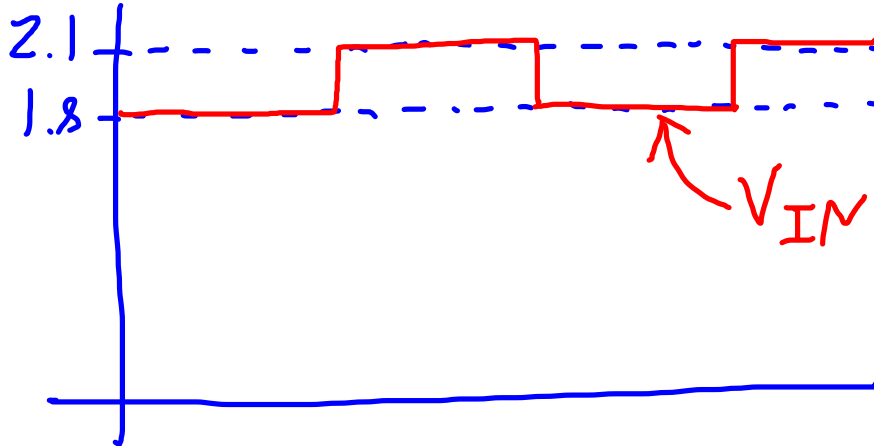3. For the same PLL sketch the input to the VCO to scale when the input signal is frequency-shift-key modulated between 3.8 kHz and 4.1 kHz.

$$3.8 \text{ kHz} \Rightarrow V_{IN} = \frac{3.8 - 2}{1} = 1.8 \text{ V}$$



$$4.1 \text{ kHz} \Rightarrow V_{IN} = 2.1$$




Filters

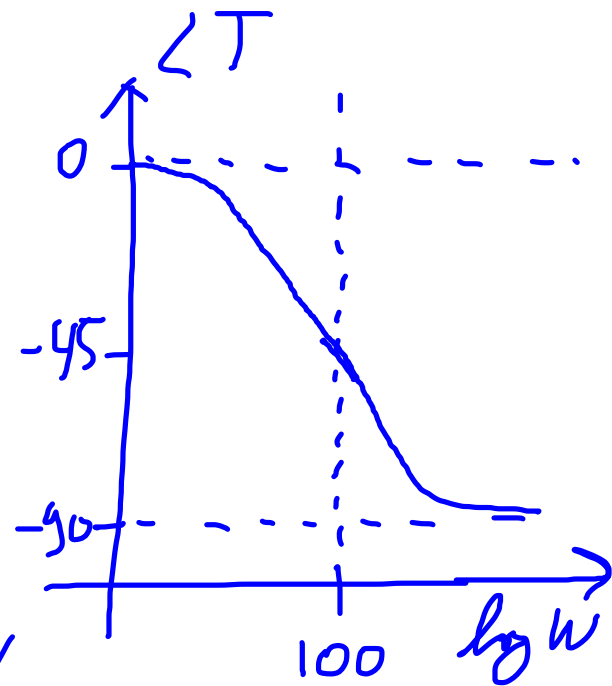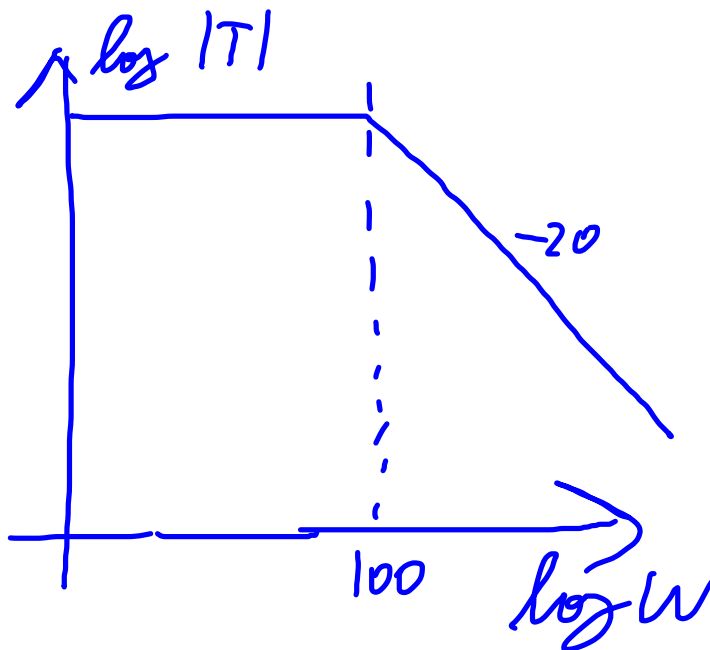4. Accurately plot the amplitude and phase of a filter which has a single pole at $-100 + j0$ rad/s. Use log-log for the amplitude plot and log-lin for the phase plot.

THIS IS JUST A 1ST ORDER LOW PASS FILTER WITH $\omega_0 = 100 \text{ s}^{-1}$
 THUS:



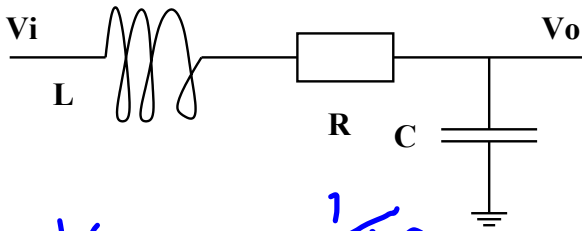5. Derive the transfer function for this filter as a ratio of polynomials in s .



$$\begin{aligned} \frac{V_o}{V_i} &= \frac{\frac{1}{sC}}{\frac{1}{sC} + sL + R} \\ &= \frac{1}{1 + s^2 LC + sCR} \\ &= \frac{\frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}} \end{aligned}$$

6. What kind of filter is it?

LP

7. If $L = 1 \text{ mH}$, $C = 100 \text{ nF}$, and $R = 100 \Omega$, what are ω_0 and Q ?

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \cdot 10^{-7}}} = 10^5 \text{ s}^{-1}$$

$$\frac{\omega_0}{Q} = \frac{R}{L} \Rightarrow Q = \omega_0 \frac{L}{R} = 10^5 \frac{10^{-3}}{100} = \underline{\underline{1}}$$