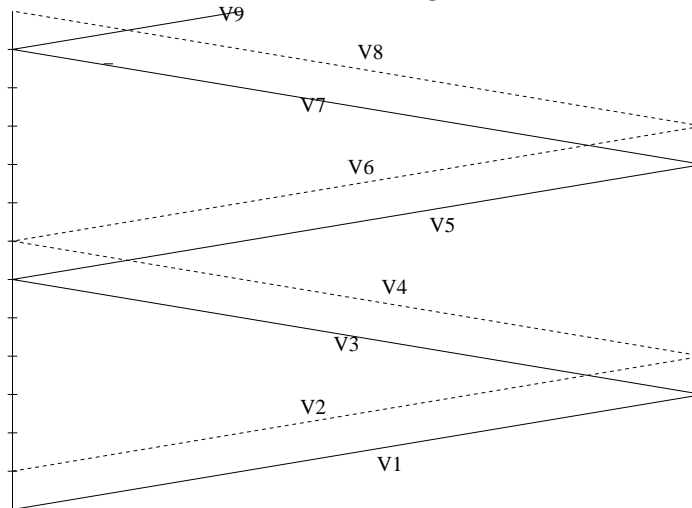


## EE 333 Electricity and Magnetism, Fall 2009 Homework #13 solution

7.12. A pulse generator of output voltage  $V_G = 1, \text{V}$  and pulse duration of  $1 \mu\text{s}$  is connected to a transmission line of characteristic impedance  $Z_0 = 50 \Omega$ . and a velocity of propagation of  $u = 3 \times 10^8 \text{ m/s}$ . The internal resistance of the pulse generator is  $R_G = 75 \Omega$ , and the resistance terminating the transmission line is  $R_L = 150 \Omega$ . The length of the transmission line is  $d = 900 \text{ m}$ . Use the reflection diagram to determin the following:

1. The voltage at the sending end as a function of time  $t$  up to  $t = 12 \mu\text{s}$ .
  2. The voltage at the load terminating the transmission line as a function of time up to time  $t = 10 \mu\text{s}$ .
1. The pulse consists of a positive transient followed by a negative transient. I draw the positive transient as a solid curve and the negative transient as a dashed curve.



The reflection coefficient at the load is

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{150 - 50}{150 + 50} = \frac{1}{2}$$

and at the generator it is

$$\Gamma_G = \frac{Z_G - Z_0}{Z_G + Z_0} = \frac{75 - 50}{75 + 50} = \frac{1}{5}$$

Then we have

$$V_1 = V_G \frac{Z_0}{Z_G + Z_0} = 1 \times \frac{50}{50 + 75} = 0.4 \text{ V}$$

$$V_2 = -V_1 = -0.4 \text{ V}$$

$$V_3 = V_1 \Gamma_L = 0.4 \times 0.5 = 0.2 \text{ V}$$

$$V_4 = -V_3 = -0.2 \text{ V}$$

$$V_5 = V_3 \Gamma_G = 0.2 \times 0.2 = 0.04 \text{ V}$$


$$V_6 = -V_5 = -0.04 \text{ V}$$

$$V_7 = V_5 \Gamma_L = 0.04 \times 0.5 = 0.02 \text{ V}$$

$$V_8 = -V_7 = -0.02 \text{ V}$$

$$V_9 = V_7 \times \Gamma_G = 0.02 \times 0.2 = 0.004 \text{ V}$$

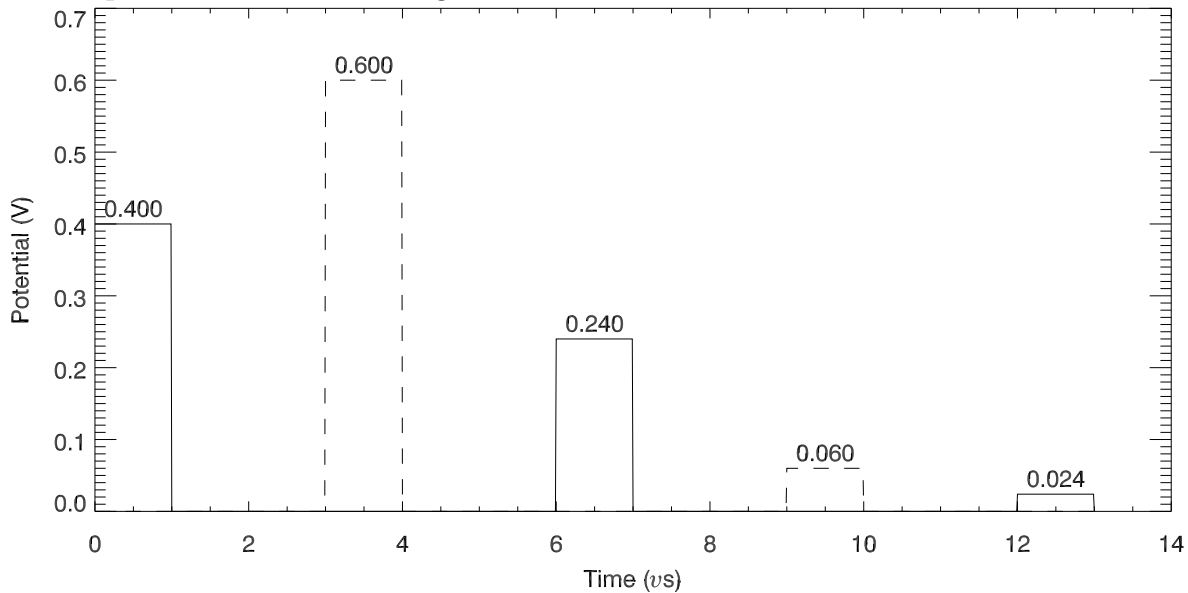2. Here are the waveforms. The solid curve is the potential at the sending end, the dashed the potential at the receiving end.



**7.17.** An antenna of input impedance  $Z_L = 75 + j150 \Omega$  at 2 MHz is connected to a transmitter through a 100-m section of coaxial cable, which has the following distributed constants:  $r = 150 \Omega/\text{km}$ ,  $l = 1.4 \text{ mH}/\text{km}$ ,  $c = 88 \text{ nF}/\text{km}$ , and  $g = 0.8 \mu\text{S}/\text{km}$ . If the output voltage of the transmitter is  $V_G = 100e^{j0^\circ} \text{ V}$  and its internal impedance is  $75 \Omega$  as shown in Figure P7-17, determine the following:

1. The characteristic impedance  $Z_0$  and the propagation constant  $\gamma = \alpha + j\beta$  of the coaxial cable.
2. The input impedance  $Z_{\text{in}}$  of the cable terminated by the antenna.
3. The average power delivered to the load antenna.

1. The characteristic impedance. We have

$$\begin{aligned} r + j\omega l &= 153 + j \times 2 \times \pi \times 2 \times 10^6 \times 1.4 \times 10^{-3} \\ &= 153 + j17593 \Omega/\text{km} \end{aligned}$$

$$\begin{aligned} g + j\omega c &= 0.8 \times 10^{-6} + j \times 2 \times \pi \times 2 \times 10^6 \times 88 \times 10^{-9} \\ &= 0.8 \times 10^{-6} + j1.11 \Omega^{-1}/\text{km} \end{aligned}$$

To a good approximation the characteristic impedance is then

$$Z_0 = \sqrt{\frac{l}{c}} = \sqrt{\frac{1.4 \times 10^{-3}}{88 \times 10^{-9}}} = 126 \Omega$$

For low-loss lines we have

$$\begin{aligned} \alpha &= \frac{1}{2} \left( r\sqrt{\frac{c}{l}} + g\sqrt{\frac{l}{c}} \right) \\ &= \frac{1}{2} \left( 150\sqrt{\frac{88 \times 10^{-9}}{1.4 \times 10^{-3}}} + 0.8 \times 10^{-6}\sqrt{\frac{1.4 \times 10^{-3}}{88 \times 10^{-9}}} \right) \\ &= 0.595 \text{ km}^{-1} \end{aligned}$$

$$\beta = \omega\sqrt{lc} = 2 \times \pi \times 2 \times 10^6 \times \sqrt{1.4 \times 10^{-3} \times 88 \times 10^{-9}} = 139 \text{ km}^{-1}$$

2. The reflection coefficient at the load is

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{75 + j150 - 126}{75 + j150 + 126} = -51 + j150201 + j150 = \frac{158e^{j109^\circ}}{250e^{j37^\circ}} = 0.632e^{j72^\circ}$$

We can then propagate this to a reflection coefficient at the transmitting end

$$\Gamma_G = \Gamma_L e^{-2\gamma d}$$

where  $d = 100 \text{ m}$ ,

$$\gamma d = \alpha d + j\beta d = 0.595 \times 0.1 + j139 \times 0.1 = 0.0595 + j13.9 = 0.0595 + j796^\circ$$

$$\begin{aligned} \Gamma_G &= 0.632e^{j72^\circ} e^{-2 \times 0.595} e^{-2j \times 796^\circ} \\ &= 0.561e^{j280^\circ} \end{aligned}$$

3. Next convert that into an impedance,

$$\begin{aligned}
 Z_{\text{in}} &= Z_0 \frac{1 + \Gamma_G}{1 - \Gamma_G} = 126 \frac{1 + 0.561e^{j280^\circ}}{1 - 0.561e^{j280^\circ}} = 126 \frac{1 + 0.974 - 0.552j}{1 - 0.0974 + 0.552j} \\
 &= 126 \frac{1.0974 - j0.552}{0.903 + j0.552} = 126 \frac{1.228e^{-j27^\circ}}{1.058e^{j31^\circ}} = 146e^{-j58^\circ} \\
 &= 77 - j124 \Omega
 \end{aligned}$$

Now I will cheat a little and find total input power to the cable plus antenna, not just to the antenna (which would require finding voltage and current at the load end of the line).

$$\begin{aligned}
 V_{\text{in}} &= V_G \frac{Z_{\text{in}}}{Z_G + Z_{\text{in}}} = 100 \times \frac{146e^{-j58^\circ}}{75 + 77 - j124} = 100 \frac{146e^{-j58^\circ}}{152 - j124} = 100 \times \frac{146e^{-j58^\circ}}{196e^{-j32^\circ}} \\
 &= 74.5e^{-j26^\circ} \text{ V}
 \end{aligned}$$

The average input power is then

$$P_{\text{in}} = \frac{1}{2} \text{Re}(VI^*) = \frac{1}{2} \text{Re} \left( \frac{V^2}{|Z_{\text{in}}|} \cos(\phi) \right) = \frac{1}{2} \frac{74.5^2}{146} \cos(58^\circ) = 10.1 \text{ W}$$