

## Lab 3: Decoders and Multiplexers

September 22, 2009

Decoders and multiplexers are important combinational circuits in many logic designs. Decoders convert  $n$  inputs to a maximum of unique  $2^n$  outputs. A special case is the BCD-to-seven-segment decoder, where a four-bit decimal digit (represented in BCD) is decoded into the corresponding seven segment code used as an input to the seven-segment display (Figure 1).

 


Figure 1: 7-segment display

## Contents

<b>1 Prelab</b>	<b>2</b>
<b>2 Lab</b>	<b>4</b>
<b>3 Supplementary Material</b>	<b>7</b>
3.1 More on Verilog . . . . .	7
3.1.1 Three-State Gates . . . . .	7
3.1.2 Logic Levels . . . . .	7
3.2 Verilog - Behavioral Modeling . . . . .	7
3.2.1 <code>always</code> and <code>reg</code> . . . . .	7
3.2.2 <code>if-else</code> Statements . . . . .	8
3.2.3 <code>case</code> Statements . . . . .	9

## 1 Prelab

1. Wire wrap the two 7-segment displays along with the pin header needed on a perf board (as shown in Figure 2). schematics of MAN74 7-segment display. **What is shown in the figure is only a**

 


Figure 2: Dip switches

**suggestion as a start and you may need to do some modifications. For example, rather**

than having the ground pins at the top and bottom of the board, you may put those pins seperately on the side. So rather than having 10 pins at the top and the bottom, you will have 8 pins on the top, 8 pins on the bottom and 4 pins on the side. This will give you more flexibility in connecting the board.

2. Fill in the truth table for the BCD-to-7-segment decoder shown in Table 1, e.g., if the input is 0011, LEDs a,b,c,d and g should be on while LEDs f and e will be off (see Figure 1). For inputs 0xA through 0xF, naturally they don't correspond to any number in the range 0-9, therefore output the corresponding hex value instead, i.e., for 0xA the display should show the letter A.
3. A simple computer has several main blocks, e.g.,
  - Arithmetic logic unit (ALU): performs arithmetic operations on numbers.
  - Memory: where the program is stored.
  - Multiplexers: select which piece of information to be passed on.
  - Decoders: to determine, based on the input, whether to read from memory or input/output lines.
  - Computer control unit: outputs the control signals that direct the operation of the rest of the computer.

Even though we are not building a computer, this information gives you some prospective on the different components that you will be building and what they may be used for.

In this labs lab we will focus on the multiplexer that chooses either a program address (PROG\_ADDR), program counter (PC), memory address register (MAR) or index register X (X). These signals are used to determine the information required to enter the arithmetic logic unit component of the computer.

- (a) Design a multiplexer with MEM\_SEL as the select signal, PROG\_ADDR, PC, MAR and X as 8-bit input signals.
- (b) Design a Verilog program to implement this multiplexer.

Digit	Binary	a	b	c	d	e	f	g
0								
1								
2								
3	0011	1	1	1	1	0	0	1
4								
5								
6								
7								
8								
9								
A								
B								
C								
D								
E								
F								

Table 1: Truth table for 7-segment-display decoder (1 means that LED is on and 0 means off).

## 2 Lab

1. Place a block of 8 DIP switches on your breadboard, see Figure 3.
2. Connect each lead on one side to VCC.
3. Put a 1k resistor from each of the leads on the other side to ground. Also on this side, place a row of 8 pin headers so that you have outputs from all of these switches.
4. Use Figure 6 for the pin labels.
5. Now that you have all the hardware setup. Design the BCD-to-seven-segment decoder and test it using different inputs using the dip switches.
6. Implement your multiplexer program that you developed in the prelab.

 


Figure 3: Dip switches

 


Figure 4: MAX II micro board



Figure 5: MAX II micro board with pin headers

 


Figure 6: I/O map of prototyping areas

## 3 Supplementary Material

### 3.1 More on Verilog

#### 3.1.1 Three-State Gates

If the control signal is 1, the output is enabled, and if the control signal is 0, the output is disabled and the gate is in high-impedance mode. There are three types of three-state gates.

1. `bufif1(output, input, control)`: output equals the input if the control signal is 1, and high-impedance state, `z`, if the control signal is 0.
2. `bufif0(output, input, control)`: the control signal is the complement of `bufif1`.
3. `notif1(output, input, control)`: same as `bufif1` except the output is the complement of the input if the control signal is 1.
4. `notif0(output, input, control)`: same as `bufif0` except the output is the complement of the input if the control signal is 0.

#### 3.1.2 Logic Levels

0		logic zero, false condition
1		logic one, true condition
x		unknown logic value
z		high impedance

### 3.2 Verilog - Behavioral Modeling

#### 3.2.1 `always` and `reg`

1. Behavioral modeling use the keyword `always`.

 


Figure 7: Three-state gate

2. Target output is of type `reg`. Unlike a `wire`, `reg` is updated only when a new value is assigned. In other words, it is not continuously updated as `wire` data types.
3. `always` may be followed by an event control expression.
4. `always` is followed by the symbol `@` followed by a list of variables. Each time there is a change in those variables, the `always` block is executed.
5. There is no semicolon at the end of the `always` block.
6. The list of variables are separated by logical operator `or` and not bitwise OR operator `"|"`.
7. Below is an example of an `always` block.

---

```
always @(A or B)
.
.
.
```

---

### 3.2.2 if-else Statements

`if-else` statements provide means for a conditional output based on the arguments of the `if` statement.

---

```
.
.
.

output out;
input s,A,B;
reg out;

.
.
.

if (s) out = A; //if select is 1 then out is A
else out = B; //else output is B

.
.
.
```

---



### 3.2.3 case Statements

case Statements provide an easy way to represent a multi-branch conditional statement.

1. The first statement that makes a match is executed.
2. Unspecified bit patterns could be treated using `default` keyword.

---

**Program 1** four-to-one line multiplexer

---

```
module mux_4x1_example(  
    output reg out,  
    input [1:0] s,          // select is represented by 2 bits  
    input in_0, in_1, in_2, in_3  
);  
  
always @(in_0, in_1, in_2, in_3, s)  
    case (s)                //no semi-colon  
        2'b00: out = in_0; //if s is 00 then output is in_0  
        2'b01: out = in_1; //else if s is 01 then out is in_1  
        2'b10: out = in_2; //else if s is 10 then out is in_2  
        2'b11: out = in_3; //else if s is 11 then out is in_3  
    endcase                //case statement ends with endcase  
endmodule
```

---