

# Lecture 2 - B

## Analog Signal Conditioning

EE 521: Instrumentation and Measurements

Lecture Notes Update on September 9, 2009

Aly El-Osery, Electrical Engineering Dept., New Mexico Tech

2 - B.1

### Contents

<b>1 Frequency Response</b>	<b>1</b>
<b>2 Current Feedback Op-amps</b>	<b>2</b>
<b>3 CFA Circuit Examples</b>	<b>4</b>
<b>4 Additional References</b>	<b>5</b>

2 - B.2

## 1 Frequency Response

Open-Loop Frequency Response

$$A_D(f) = \frac{k_{ov}}{1 + j\frac{f}{f_{PD}}} \quad (1)$$

where  $f_{PD}$  is the dominant-pole frequency and  $k_{ov}$  is the low frequency open-loop gain. In addition, the unity-gain bandwidth is given by

$$f_T = f_{PD}k_{ov} \quad (2)$$

2 - B.3

Open-loop Gain Magnitude

See Figure 1

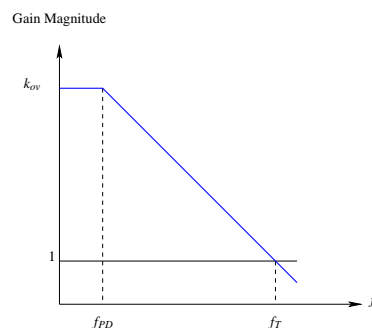


Figure 1: Bode plot

2 - B.4

## Close-loop Frequency Response

For non-inverting amplifier

$$A_D(f) = \frac{1/\beta}{1 + j \frac{f}{f_{PD}\beta k_{ov}}} \quad (3)$$

where  $\beta = R_1/(R_1 + R_F)$ , the 3dB frequency is

$$f_{3dB} = f_{PD}\beta k_{ov} \quad (4)$$

and

$$GBWP = f_T \quad (5)$$

See Figure 2

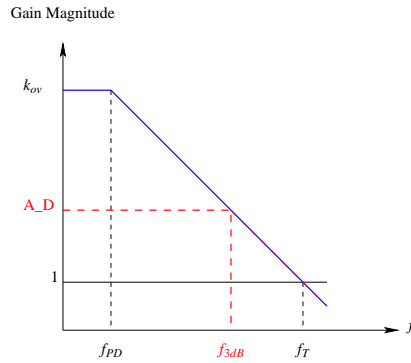


Figure 2: Bode plot

2 - B.5

## 2 Current Feedback Op-amps

Unlike Voltage Feedback Amplifiers (VFA), in Current Feedback Amplifiers (CFA) the inverting input is sensitive to current. CFAs offer much higher slew rates as compared to voltage feedback op-amps. See Figure 3

$$\Omega_s = \Omega_o / (\tau s + 1) \quad (6)$$

$$V_o = I_n [\Omega_o / (\tau s + 1)] \quad (7)$$

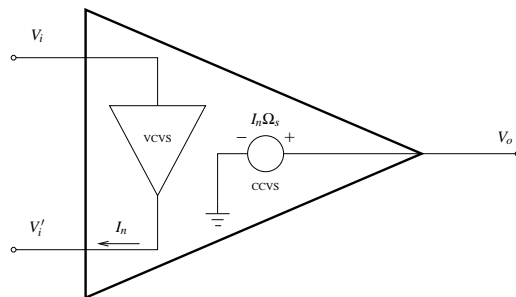


Figure 3: Current Feedback Op-amp model

2 - B.6

**Non-inverting**  
See Figure 4

$$I_n = V_s G_1 + (V_s - V_o) G_F \quad (8)$$

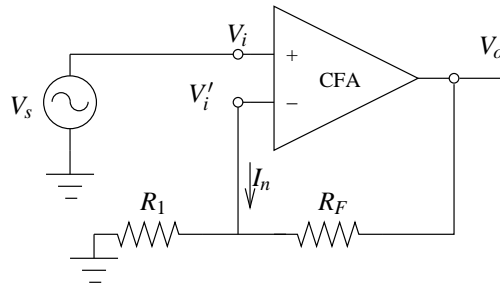


Figure 4: Non-inverting current feedback amplifier

2 - B.7

**Non-inverting**

- Transfer function:

$$V_o/V_s = \frac{(G_1 + G_F)\Omega_o/(1 + G_f\Omega_o)}{s[\tau/(1 + G_F\Omega_o)] + 1} \quad (9)$$

if we assume that  $G_F\Omega_o \gg 1$

$$V_o/V_s = \frac{1 + R_F/R_1}{s\tau R_F/\Omega_o + 1} \quad (10)$$

- dc gain:

$$A_{vo} = (R_1 + R_F)/R_1 \quad (11)$$

- GBWP:

$$GBWP = \frac{\Omega_o(R_F + R_1)}{2\pi R_F R_1} = \Omega_o A_{vo} / (2\pi\tau R_F) \quad (12)$$

2 - B.8

**Non-inverting Current Feedback Op-amps - Remarks**

- The -3dB frequency is given by

$$f_{3dB} = (\Omega_o + R_f)/(2\pi\tau R_F) \approx \Omega_o/(2\pi\tau R_F) \quad (13)$$

- $f_{3dB}$  is only dependent on  $R_F$ , therefore unlike conventional non-inverting amplifiers, the dc gain is set with only  $R_1$  and holding the  $f_{3dB}$  constant with  $R_F$ .
- High slew rate.
- Not flexible in terms of stability and ability to synthesize transfer functions.

2 - B.9

**Inverting**

See Figure 5

$$I_n = -(V_s G_1 + V_o G_F) \quad (14)$$

Assuming  $\Omega_o G_F \gg 1$

$$V_o/V_s = \frac{-R_F/R_1}{s(\tau R_F/\Omega_o) + 1} \quad (15)$$

2 - B.10

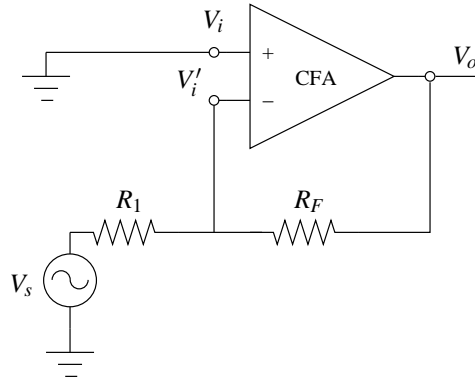


Figure 5: Inverting current feedback amplifier

### Inverting Current Feedback Op-amps - Remarks

- dc gain is  $-R_F/R_1$ .
- -3dB frequency is  $\Omega_o/(2\pi\tau R_F)$ .
- $GBWP$  is  $\Omega_o/(2\pi\tau R_1)$ .
- Avoid applying capacitor directly in a feedback between  $V_o$  and  $V_i'$ .

2 - B.11

### Summary

- Stability is affected by  $R_F$ , therefore caution must be used if different feedback resistance, other than the one specified by the manufacturer is used.
- Inverting input impedance is very high.
- Non-inverting input impedance is very low.
- Stray capacitance on the inverting input or in the feedback connection leads to oscillations.

2 - B.12

## 3 CFA Circuit Examples

### Integrator using $C$ instead of $R_f$

$$I_n = -(V_s G_1 + V_o s C) \quad (16)$$

and

$$V_o/V_s = \frac{-\Omega_o G_1}{s(\tau + C\Omega_o) + 1} \quad (17)$$

If  $R_1 = 1M\Omega$ ,  $C = 1\mu F$  and  $\Omega_o = 10^8\Omega$ , then

$$V_o/V_s = -100/(s100 + 1)$$

which is not an integrator but rather an inverting low-pass filter with a cutoff frequency of  $10^{-2}\text{rad/s}$

2 - B.13

### Integrator

See Figure 6

2 - B.14

### General

See Figure 7

$$V_o/V_s = \frac{Y_1 \Omega_1 G_{o1}}{Y_1 + Y_2 [(1 + \Omega_1 \Omega_2 G_{o1} G_A)/(G_F \Omega_2)]} \quad (18)$$

2 - B.15

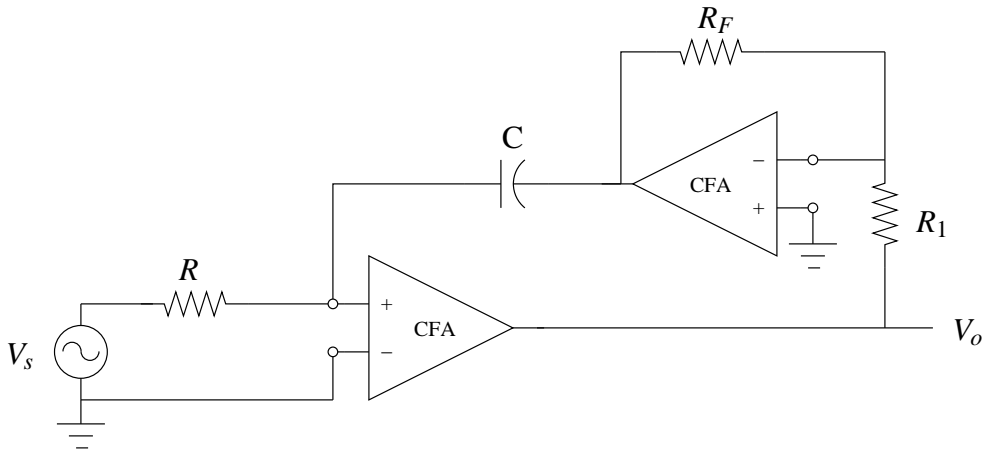


Figure 6: Non-inverting integrator using CFA

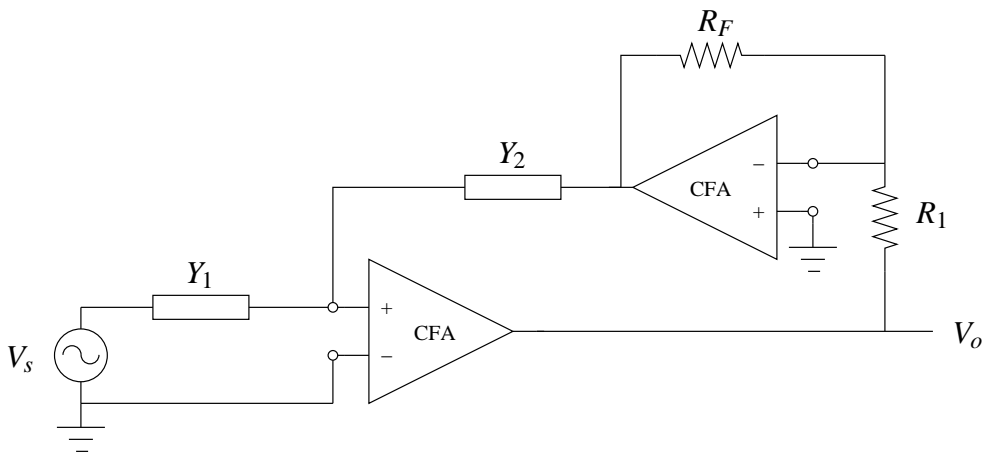


Figure 7: General non-inverting CFA circuit

## 4 Additional References

- Donald A. Neamen, “*Electronic Circuit Analysis and Design*”, Irwin, Chicago, 1996.
- Operational Amplifiers, <http://www-s.ti.com/sc/psheets/slod006b/slod006b.pdf>
- Current Feedback Op-Amp Applications Circuit Guide, <http://www.national.com/an/OA/OA-07.pdf>