

EE 521: Instrumentation and Measurements

Aly El-Osery

Electrical Engineering Department, New Mexico Tech
Socorro, New Mexico, USA

September 13, 2009

1 Integrators and Differentiators

2 Active Filters

- Sallen-Key
- Biquad Active Filters
- Generalized Impedance Converter Active Filters

Integrators

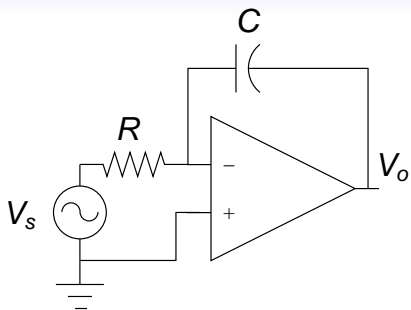


Figure: Integrator

Integrators

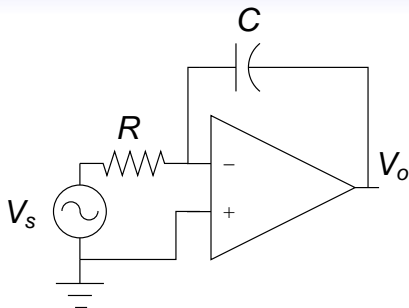


Figure: Integrator

- Drifts if there is dc or average levels in the signal.
- Will also drift due to current biases in the op-amp.

Differentiator

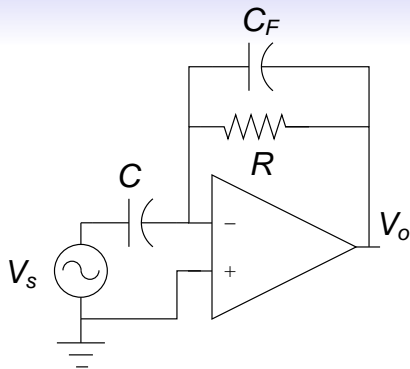


Figure: Practical differentiator

Differentiator

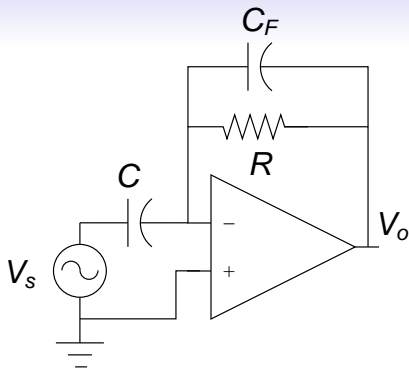


Figure: Practical differentiator

- dc or average levels in the signal and op-amp biases pose no issues.
- High frequency issues.

Common Filter Types

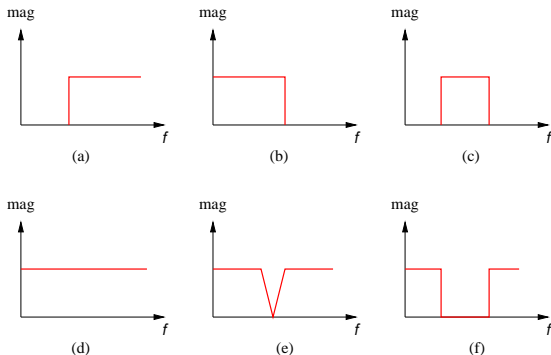


Figure: Sample of ideal filters: (a) lowpass; (b) highpass; (c) bandpass; (d) allpass; (e) notch; (f) bandstop

Active Filters - Generalized Circuit

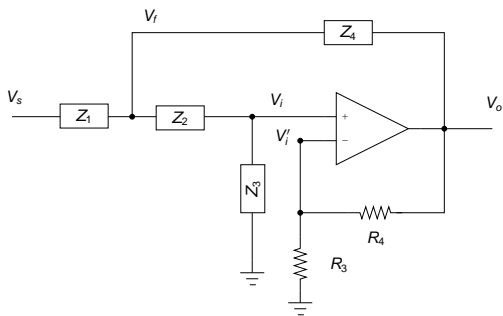


Figure: Generalized Sallen-Key Circuit

Non-Ideal Transfer Function

$$\frac{V_o}{V_s} = \left(\frac{c}{d}\right) \left[\frac{1}{1 + \frac{1}{A_D(f)b} - \frac{d}{b}} \right] \quad (1)$$

where

$$b = \frac{R_3}{R_3 + R_4}$$

$$c = \frac{Z_2 Z_3 Z_4}{Z_2 Z_3 Z_4 + Z_1 Z_2 Z_4 + Z_1 Z_2 Z_3 + Z_2 Z_2 Z_4 + Z_2 Z_2 Z_1}$$

$$d = \frac{Z_1 Z_2 Z_3}{Z_2 Z_3 Z_4 + Z_1 Z_2 Z_4 + Z_1 Z_2 Z_3 + Z_2 Z_2 Z_4 + Z_2 Z_2 Z_1}$$

Ideal Transfer Function

$$\frac{1}{A_D(f)b} \approx 0$$

$$\frac{V_o}{V_s} = \frac{K}{\frac{Z_1 Z_2}{Z_3 Z_4} + \frac{Z_1}{Z_3} + \frac{Z_2}{Z_3} + \frac{Z_1(1-K)}{Z_4} + 1} \quad (2)$$

where

$$K = \frac{R_3 + R_4}{R_3} \quad (3)$$

Quadratic Form

$$s^2/\omega_n^2 + s2\zeta/\omega_n + 1$$

where ω_n is the natural frequency and ζ is the damping factor.
Also, $Q = 1/(2\zeta)$.

Low-Pass Filter

$$Z_1 = R_1, \quad Z_2 = R_2, \quad Z_3 = \frac{1}{sC_1}, \quad Z_4 = \frac{1}{sC_2}, \quad K = 1 + \frac{R_4}{R_3} \quad (4)$$

$$\frac{V_o}{V_s} = \frac{K}{s^2(R_1R_2C_1C_2) + s(R_1C_1 + R_2C_1 + R_1C_2(1 - K)) + 1} \quad (5)$$

let

$$\omega_n^2 = \frac{1}{R_1R_2C_1C_2}, \quad \zeta^2 = \frac{R_1R_2C_1C_2}{(R_1C_1 + R_2C_1 + R_1C_2(1 - K))^2}$$

High-Pass Filter

$$Z_1 = \frac{1}{sC_1}, \quad Z_2 = \frac{1}{sC_2}, \quad Z_3 = R_1, \quad Z_4 = R_2, \quad K = 1 + \frac{R_4}{R_3} \quad (6)$$

$$\frac{V_o}{V_s} = \frac{K(s^2(R_1 R_2 C_1 C_2))}{s^2(R_1 R_2 C_1 C_2) + s(R_2 C_2 + R_2 C_1 + R_1 C_2(1 - K)) + 1} \quad (7)$$

let

$$\omega_n^2 = \frac{1}{R_1 R_2 C_1 C_2}, \quad \zeta^2 = \frac{R_1 R_2 C_1 C_2}{(R_2 C_2 + R_2 C_1 + R_1 C_2(1 - K))^2}$$

Bandpass Filter

$$Z_1 = R_1, \quad Z_2 = \frac{1}{sC_1}, \quad Z_3 = R_2, \quad Z_4 = R_3 \parallel C_2, \quad K = 1 + \frac{R_4}{R_3} \quad (8)$$

Biquad Active Filter

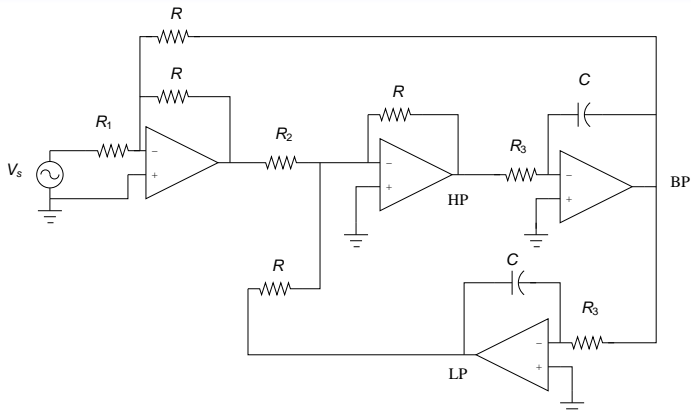


Figure: Biquad Active Filter

Notch filter

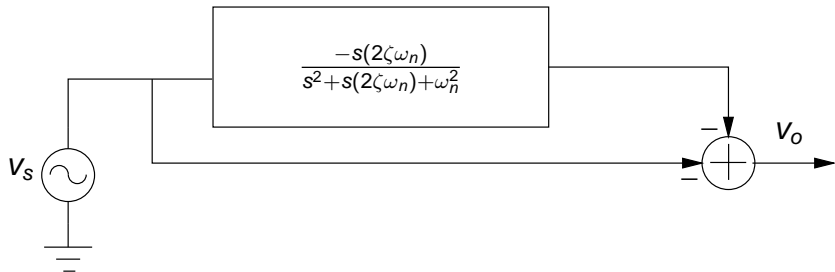


Figure: Biquad notch filter

Biquad notch filter

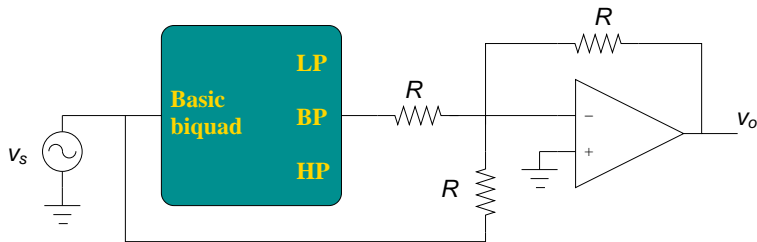


Figure: Biquad notch filter

where $R_1 = R$.

Biquad allpass filter

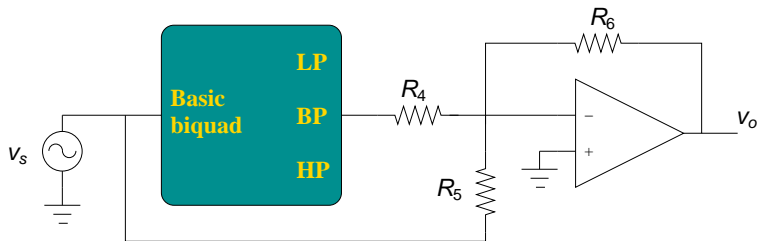


Figure: Biquad allpass filter

where $R_1 = R$, $R_5 = 2R_4$, and $R_6 = R_5$.

Generalized Impedance Converter (GIC)

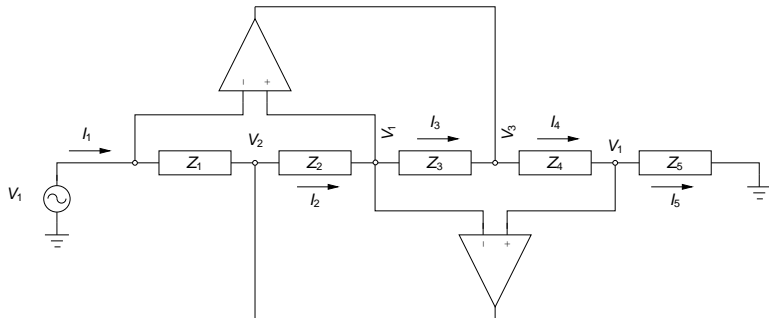


Figure: Generalized Sallen-Key Circuit

GIC driving point impedance

$$Z_{11}(s) = V_1/I_1 = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4} \quad (9)$$

- If $Z_2 = 1/(sC_2)$ and the rest of the Z s are resistors

$$Z_{11} = s(C_2 R_1 R_3 / R_4) \quad (10)$$

where the equivalent inductance is given by

$$L_{eq} = C_2 R_1 R_3 / R_4 \quad (11)$$

- If Z_1 and Z_5 are made capacitors, then

$$Z_{11} = -1/(Ds^2) \quad (12)$$

where the D element is

$$D = C_1 C_5 R_2 R_4 / R_3 \quad (13)$$

Filter examples using GIC

- Bandpass filter

$$V_o/V_s = \frac{sL_{eq}/R}{s^2 C I_{eq} + (sL_{eq}/R) + 1} \quad (14)$$

- Low-pass filter

$$V_o/V_s = \frac{1}{s^2 R D + s R C + 1} \quad (15)$$

Bandpass Filter

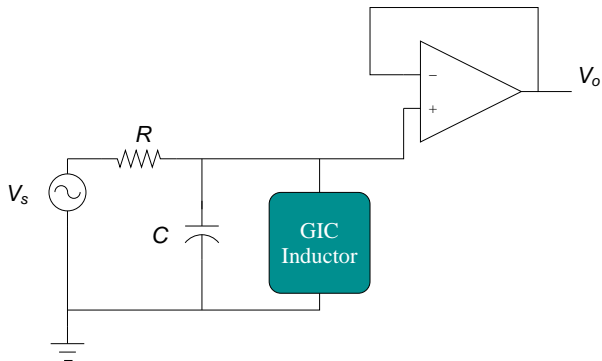


Figure: Bandpass filter using GIC

Low-pass Filter

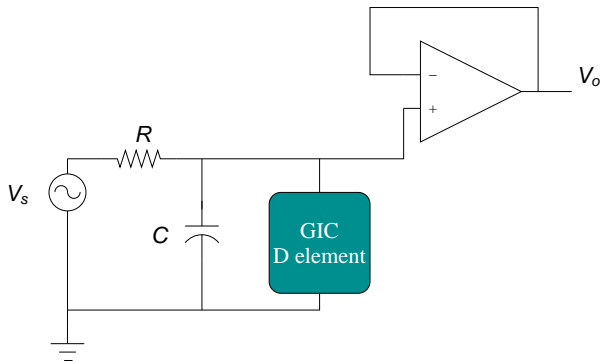


Figure: Lowpass filter using GIC