

# Lecture 2 - F

## Analog Signal Conditioning

EE 521: Instrumentation and Measurements

Lecture Notes Update on October 5, 2009

Aly El-Osery, Electrical Engineering Dept., New Mexico Tech

2 - F.1

### Contents

<b>1 Bridge Circuits</b>	<b>1</b>
<b>2 Wheatstone Bridge</b>	<b>1</b>
<b>3 Constant-Current Bridge</b>	<b>3</b>
<b>4 Linearized Bridge</b>	<b>3</b>
<b>5 Half Bridge</b>	<b>4</b>

2 - F.2

## 1 Bridge Circuits

### Bridge Circuits

Used for a variety of applications including measuring change in resistance, change in inductance, change in capacitance, etc.

#### Basic measuring methods

- bridge balance method, and
- imbalance output method.

2 - F.3

## 2 Wheatstone Bridge

### Constant-Voltage Resistance Bridge

See Figure 1.

2 - F.4

$$\begin{aligned}v_o &= v_A - v_B \\ &= \frac{R_1 v_{ref}}{R_1 + R_2} - \frac{R_3 v_{ref}}{R_3 + R_4} \\ &= \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} v_{ref}\end{aligned}\quad (1)$$

2 - F.5

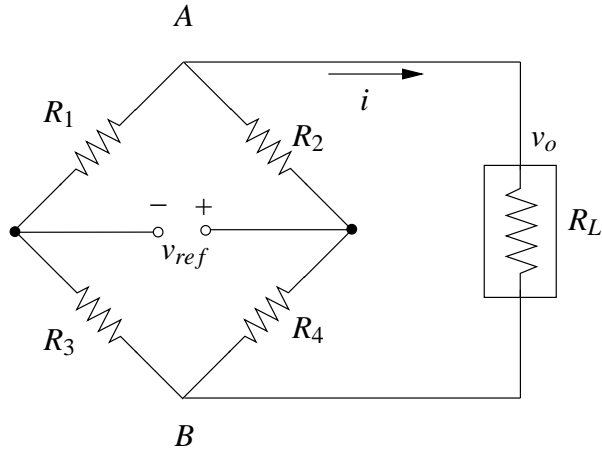


Figure 1: Wheatstone bridge (constant voltage resistance bridge)

For balanced bridge

$$\begin{aligned}
 v_o &= v_A - v_B \\
 &= \frac{R_1 v_{ref}}{R_1 + R_2} - \frac{R_3 v_{ref}}{R_3 + R_4} \\
 &= \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} v_{ref} = 0
 \end{aligned} \tag{2}$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \tag{3}$$

2 - F.6

Measuring change in voltage

Assuming  $R_1 = R_2 = R_3 = R_4 = R$ , then if there is a slight change in the resistance of  $R_1 = R + \delta R$ ,

$$\delta v_o = \frac{R(R + \delta R) - R^2}{(2R + \delta R)(2R)} v_{ref} \tag{4}$$

non-linear

$$\frac{\delta v_o}{v_{ref}} = \frac{\delta R/R}{4 + 2\delta R/R} \tag{5}$$

linearized assuming  $\delta R/R$  is small

$$\frac{\delta v_o}{v_{ref}} = \frac{\delta R}{4R} \tag{6}$$

2 - F.7

Linearization Error

$$N_P = \left( 1 - \frac{\text{linearized}}{\text{actual}} \right) \times 100 \tag{7}$$

for Wheatstone bridge

$$N_P = \frac{1}{2} \frac{\delta R}{R} \times 100 \tag{8}$$

2 - F.8

### 3 Constant-Current Bridge

#### Constant-Current Resistance Bridge

See Figure 2.

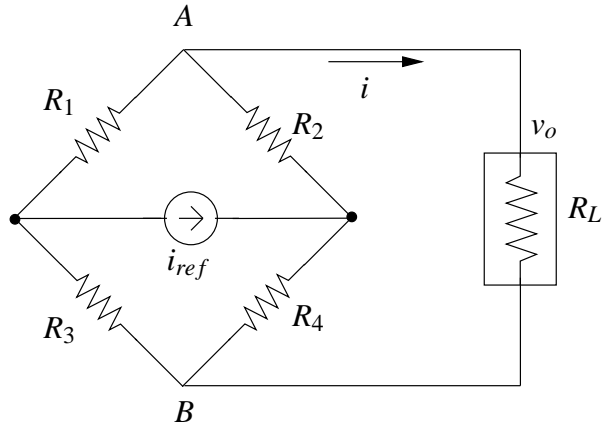


Figure 2: Constant-current resistance bridge

2 - F.9

$$i_{ref} = \frac{v_{ref}}{R_1 + R_2} + \frac{v_{ref}}{R_3 + R_4} \quad (9)$$

therefore,

$$v_{ref} = \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4} \quad (10)$$

and

$$v_o = \frac{R_1 R_4 - R_2 R_3}{R_1 + R_2 + R_3 + R_4} i_{ref} \quad (11)$$

2 - F.10

#### For balanced bridge

Assuming  $R_1 = R_2 = R_3 = R_4 = R$ , then if there is a slight change in the resistance of  $R_1 = R + \delta R$ ,

$$\frac{\delta v_o}{R i_{ref}} = \frac{\delta R / R}{4 + \delta R / R} \quad (12)$$

**linearized assuming  $\delta R / R$  is small**

$$\frac{\delta v_o}{R i_{ref}} = \frac{\delta R}{4R} \quad (13)$$

2 - F.11

#### Linearization Error

**for constant current bridge**

$$N_P = \frac{1}{4} \frac{\delta R}{R} \times 100 \quad (14)$$

2 - F.12

### 4 Linearized Bridge

#### Hardware Linearized Bridge

See Figure 3.

2 - F.13

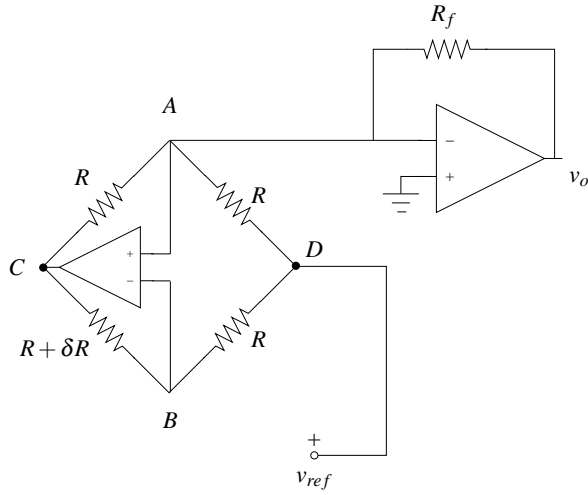


Figure 3: Linearized bridge

Writing the current summation at nodes  $A$  and  $B$ , respectively,

$$\frac{v}{R} + \frac{v_{ref}}{R} + \frac{v_o}{R_f} = 0 \quad (15)$$

$$\frac{v_{ref}}{R} + \frac{v}{R + \delta R} = 0 \quad (16)$$

then,

$$\frac{\delta v_o}{v_{ref}} = \frac{R_f \delta R}{R^2} \quad (17)$$

## 5 Half Bridge

### Half Bridge

See Figure 4.

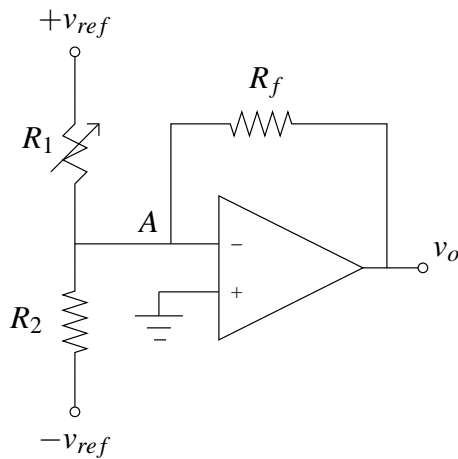


Figure 4: Half bridge

$$v_o = R_f \left( \frac{1}{R_2} - \frac{1}{R_1} \right) \quad (18)$$

Assuming  $R_1 = R_2 = R$ , then if there is a slight change in the resistance of  $R_1 = R + \delta R$ ,

**non-linear equation**

$$\frac{\delta v_o}{v_{ref}} = \frac{R_f}{R} \frac{\delta R/R}{1 + \delta R/R} \quad (19)$$

**Linearization error**

$$N_P = \frac{\delta R}{R} \times 100 \quad (20)$$