

EE 521: Instrumentation and Measurements

Aly El-Osery

Electrical Engineering Department, New Mexico Tech
Socorro, New Mexico, USA

October 5, 2009

- 1 **Bridge Circuits**
- 2 **Wheatstone Bridge**
- 3 **Constant-Current Bridge**
- 4 **Linearized Bridge**
- 5 **Half Bridge**

Bridge Circuits

Used for a variety of applications including measuring change in resistance, change in inductance, change in capacitance, etc.

Bridge Circuits

Used for a variety of applications including measuring change in resistance, change in inductance, change in capacitance, etc.

Basic measuring methods

- bridge balance method, and
- imbalance output method.

Constant-Voltage Resistance Bridge

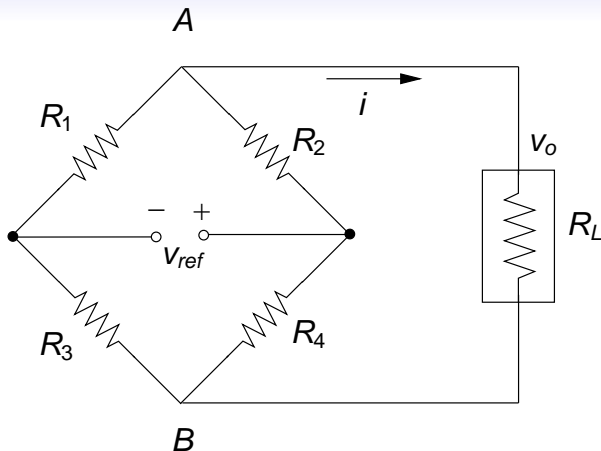


Figure: Wheatstone bridge (constant voltage resistance bridge)

$$\begin{aligned}V_o &= V_A - V_B \\&= \frac{R_1 V_{ref}}{R_1 + R_2} - \frac{R_3 V_{ref}}{R_3 + R_4} \\&= \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} V_{ref}\end{aligned}\tag{1}$$

For balanced bridge

$$\begin{aligned}V_o &= V_A - V_B \\&= \frac{R_1 V_{ref}}{R_1 + R_2} - \frac{R_3 V_{ref}}{R_3 + R_4} \\&= \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} V_{ref} = 0\end{aligned}\tag{2}$$

For balanced bridge

$$\begin{aligned}V_o &= V_A - V_B \\&= \frac{R_1 V_{ref}}{R_1 + R_2} - \frac{R_3 V_{ref}}{R_3 + R_4} \\&= \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} V_{ref} = 0\end{aligned}\tag{2}$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}\tag{3}$$

Measuring change in voltage

Assuming $R_1 = R_2 = R_3 = R_4 = R$, then if there is a slight change in the resistance of $R_1 = R + \delta R$,

$$\delta v_o = \frac{R(R + \delta R) - R^2}{(2R + \delta R)(2R)} v_{ref} \quad (4)$$

Measuring change in voltage

Assuming $R_1 = R_2 = R_3 = R_4 = R$, then if there is a slight change in the resistance of $R_1 = R + \delta R$,

$$\delta v_o = \frac{R(R + \delta R) - R^2}{(2R + \delta R)(2R)} v_{ref} \quad (4)$$

non-linear

$$\frac{\delta v_o}{v_{ref}} = \frac{\delta R/R}{4 + 2\delta R/R} \quad (5)$$

Measuring change in voltage

Assuming $R_1 = R_2 = R_3 = R_4 = R$, then if there is a slight change in the resistance of $R_1 = R + \delta R$,

$$\delta v_o = \frac{R(R + \delta R) - R^2}{(2R + \delta R)(2R)} v_{ref} \quad (4)$$

non-linear

$$\frac{\delta v_o}{v_{ref}} = \frac{\delta R/R}{4 + 2\delta R/R} \quad (5)$$

linearized assuming $\delta R/R$ is small

$$\frac{\delta v_o}{v_{ref}} = \frac{\delta R}{4R} \quad (6)$$

Linearization Error

$$N_P = \left(1 - \frac{\textit{linearized}}{\textit{actual}} \right) \times 100 \quad (7)$$

Linearization Error

$$N_P = \left(1 - \frac{\textit{linearized}}{\textit{actual}} \right) \times 100 \quad (7)$$

for Wheatstone bridge

$$N_P = \frac{1}{2} \frac{\delta R}{R} \times 100 \quad (8)$$

Constant-Current Resistance Bridge

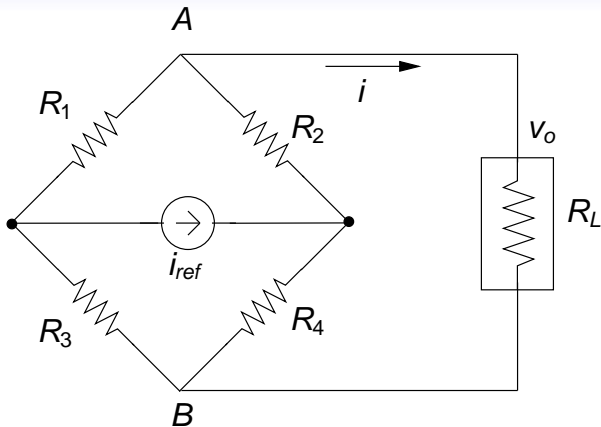


Figure: Constant-current resistance bridge

$$i_{ref} = \frac{V_{ref}}{R_1 + R_2} + \frac{V_{ref}}{R_3 + R_4} \quad (9)$$

therefore,

$$V_{ref} = \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4} \quad (10)$$

and

$$V_o = \frac{R_1 R_4 - R_2 R_3}{R_1 + R_2 + R_3 + R_4} i_{ref} \quad (11)$$

For balanced bridge

Assuming $R_1 = R_2 = R_3 = R_4 = R$, then if there is a slight change in the resistance of $R_1 = R + \delta R$,

$$\frac{\delta v_o}{R i_{ref}} = \frac{\delta R/R}{4 + \delta R/R} \quad (12)$$

For balanced bridge

Assuming $R_1 = R_2 = R_3 = R_4 = R$, then if there is a slight change in the resistance of $R_1 = R + \delta R$,

$$\frac{\delta v_o}{R i_{ref}} = \frac{\delta R/R}{4 + \delta R/R} \quad (12)$$

linearized assuming $\delta R/R$ is small

$$\frac{\delta v_o}{R i_{ref}} = \frac{\delta R}{4R} \quad (13)$$

Linearization Error

for constant current bridge

$$N_P = \frac{1}{4} \frac{\delta R}{R} \times 100 \quad (14)$$

Hardware Linearized Bridge

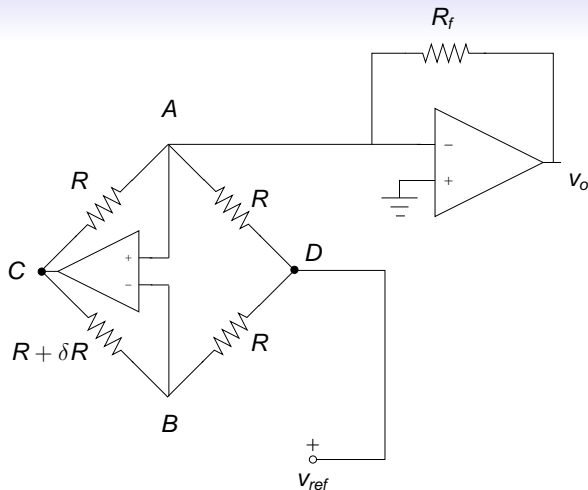


Figure: Linearized bridge

Writing the current summation at nodes A and B , respectively,

$$\frac{V}{R} + \frac{V_{ref}}{R} + \frac{V_o}{R_f} = 0 \quad (15)$$

$$\frac{V_{ref}}{R} + \frac{V}{R + \delta R} = 0 \quad (16)$$

then,

$$\frac{\delta V_o}{V_{ref}} = \frac{R_f \delta R}{R^2} \quad (17)$$

Half Bridge

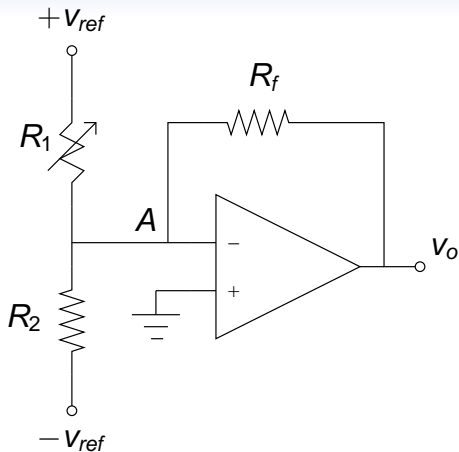


Figure: Half bridge

$$v_o = R_f \left(\frac{1}{R_2} - \frac{1}{R_1} \right) \quad (18)$$

$$v_o = R_f \left(\frac{1}{R_2} - \frac{1}{R_1} \right) \quad (18)$$

Assuming $R_1 = R_2 = R$, then if there is a slight change in the resistance of $R_1 = R + \delta R$,

non-linear equation

$$\frac{\delta v_o}{v_{ref}} = \frac{R_f}{R} \frac{\delta R/R}{1 + \delta R/R} \quad (19)$$

$$v_o = R_f \left(\frac{1}{R_2} - \frac{1}{R_1} \right) \quad (18)$$

Assuming $R_1 = R_2 = R$, then if there is a slight change in the resistance of $R_1 = R + \delta R$,

non-linear equation

$$\frac{\delta v_o}{v_{ref}} = \frac{R_f}{R} \frac{\delta R/R}{1 + \delta R/R} \quad (19)$$

Linearization error

$$N_P = \frac{\delta R}{R} \times 100 \quad (20)$$