

EE 521: Instrumentation and Measurements

Aly El-Osery

Electrical Engineering Department, New Mexico Tech
Socorro, New Mexico, USA

October 5, 2009

- 1 **Impedance Bridge Circuits**
- 2 **Linearizing Devices**
- 3 **Phase Shifter**

General Circuit

Bridge is excited by an ac supply.

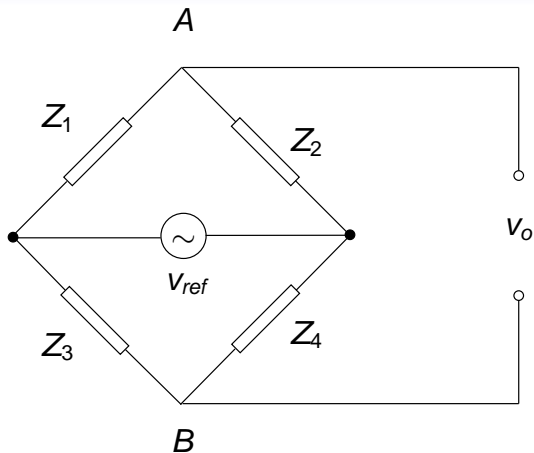


Figure: General impedance bridge

Impedance-bridge output

$$V_o(\omega) = \frac{Z_1 Z_4 - Z_2 Z_3}{(Z_1 + Z_2)(Z_3 + Z_4)} V_{ref}(\omega) \quad (1)$$

Balanced if

$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4} \quad (2)$$

Owen Bridge

See Figure 1. If $Z_1 = C_1$, $Z_2 = R_2$, $Z_3 = R_3 + C_3$, $Z_4 = R_4 + L_4$. We can measure both inductance L_4 and capacitance C_3 using balanced bridge method, i.e.,

$$\frac{1}{j\omega C_1}(R_4 + j\omega L_4) = R_2 \left(R_3 + \frac{1}{j\omega C_3} \right) \quad (3)$$

Equating real parts:

$$\frac{L_4}{C_1} = R_2 R_3 \quad (4)$$

Equating imaginary parts:

$$\frac{R_4}{C_1} = \frac{R_2}{C_3} \quad (5)$$

Measuring L_4 and C_3

By solving the previous two equations for L_4 and C_3

$$L_4 = C_1 R_2 R_3 \quad (6)$$

and

$$C_3 = C_1 \frac{R_2}{R_4} \quad (7)$$

Wien-Bridge Oscillator

See Figure 1. If $Z_1=R_1$, $Z_2 = R_2$, $Z_3 = R_3 + C_3$, $Z_4 = R_4 || C_4$.
We can measure both inductance L_4 and capacitance C_3 using balanced bridge method, i.e.,

$$\frac{R_1}{R_2} = \left(R_3 + \frac{1}{j\omega C_4} \right) \left(\frac{1}{R_4} + j\omega C_4 \right) \quad (8)$$

Equating real parts:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} + \frac{C_4}{C_3} \quad (9)$$

Equating imaginary parts:

$$0 = \omega C_4 R_3 - \frac{1}{\omega C_3 R_4} \Rightarrow \omega = \frac{1}{\sqrt{C_3 C_4 R_3 R_4}} \quad (10)$$

Linearizing Methods

- Digital software,
- digital hardware, or
- analog circuitry.

Offsetting Circuit

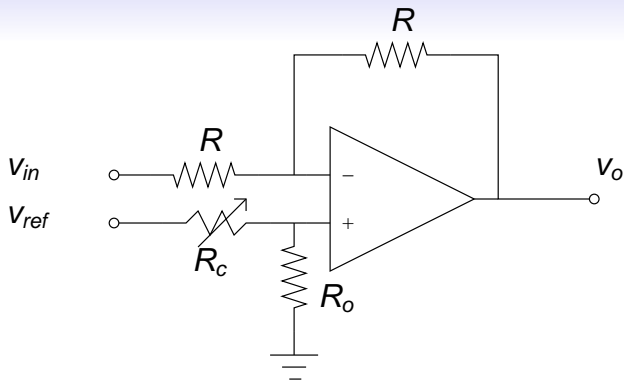


Figure: Offset Compensation

$$V_o = -V_i + \frac{2R_o}{R_o + R_c} V_{ref} \quad (11)$$

Proportional Output Circuit

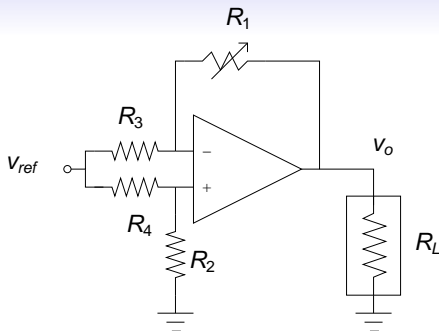


Figure: Proportional output circuit

Assuming $R_1 = R_2 = R_3 = R_4 = R$,

$$\frac{\delta V_o}{V_{ref}} = -\frac{1}{2} \frac{\delta R}{R} \quad (12)$$

Curve Shaping

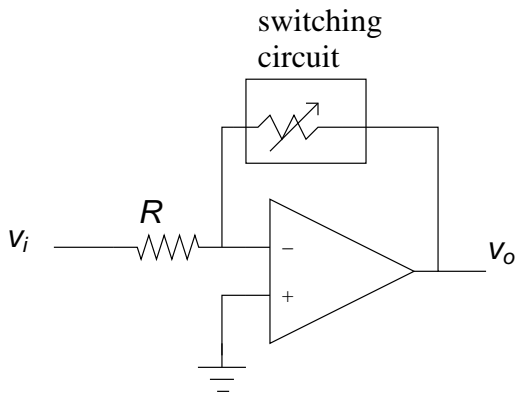


Figure: Curve shaping using resistance switching circuit

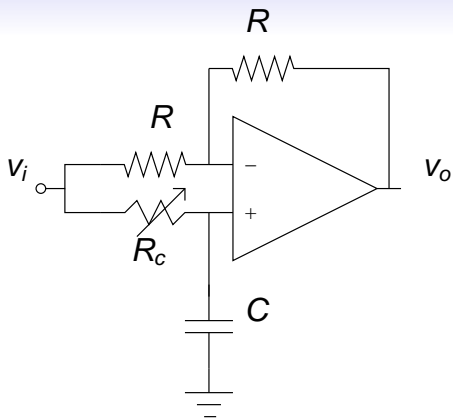


Figure: Simple phase shifter