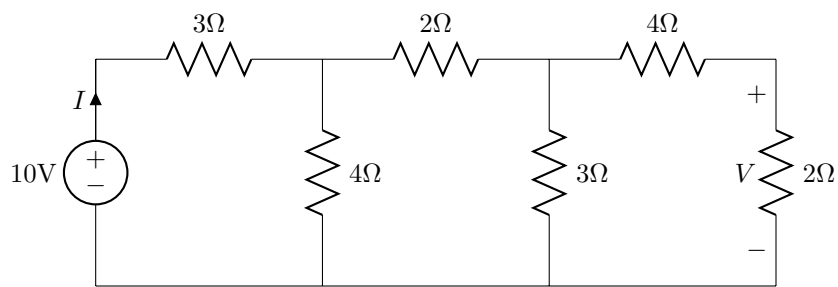



**Important Remarks**

- Homework is due on Sept. 13th, 2011 at the beginning of class
- **For all problems, keeping your work in fractions will produce easier, more accurate results.**
- Start early and get help if you need it
- Start a new page per problem
- Show all the work
- Specify all the units
- Circle your answers
- Staple pages


1. Given figure below, find  $I$  and  $V$  using circuit reduction and other techniques.



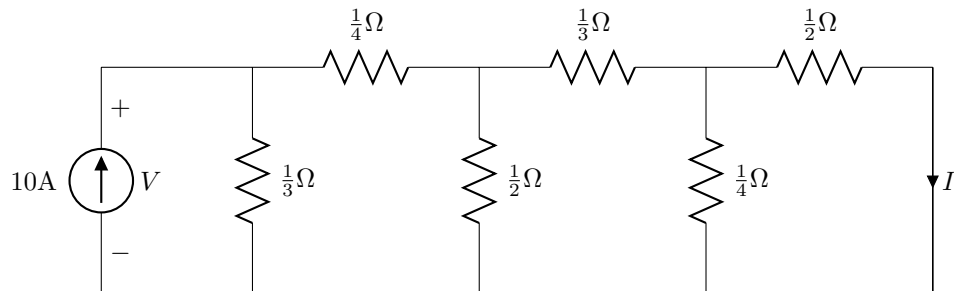
2. Given the figure below, find  $I$  and  $V$  using circuit reduction and other techniques.



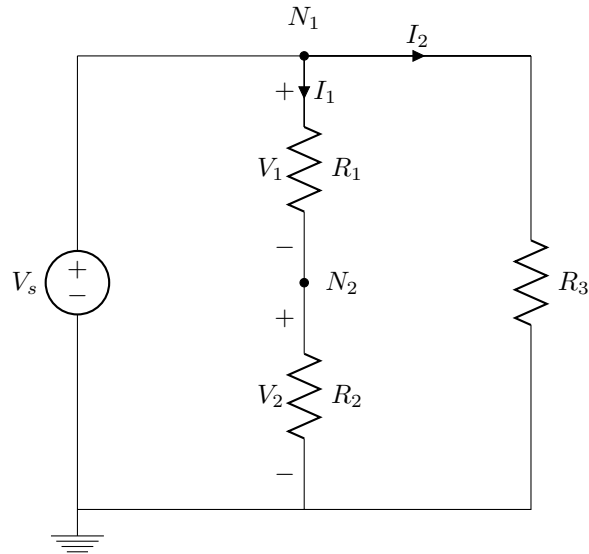
3. Given the figure below,  $V_s = 5\text{V}$ ,  $R_1 = 375\Omega$ ,  $R_3 = 25\Omega$ . With a multimeter we measure  $1.25\text{V}$  at  $N_2$  with respect to ground. Find the voltage at  $N_1$  (w.r.t. Gnd),  $R_2$ ,  $V_1$ ,  $I_1$ , and  $I_2$  using nodal analysis and other techniques.



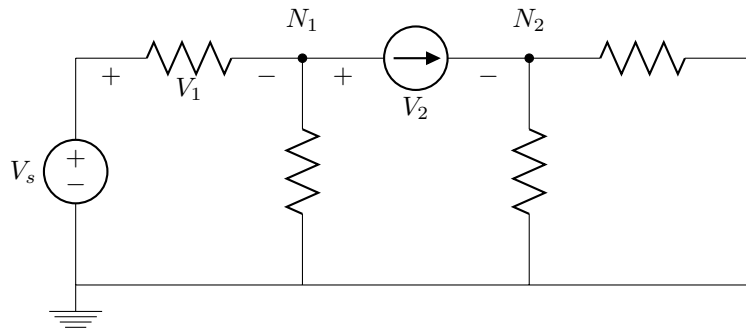
4. Given the figure below,  $V_s = 10\text{V}$ . With a multimeter we measure (w.r.t. Gnd)  $4\text{V}$  at  $N_1$  and  $7\text{V}$  at  $N_2$ . Find  $V_1$  and  $V_2$ .



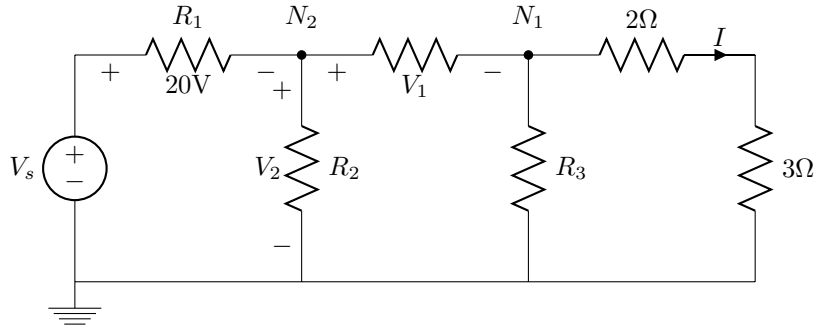
5. In the figure below,  $I = 8A$ . With a multimeter we measure (w.r.t. Gnd) 60V at  $N_2$ . Using nodal analysis and other techniques, find  $V_s$ ,  $V_1$ ,  $V_2$ , and the measurement we would expect to get at  $N_1$  (w.r.t. Gnd).



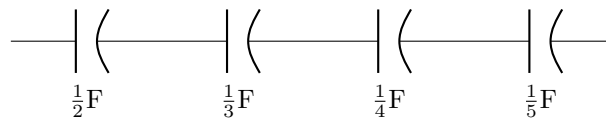
6. The figure below shows a number of capacitors connected in series. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ .



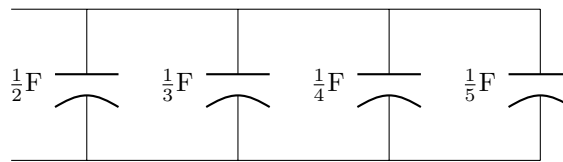7. The figure shows a number of capacitors connected in parallel. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ .



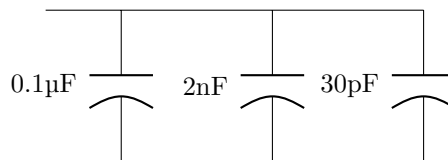8. The figure below shows a number of capacitors connected in parallel. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ . **Don't round off your answer.**



9. The figure below shows a number of capacitors connected in series. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ .

