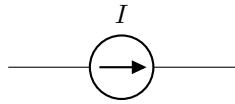


## Current Source




Fixed current,  $I$ , in that branch.

## Resistor and Capacitor Networks

### Resistors in Series




### Resistors in Parallel

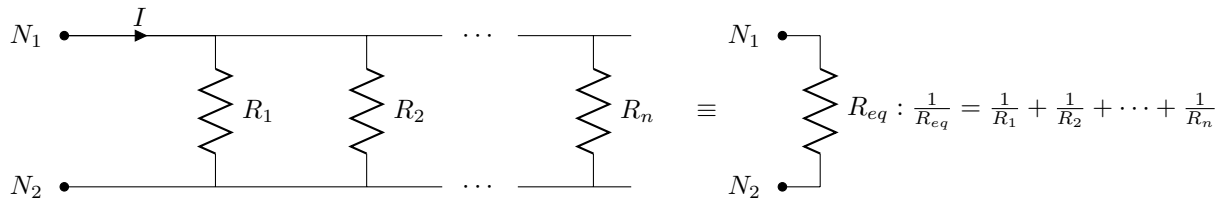

For two resistors in parallel

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

### Capacitors in Series

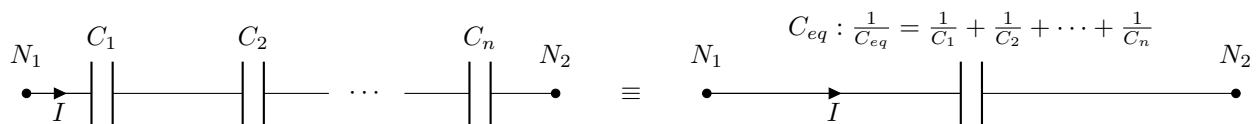

### Capacitors in Parallel

