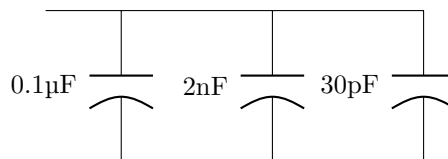



**Important Remarks**

- Homework is due on Sept. 17th, 2013 at the beginning of class
- **For all problems, keeping your work in fractions will produce easier, more accurate results.**
- Start early and get help if you need it
- Start a new page per problem
- Show all the work
- Specify all the units
- Circle your answers
- Staple pages

1. The figure below shows a number of capacitors connected in parallel. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ . **Don't round off your answer.**



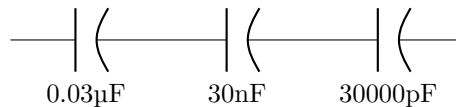2. The figure below shows a number of capacitors connected in series. Redraw this circuit as a single capacitor equivalent to this combination, and calculate its value  $C_{eq}$ .



3. For the circuit shown in Figure 1, assume  $V_s = 5V$  and  $R$  is unknown. In the lab we observe the charge curve for this circuit on an oscilloscope. We measure the following:

$$\begin{aligned} V_C &= 0.5V & \text{when } t &= 50\mu\text{s} \\ V_C &= 4.5V & \text{when } t &= 1150\mu\text{s} \end{aligned}$$

- (a) Using the 10% - 90% rise time rule of thumb, calculate the time constant  $\tau$  for this circuit.
- (b) Using your results from part a, determine the value of  $R$ .
- (c) Assume the switch has been in position  $A$  for a long time and switches to  $B$  at  $t = 0$ . Plot  $V_C$  for  $0 < t < 4\tau$  using at least four points. Show all your work! Be sure to plot and confirm that your 10% values and 90% values match those used earlier. (Remember that the rule of thumb for the earlier calculation is an approximation).
- (d) Assume the switch has been in position  $B$  for a long time and switches to  $A$  at  $t = 0$ . Plot  $V_C$  for  $0 < t < 4\tau$  using at least four points. Show all your work! Be sure to plot and confirm that your 10% values and 90% values match those used earlier. (Remember that the rule of thumb for the earlier calculation is an approximation).

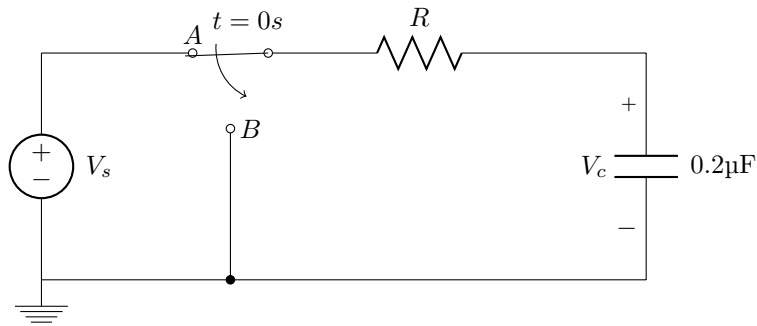


Figure 1: Circuit for problem 3

4. For the circuit shown in Figure 2:  $\tau = 2\text{ms}$ ,  $V_s = 15\text{V}$ .

- Determine the value of  $C$ .
- Assume the switch has been in position  $A$  for a long time and switches to  $B$  at  $t = 0$ . Plot  $V_{ceq}$  for  $0 < t < 4\tau$  using at least four points. Show all your work!
- Assume the switch has been in position  $B$  for a long time and switches to  $A$  at  $t = 0$ . Plot  $V_{ceq}$  for  $0 < t < 4\tau$  using at least four points. Show all your work!

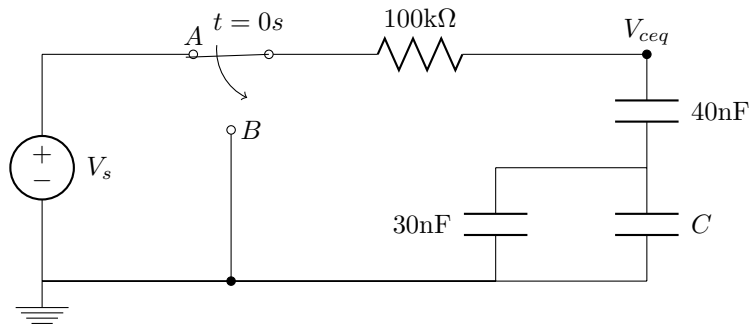


Figure 2: Circuit for problem 4