

**Important Remarks**

- Homework is due on Sept. 24th, 2013 at the beginning of class
- **For all problems, keeping your work in fractions will produce easier, more accurate results.**
- Start early and get help if you need it
- Start a new page per problem
- Show all the work
- Specify all the units
- Circle your answers
- Staple pages

The circuit shown in Figure 1 will be used for problems 1 and 2.

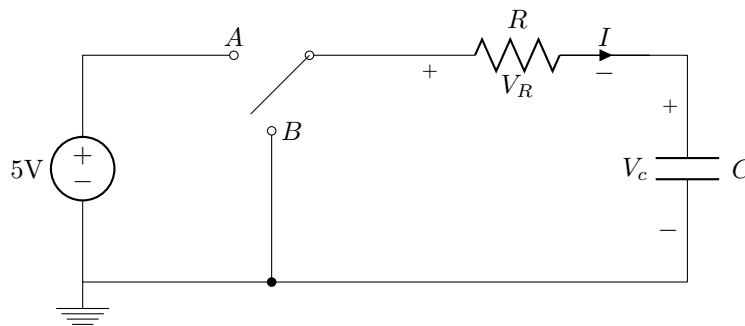


Figure 1:

1. In a simple RC circuit shown in the diagram above, the switch has been in position  $B$  for a long time and switches to  $A$  at  $t = 0$ . We observe a capacitor charging with the standard exponential growth curve. At  $t = 37.5\text{ms}$  we measure the resistor voltage  $V_R$  is  $1.115\text{V}$ . Determine the time constant  $\tau$  for the circuit.
2. For the diagram above, we determine that the time constant  $\tau$  is  $7.00\mu\text{s}$ . We assume that the switch has been in position  $A$  for a long time and moves to position  $B$  at  $t = 0$ . At a particular time after the switch has moved to position  $B$ , we observe that  $I = -9.1\text{mA}$ , and  $V_c = 0.725\text{V}$ .
  - (a) Determine what time these observations occur.
  - (b) Solve for the capacitor value  $C$ .
3. For Figure 2, find the indicated values and express the function  $v(t)$  in equation form:  
Find: Peak voltage  $V_p$ , peak-to-peak voltage  $V_{pp}$ , Period  $T$ , frequency  $f$ , angular frequency  $\omega$ , time shift  $t_{max}$ , and phase angle  $\theta$ .

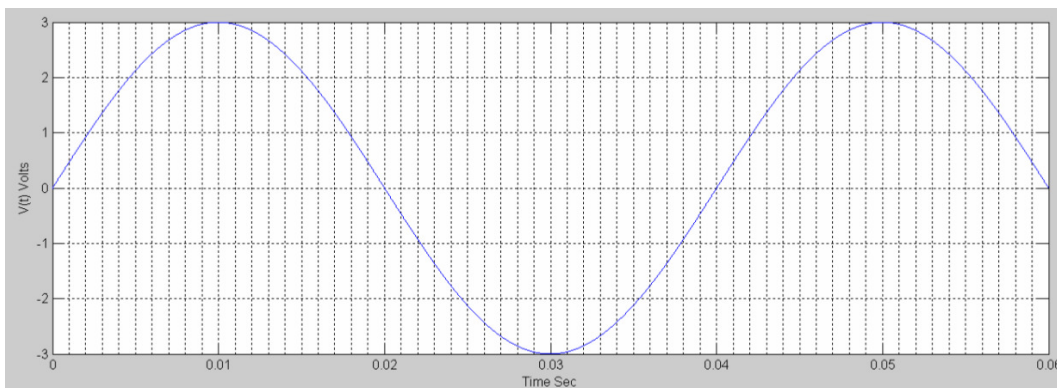


Figure 2:

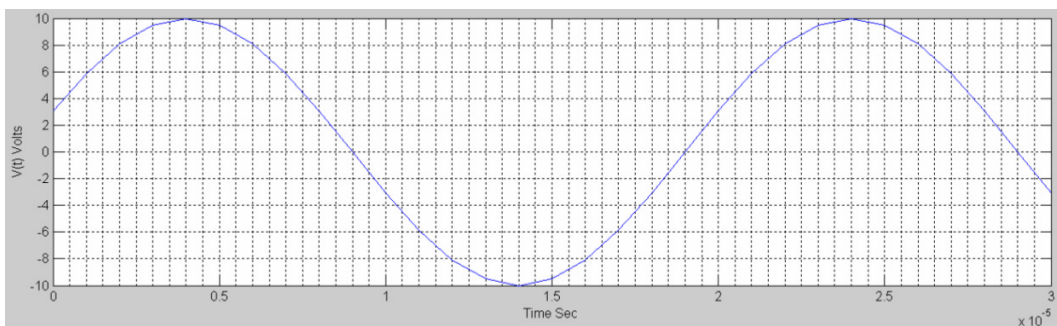


Figure 3:

4. For Figure 3, find the indicated values and express the function  $v(t)$  in equation form (be careful to note that the units for time on this graph are in  $10^{-5}$  seconds).

Find: Peak voltage  $V_p$ , peak-to-peak voltage  $V_{pp}$ , Period  $T$ , frequency  $f$ , angular frequency  $\omega$ , time shift  $t_{max}$ , and phase angle  $\theta$ .

5. For the equation below, find  $V_p$ ,  $V_{pp}$ ,  $T$ ,  $f$ ,  $\omega$ ,  $t_{max}$ ,  $\theta$ ; and graph the function for  $0 < t < 5/16$  seconds. Remember to label you axes, units, and all relevant points on the graph. Hint: Try to keep your time divisions in terms of fractions rather than decimals, this will be easier to graph. This entire problem is easier without a calculator if you use fractions!

$$v(t) = 25 \cos(8\pi t - 30^\circ) \quad (1)$$