

Important Remarks

- Homework is due on August 26th, 2014 at the beginning of class
- Start early and get help if you need it
- Start a new page per problem
- Show all the work
- Specify all the units
- Circle your answers
- Staple pages

Homework Problems:

1. Given the circuit shown in Figure 1 determine the unknown voltage drop V_1

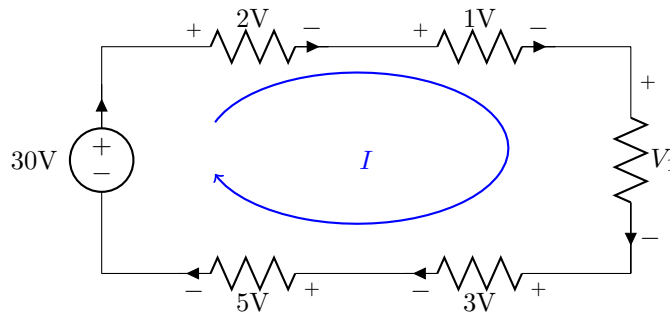


Figure 1: Schematic for Problem 1

2. Given the circuit shown in Figure 2, if $I = 5\text{A}$,
 - (a) determine the voltage drop across, R_1 , R_2 , R_3 and R_4 . Label the voltages on the schematic.
 - (b) Compute the power absorbed by each resistor.
 - (c) Compute the power of the source.
 - (d) Does the total power absorbed by all resistors equal the power of the source.?

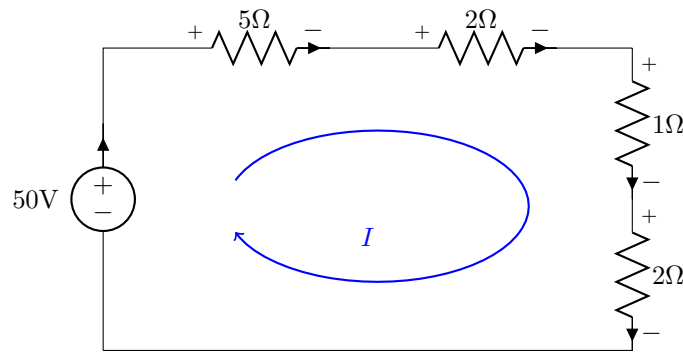


Figure 2: Schematic for Problem 2

3. Given the circuit shown in Figure 3. The circuit element **u** is a mystery component that is consuming 1.5W.
- How many current loops are in the circuit?
 - Draw the current loops in your schematics and label them.
 - Using Ohm's law, Kirchhoff's voltage law and/or Kirchhoff's current law compute the following (*note: some technique may be easier than another*)
 - the voltage across R_1 ,
 - the current through R_2 ,
 - the voltage across R_3 ,
 - the current through the mysterious component **u**, and
 - the resistance of R_4 .
 - Compute the power of each component, indicate whether they consume or provide power, and show that the sum is equal to zero.

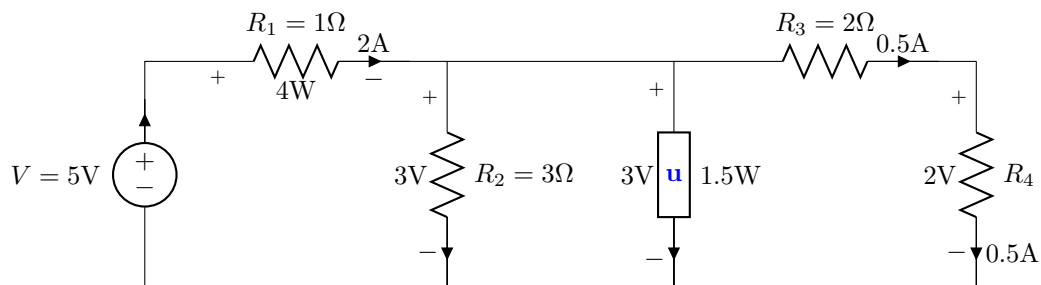


Figure 3: Schematic for Problem 3