

Department of Electrical Engineering  
New Mexico Institute of Mining and Technology

## EE 101: Introduction to Electrical Engineering

Exam 1

Fall 2013

Oct. 1st, 2013

Name: \_\_\_\_\_


Instructor: Aly El-Osery

Answer all questions in the space provided on the question sheets.  
When applicable justify your answers. The problem solving process is more  
important than the answer. Partial credit can be earned.


**Make sure you list all the units**  
**You must show all your work to get full credit.**

1. (15 points)

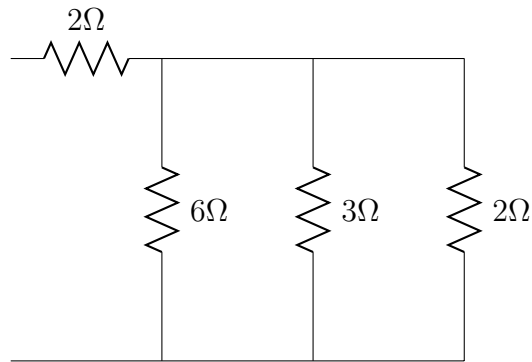
(a) Given the schematic below, find the equivalent resistance



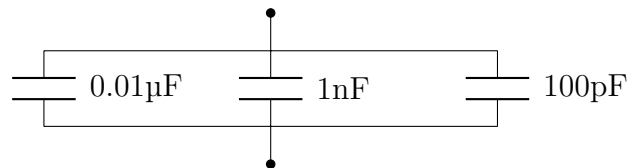(b) Given the schematic below, find the equivalent capacitance




2. (10 points) Given the circuit below

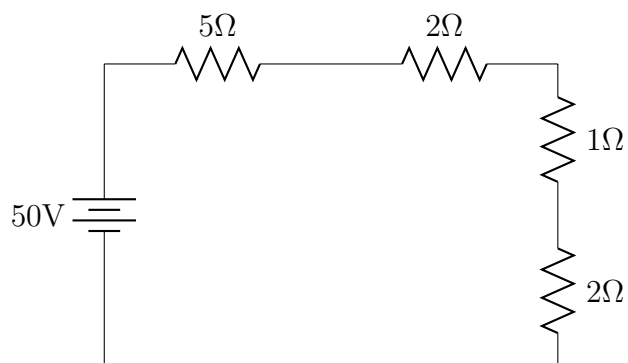


- (a) What is the current in this circuit? (make sure you mark its direction on the circuit).
- (b) Compute the power dissipated by each resistor then perform a power balance.

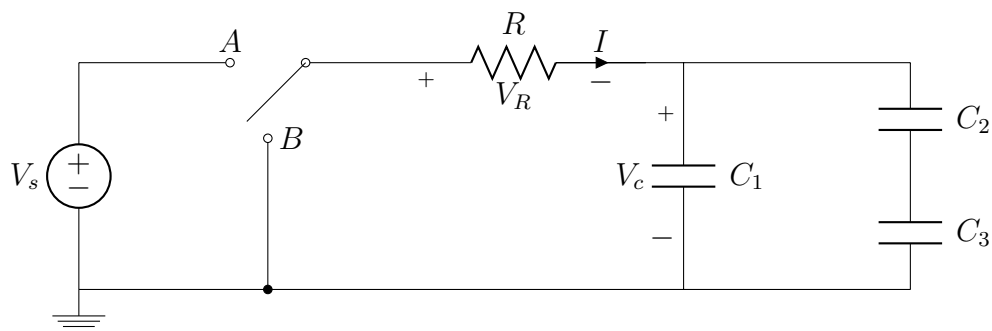3. (25 points) Given the schematic below and assuming the switch was in position  $B$  for a long time.




- (a) Given  $R = 25\text{k}\Omega$ ,  $C_1 = 5\mu\text{F}$  and  $C_2 = C_3 = 10\mu\text{F}$  what is the time constant  $\tau$  of the circuit.

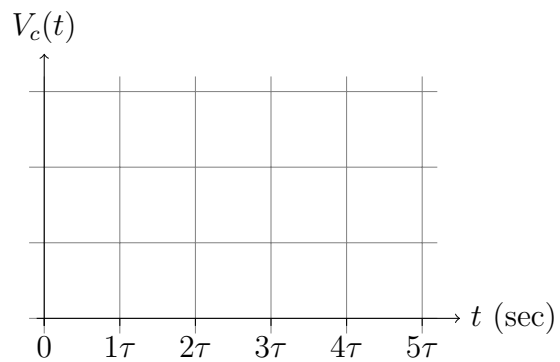- (b) Describe and sketch what happens to  $V_c$  when the switch is turned to position  $A$  at time  $t = 0$ . Write down the equation that describes that behavior.




(Problem 3 continue)

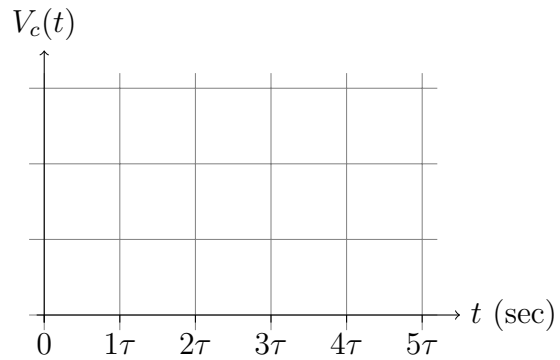- (c) Describe and sketch what happens to  $V_c$  when the switch is turned back to position  $B$  after it has been in position  $A$  for a long time and we reset the time to  $t = 0$ . Write down the equation that describes that behavior.



- (d) Given the situation in part (c) and assuming  $V_s = 1\text{V}$ , compute  $t_{10}$  and at  $t_{90}$  corresponding to 10% and 90% of  $V_s$ , respectively.

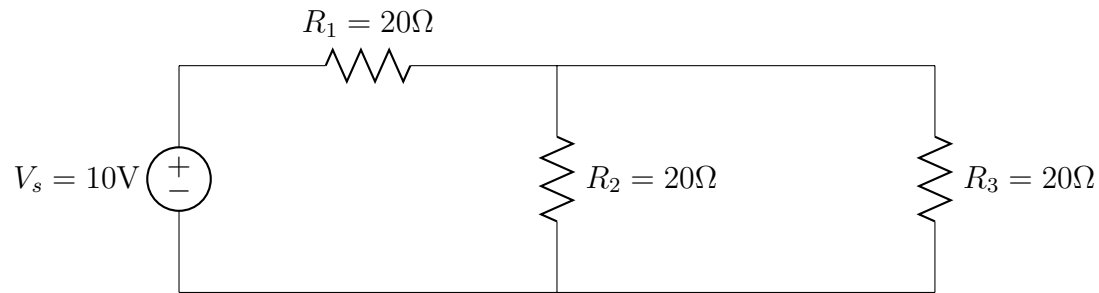4. (20 points) Given the circuit below (**You must put the labels and directions on the schematic.**)



- (a) Label, compute and indicate the direction or polarity of:
1.  $I_s$  supplied by the voltage source.
  2.  $V_1$  across the resistor  $R_1$ .
  3.  $I_2$  through the resistor  $R_2$  and the voltage  $V_2$  across it.
  4.  $I_3$  through the resistor  $R_3$  and the voltage  $V_3$  across it.
- (b) Compute the power balance of the circuit and show conservation of energy