

EE 231L Lab 2**Prelab Part 2**

Design a 2-bit up-down counter using 3 different methods:

1. Use discrete gates and D flip-flops.
2. Write an Verilog text design file which uses a state transition table.
3. Write a Verilog text design file which uses D flip-flops and If-Then statements.