 


---

**EE 231 Lab 2****Decoders and Multiplexers****1.Lab**

1.1. Place a block of 8 DIP switches on your proto-board, Figure 1.



**Figure 1:** Dip Switches

- 1.2. Connect each lead on one side to VCC. You can use an external power or the VCC\_SYS provided on your board.
- 1.3. Put a 1k resistor from each of the leads on the other side to ground. Also on this side, place a row of 8 pin header so that you have the outputs from all of these switches.
- 1.4. In order to be able to connect to the board you will need to assign pins to the proper expansion header on your board. The easiest to use is the GPIO-0 at the top of the board, Figure 2.
- 1.5. Now that the hardware is setup, design the binary coded decimal (BCD)-to-seven-segment decoder and then test it using different inputs from the dip switches.

 


Figure 2: DE0-NANO Development Board

Use Figure 3 for the pin labels for the GPIO-0. Table 2 shows the pins assignments for the GPIO-0.


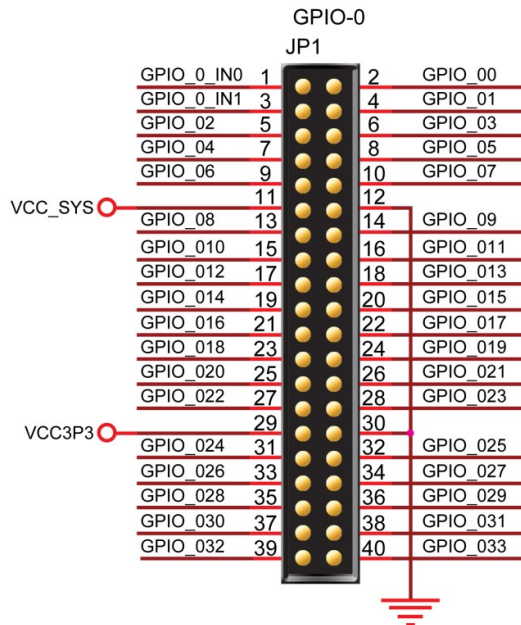


Figure 3: Pin Distribution of the GPIO-0 Expansion header

GPIO-0 Left Column	CPLD Pin #	GPIO-0 Right Column	CPLD Pin #
1	A8	2	D3
3	B8	4	C3
5	A2	6	A3
7	B3	8	B4
9	A4	10	B5
11	--	12	--
13	A5	14	D5
15	B6	16	A6
17	B7	18	D6
19	A7	20	C6
21	C8	22	E6
23	E7	24	D8
25	E8	26	F8
27	F9	28	E9
29	--	30	--
31	C9	32	D9
33	E11	34	E10
35	C11	36	B11
37	A12	38	D11
39	D12	40	B12

**Table 1:** Pin Assignments for GPIO-0

- 1.6. Implement the multiplexer program that you made in the Prelab, as shown in Figure 4. To test the multiplexer we need to hard wire in Verilog RST\_ADDR to 0xFF, PC to the address 0x0A, and MAR to 0x10. Connect IR to the 8 DIP switches, and MEM\_SEL to the 2 push-button switches on the board.

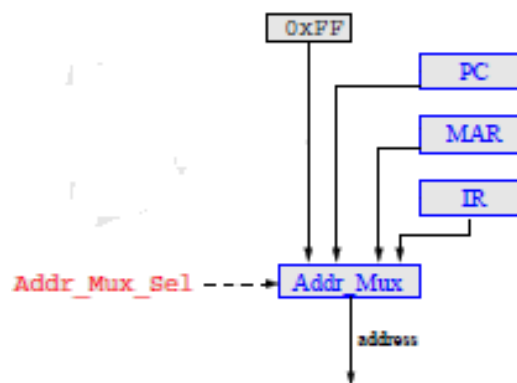

**Figure 4:** Implementation of a Simple Multiplexer

## 2. Supplementary Material

### 2.1. More on Verilog

#### 2.1.1. Logic Levels

•0		Logic zero, false condition
•1		Logic one, true condition
•x		Unknown logic value
•z		High impedance

### 1.1. Verilog – Behavioral Modeling

#### 1.1.1. Always and Reg

1. Behavioral modeling uses the keywords *always*.

2. Target output is a type *reg*. Unlike a wire, *reg* is updated only when a new value is assigned. In other words, it is not continuously updated as wire data types.

3. *Always* may be followed by an event control expression.

4. *Always* is followed by the symbol '@' which is followed by a list of variables. Each time there is a change in those variables, the *always* block is executed.

5. There is no semicolon at the end of the *always* block.

6. The list of variables are separated by logical operator or and not the bitwise OR operator "\_\_\_".

7. Below is an example of an always block:

```
always @(A or B)
...
...
...
```

#### 1.1.1. if-else Statements

if-else statements provide a means for conditional outputs based on the arguments of the if statement.

```
...
output out;
input s, A, B;
reg out;
```

```

...
...
if(s)  out = A;    // if select is 1 then out is A
else   out = B;    // else output is B
...
...

```

### 1.1.2.case Statements

case Statements provide an easy way to represent a multi-branch conditional statement.

1.The first statement that makes a match is executed

2.Unspecified bit patterns should be treated using “default” as the keyword.

#### **Program 1** Four-to-one Line Multiplexer

```

module mux_4x1_example(
    output reg out,
    input [1:0] s,           // select represented by 2 bits
    input in_0, in_1, in_2, in_3);

always @(in_0, in_1, in_2, in_3, s)
    case(s)
        2'b00: out = in_0;    // if s is 00 then output is in_0
        2'b01: out = in_1;    // if s is 01 then output is in_1
        2'b10: out = in_2;    // ...
        2'b11: out = in_3;
    endcase
endmodule

```