

## EE 231 – Homework Chapter 4

**4.10** Derive a minimum-cost realization of the four-variable function that is equal to 1 if exactly two or exactly three of its variables are equal to 1; otherwise it is equal to 0.

**4.12** A circuit with 2 outputs has to implement the following functions

$$f(x_1, \dots, x_4) = \sum m(0,2,4,6,7,9) + D(10,11)$$
$$g(x_1, \dots, x_4) = \sum m(2,4,9,10,15) + D(0,13,14)$$

Design the minimum-cost circuit and compare its cost with combined costs of two circuits that implement  $f$  and  $g$  separately. Assume that the input variables are available in both uncomplemented and complemented forms.

**4.16** Implement the logic circuit in Figure 4.25 using NAND gates only.

**4.20** Find the simplest realization of the function

$f(x_1, \dots, x_4) = \sum m(0,3,4,7,9,10,13,14)$ , assuming that the logic gates have a maximum fan-in of two.

**4.35** Write Verilog code to implement the circuit in Fig 4.25b using the gate level primitives.

**4.38** Write Verilog code to implement the circuit in Figure 4.27c using the continuous assignment.