

Use the diagram of the interface shown below to answer the following questions:

1. Is the IC an input or an output port? Why?
2. Should the data lines of IC be connected to Port A or Port B pins? Explain.
3. For what range of addresses will the IC be selected? Explain.

