

1. Convert the two decimal numbers into signed 8-bit numbers in the following representations. Use 2's complement representation.

Signed Decimal	Binary	Hex
32		
-64		

2. Design a minimum-cost SOP circuit that implements a three-variable majority function.

3. Design the simplest circuit that implements the function $f = A \oplus B \oplus C$ using NOR gates.

4. Perform the following operations involving 8-bits 2's complement numbers, and indicate whether a carry and/or an arithmetic overflow occurs in each case.

$$\begin{array}{r} 0001\ 0101 \\ + 1001\ 1110 \\ \hline \end{array}$$

$$\begin{array}{r} 1110\ 0101 \\ - 1101\ 0110 \\ \hline \end{array}$$

5. Implement the function $f(x_1, x_2) = \sum m(0, 3)$ using a 2-to-4 binary decoder and an OR gate.

6. Implement the function $f(w_1, w_2, w_3) = \overline{w_1} \overline{w_3} + w_1 w_2 + w_1 w_3$ using a 4-to-1 Mux and other gates. Use w_1 and w_2 as selectors.