

1. Simulate the following Verilog programs. Use timing diagrams to show if the D flip-flops are reset **synchronous** -or-**asynchronously**.

a) **module** flipflop (D, Clock, Resetn, Q);
 input D, Clock, Resetn;
 output reg Q;

 always @(negedge Resetn, posedge Clock)
 if (!Resetn)
 Q <= 0;
 else
 Q <= D;


 endmodule

b) **module** flipflop (D, Clock, Resetn, Q);
 input D, Clock, Resetn;
 output reg Q;


 always @(posedge Clock)
 if (!Resetn)
 Q <= 0;
 else
 Q <= D;

 endmodule

 2. Find out how Verilog implements (Mux or Gate) the code below.



(a) Using a multiplexer

 

(b) Clock gating

Figure 5.56 Providing an enable input for a D flip-flop.

```

module rege (D, Clock, Resetn, E, Q);
  input D, Clock, Resetn, E;
  output reg Q;

  always @(posedge Clock, negedge Resetn)
    if (Resetn == 0)
      Q <= 0;
    else if (E)
      Q <= D;

endmodule

```

Figure 5.57 Code for a D flip-flop with enable.