Bounce counter for high-speed detection of switch bouncing

by: Alex Mazarakis (suvervised by William Brooks)

FPGA-based bounce counter for high-speed detection of switch bouncing as prescribed in the lab 6 (week of 2016-10-10 - 2016-10-14).

This code takes advantage of the core generation utility in Xilinx's suite to construct a digital clock multiplier (likely through a phase-locked loop) to boost the onboard clock from 8 MHz to 32 MHz.

The bounce counter itself is implemented as a simple, synchronous edge detector with incrementation.

Adjusting for operation of flip-flop on a single edge of the 32 MHz clock, and Nyquist sampling criterion, the system should be sensitive to bounces of width T = 62.5 ns or greater (F = 16 MHz).

```
"module bounce counter(
       output [7:0] count, //the number of bounces observed
        input switch, //input from the switch
        input clock, //32 Mhz clock
        input rst //sigal to reset the count to 0
);
        reg [8:0] transitions = 9'h4; // times switch transitions states
        reg level; //switch's initial position
        //reset the counter to initial position and check initial level
        always @(negedge clock)
        begin
                 if (rst)
                 begin
                           transitions \leq 9'h0;
                           level <= switch;
                 end else if (level != switch)
                 begin
                           transitions <= transitions + 1;
                           level <= switch;
                 end
        end
       assign count = transitions [8:1]; /** Implicit Division by 2 to account for both edges of a
```

bounce */

endmodule"

The exact wave form is not communicated to the end-user, but a non-zero count of bounces is produced consistent with sampling frequencies of modern microcontrollers.

As a secondary advantage, the FPGA based implementation is polling at 16 MHz (Responsive to 8 MHz or slower signals) making it slightly faster than the logic analyzer's maximum of 5 MHz with a more robust and easily usable interface (e.g. not Acute LA Viewer.)