

Lab 4: Arithmetic Logic Unit (ALU)

Introduction

The heart of every computer is an Arithmetic Logic Unit (ALU). This is the part of the computer which performs arithmetic operations on numbers, e.g. addition, subtraction, etc. In this lab use the Verilog language to implement an ALU having 10 functions. Use of the case structure will make this job easy.

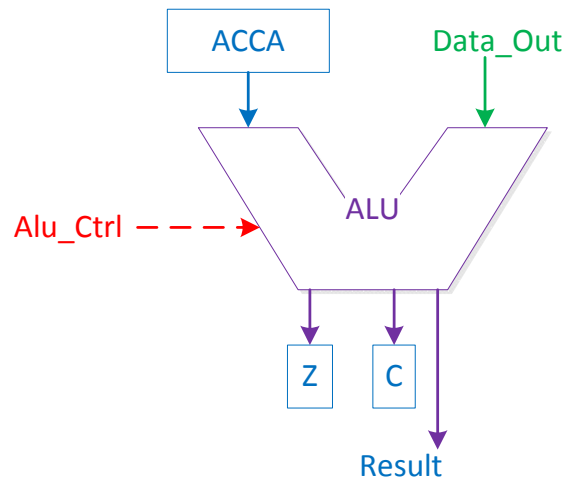


Figure 1: Arithmetic Logic Unit (ALU)

The ALU that you will build (see Figure 1) will perform 10 functions on 8-bit inputs (see Table 1). Please make sure you use the same variable name as the ones used in this lab. Do **NOT** make your own. The ALU will generate an 8-bit result (`Result`), a one bit carry (`C`), and a one bit zero-bit (`Z`). To select which of the 10 functions to implement, you will use `Alu_Ctrl` as the selection lines.

1 Prelab

- 1.1. Fill out Table 1 (Give *unique* values to each instruction.) How many bits should `Alu_Ctrl` be?
- 1.2. Write code to implement the ALU.

2 Lab

- 2.1. Write a Verilog program based off of your code written in the Prelab to implement the ALU.
- 2.2. Design the ALU using Verilog. **Make sure you deal with any unused bit combinations of the `Alu_Ctrl` lines.** (Hint: review `default` cases)

- 2.3. Simulate the ALU and test different combinations of DATA and ACCA. **Test ALL of the instructions.**
- 2.4. Create another program that will call your ALU module. In this module, have ACCA and DATA as external inputs as well as Alu_Ctrl. Output your results on two 7-segment displays. (Pinouts are included in Table 2)
- 2.5. Program your ALU code into your FPGA.

Table 1: Arithmetic Logic Unit Instructions

Alu_Ctrl	Instruction	Operation (Mnemonic)
	LDDA	Loads ACCA with the value on the Data bus. Z changes to 1 if Result == 0. (Load ACCA from Data)
	ADDA	Adds the value on the Data bus to the value in ACCA and saves the result in ACCA. C is the carry (out) from addition and Z is set if the result is 0. (Add ACCA and Data)
	SUBA	Subtracts the value on the Data bus from the value in ACCA and saves the result in ACCA. C is the carry (in) from subtraction and Z is set if the result is 0. (Subtract value in Data from ACCA)
	ANDA	Perform a bitwise AND of the value on the Data bus with the value in ACCA. Save the result in ACCA. C should be the logical AND of the value on the Data bus with the value in ACCA. Z is set if the result is 0. (AND of ACCA and value on Data)
	ORAA	Perform a bitwise OR of the value on the Data bus with the value in ACCA. Save the result in ACCA. C should be the logical OR of the value on the Data bus with the value in ACCA. Z is set if the result is 0. (OR of ACCA and value on Data)
	COMA	Replace the value in ACCA with its one's complement. C is set to 1 and Z is set if the result is 0. (Compliment ACCA)
	INCA	Increment value in ACCA. Z is set if the result is 0. (INCA ACCA)
	LSLA	Logical shift left of ACCA. C is set to the previous MSB of ACCA and Z is set if the result is 0. (Logical shift left ACCA)
	LSRA	Logical shift right of ACCA. C is set to the previous LSB of ACCA and Z is set if the result is 0. (Logical shift right ACCA)
	ASRA	Arithmetic shift right of ACCA. C is set to the previous LSB of ACCA and Z is set if the result is 0. (Arithmetic shift right ACCA)
	ZERO	Zero the value of ACCA. C is set to 0 and Z is set to 1. (Zero ACCA)
	RST	Reset ACCA to 0xFF. C is set to 0 and Z is set to 0. (Reset ACCA)

Table 2: CMOD-S6 DIP Assignments

DIP Pin	FPGA Pin	Wire	Wire	FPGA Pin	DIP Pin
1	P5	PIO01	PIO48	M2	48
2	N5	PIO02	PIO47	M1	47
3	N6	PIO03	PIO46	L2	46
4	P7	PIO04	PIO45	L1	45
5	P12	PIO05	PIO44	K2	44
6	N12	PIO06	PIO43	K1	43
7	L14	PIO07	PIO42	J2	42
8	L13	PIO08	PIO41	J1	41
9	K14	PIO09	PIO40	G2	40
10	K13	PIO10	PIO39	G1	39
11	J14	PIO11	PIO38	H2	38
12	J13	PIO12	PIO37	H1	37
13	H14	PIO13	PIO36	F2	36
14	H13	PIO14	PIO35	F1	35
15	F14	PIO15	PIO34	E2	34
16	F13	PIO16	PIO33	E1	33
17	G14	PIO17	PIO32	D2	32
18	G13	PIO18	PIO31	D1	31
19	E14	PIO19	PIO30	C1	30
20	E13	PIO20	PIO29	B1	29
21	D14	PIO21	PIO28	A2	28
22	D13	PIO22	PIO27	B3	27
23	C13	PIO23	PIO26	A3	26
24		VU	GND		25

3 Supplement: Verilog (3)

3.1 Parameterization

3.1.1 Macros

Listing 1: Macros in Verilog

```

1 'define Rst_Addr 8'hFF // Gets Expanded
2 assign data = 'Rst_Addr; // Tic is Necessary

```

3.1.2 Parameters

Listing 2: Parameters in Verilog

```
1 parameter num = 8;
```

Parameters are constants, not variables.

3.2 Operators

3.2.1 Ternary Operator

Listing 3: Ternary Operator in Verilog

```
1 assign y = sel ? a : b;
```

If `sel` is true, `y` is assigned to `a`, otherwise it is assigned to `b`.

3.2.2 Concatenation

Listing 4: Concatenation in Verilog

```
1 {a, b, c}
```

Bits are concatenated using `{ }`.

3.2.3 Comparison

Listing 5: Comparison in Verilog

```
1 if(a > b) y = a;
```

Compare `a` to `b`, if true set `y` equal to `a`. Other comparisons are listed in Listing 6.

Listing 6: Comparison Operators

```
1 > // Greater than
2 < // Less than
3 >= // Greater than or equal to
4 <= // Less than or equal to
5 == // Equality
6 === // Equality including X and Z
7 != // Inequality
8 !== // Inequality including X and Z
```

3.2.4 Logical Operators

Listing 7: Logical Operators

```
1 ! // Logical negation
2 && // Logical and
3 || // Logical or
```

3.2.5 Binary Arithmetic Operators

Listing 8: Binary Arithmetic Operators

```

1 + // Addition
2 - // Subtraction
3 * // Multiplication
4 / // Division (truncated)
5 % // Modulus

```

3.2.6 Unary Arithmetic Operators

Listing 9: Unary Arithmetic Operators

```

1 - // Change the sign of the operand

```

3.2.7 Bitwise Operators

Listing 10: Bitwise Operators

```

1 ~ // Bitwise negation
2 & // Bitwise AND
3 | // Bitwise OR
4 ^ // Bitwise XOR
5 ^^ // Bitwise XNOR
6 ^^ // Bitwise XNOR (also)

```

3.2.8 Unary Reduction Operators

- Produce a single bit result by applying the operator to all the bits of the operand.

Listing 11: Unary Reduction Operators

```

1 ~ // Bitwise negation
2 & // Bitwise AND
3 | // Bitwise OR
4 '& // Reduction NAND
5 '~| // Reduction NOR
6 ^ // Bitwise XOR
7 ^^ // Bitwise XNOR
8 ^^ // Bitwise XNOR (also)

```

3.2.9 Shift Operators

- Left operand is shifted by the number of bit positions given by the right operand.
- Zeros are used to fill vacated bit positions.

Listing 12: Shift Operators

```

1 << // Logical left shift
2 >> // Logical right shift

```

3.2.10 Precedence

Listing 13: Precedence

```
1 /* Highest Precedence */
2  !, ~
3  *, /, %
4  +, -
5  <<, >>
6  <, <=, >, >=
7  &
8  ^, ^^
9  |
10 &&
11 ||
12 ?:
13 /* Lowest Precedence */
```