
Exit Quiz -EE 231- Fall 2018

Name:_____

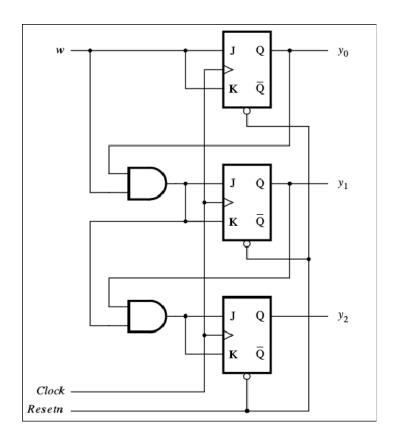1. Fill the table with the counting sequence of the circuit below.

Assume that w = 1, and the initial values of the flip-flops as shown in table.



y_0	y_1	y_2
0	0	0

2. For The above circuit,

(a) Calculate the Maximum frequency of operation.

(b) Determine if there are hold time violations.

assume that:

w = 1, $t_{su} = 0.6 \text{ ns}$, $t_h = 0.4 \text{ ns}$, $0.8 \le t_{cQ} \le 1.0 \text{ ns}$, and $t_{gate} = 1 + 0.1k$

where *k* is the number of input to the gates.