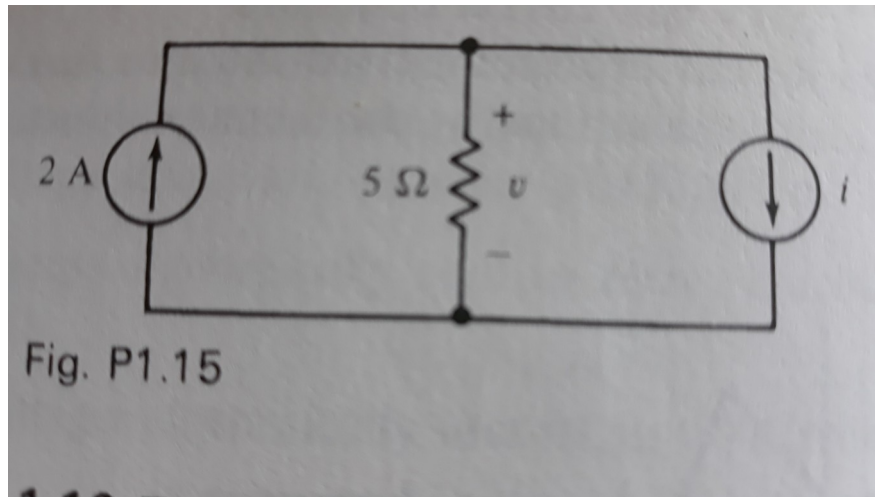


EE 211 Homework 1

From Textbook

I.- P 1.15 For the circuit shown in Fig P1.15, find the voltage 'v' for the case that

- a) $i = 1\text{ A}$
- b) $i = 2\text{ A}$
- c) $i = 3\text{ A}$



II.- P 1.16 For the circuit shown in Fig P1.16, find 'i' for the case that

- a) $v = 2\text{ V}$
- b) $v = 4\text{ V}$
- c) $v = 6\text{ V}$

Note: S stands for Siemens, which are the units for Conductances.

