

From Textbook

I.- P 1.26 Find the variables indicated for the circuits shown in Fig. P1.26 as shown below

II.- P 1.27 Find the variables indicated for the circuits shown below Fig P1.26

Note: These correspond to Problems 1.28 and 1.29 respectively of your textbook.

