

From Textbook

I.- Finish Drill Exercise 1.17 (started in class)

II. Given the circuit in the figure below.

1. Find the resistance  $R_{eq} = v_1 / i_1$ .
2. Find the voltage  $v_2$  in terms of the applied voltage  $v_1$ .

